

The how-to magazine of electronics...


ELECTRONICTM

Servicing & Technology

APRIL 1987/\$2.25

Oscilloscope: the eyes of the technician

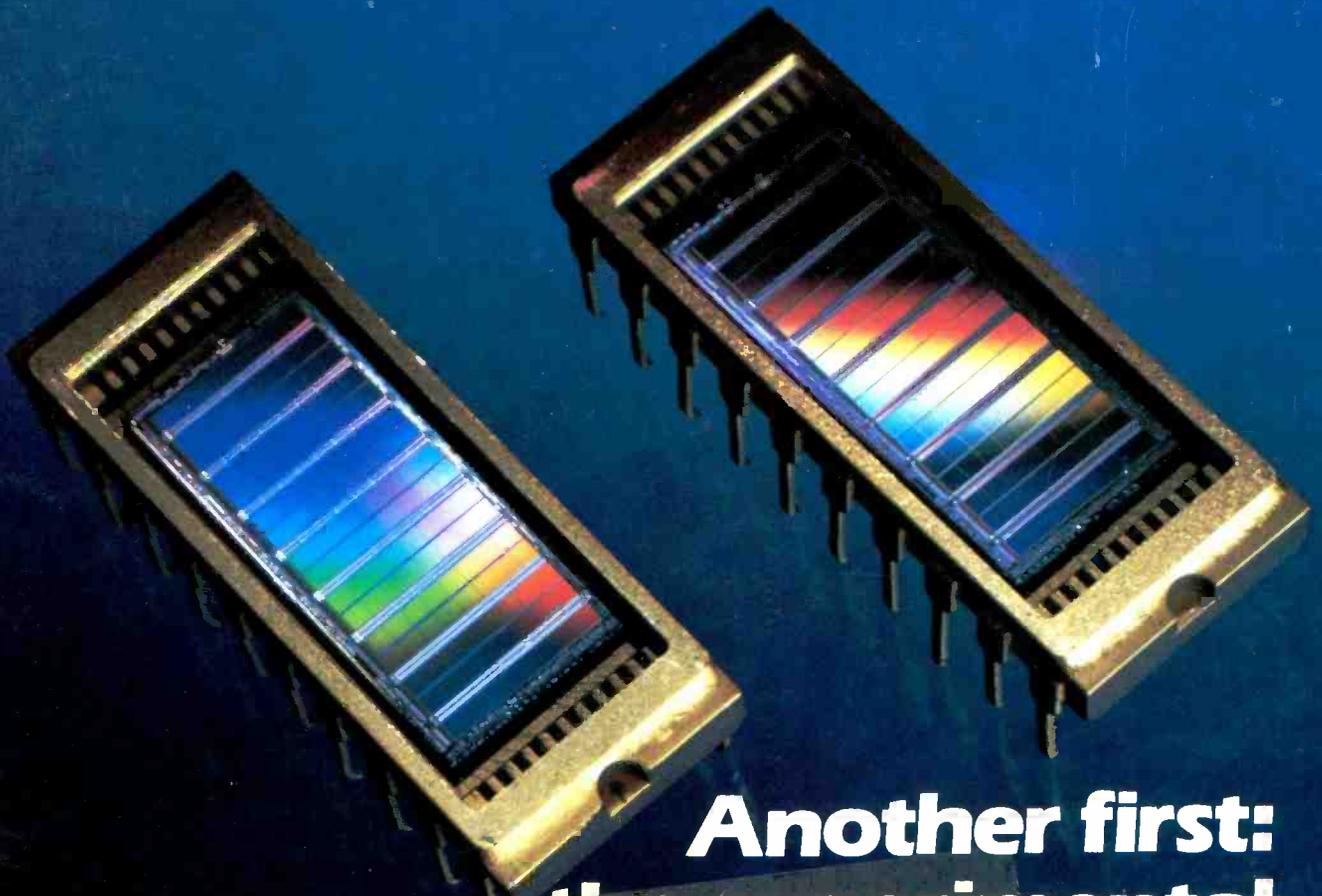Test lab: LCR meter • Troubleshooting horizontal ICs, Part 2



**Another first:
the experimental
4Mb CMOS DRAM**

Easier Testing. By Comparison.

*Scopemate 2.TM With Your Scope Or Ours,
Still The Best Price Solution
For Good/Bad IC and Component Testing.*

Now you can economically test all types of analog, digital and hybrid components—including resistors, capacitors, diodes and ICs with up to 40 pins—using a simple X-Y oscilloscope. In the field or on the bench, in-circuit or out-of-circuit. Without tedious pin-by-pin or contact-by-contact testing.

It's made possible by Scopemate 2TM from Beckman Industrial. All it does is plot voltage vs. current. Just a lot easier. A lot faster.

Scopemate 2 compares components known to be good with those to be tested, giving you a very accurate and fast way to identify bad devices. The voltage vs. current plot from a known good device is compared to the device under test. In fact, since there's no complex numerical test data to interpret, Scopemate 2 is ideal for less experienced personnel.

And, at \$495 it doesn't take too long to figure that Scopemate 2 may pay for itself in saved testing time. Real soon. Scopemate 2 comes with a simple yet comprehensive operator's manual, a complete set of leads, interconnect cables and plug-in transformer.

Although Scopemate 2 will work with just about any X-Y oscilloscope,



9020 20MHz Delayed Sweep Oscilloscope \$495.00

Vertical Accuracy: $\pm 3\%$
Time-based accuracy: $\pm 3\%$
Input Impedance: 1M ohm
35pF (2%)
Input Max. Voltage: 400V
(DC + pos. peak AC)
Sweep Delay Ranges:
10, 1.0, 0.1ms; 10, 1.0, 0.1 μ s
Mode: Normal, search, delay

Beckman Industrial CircuitmateTM Model 9020 offers capabilities seldom found on other scopes costing less than \$500.

Proven capabilities such as **delayed sweep** for easy bandwidth analysis, zoom-in for short-duration events, a variable holdoff function for a stable display of non-periodic signals—even beam finding to

Scopemate 2TM IC/Component Tester \$495.00

Test Method: Direct Visual Comparison (known good vs. device under test)

Test Sockets/Interface: 20 and 40-pin ZIF IC sockets; banana jacks

Power: 120 or 220VAC, 50/60Hz, 5VA max. (specify)

Circuit Test Voltage/Current: 14VAC RMS (voltage, approx.); 300 μ A AC RMS (current, approx.)

Pin Test selection: Push-button switch per pin.

locate and return trace to view regardless of control settings. And switchable X1/X10 probes give you more sensitivity for low frequency measurements, less circuit loading for high frequency measurements.

For real value, combine the 9020 and Scopemate 2 for performance and flexibility unmatched by systems costing \$1,500 or more. For less than \$1,000.

Both Scopemate 2 and our Circuitmate Model 9020 illustrate a simple commitment by Beckman Industrial—to provide service test instruments that meet your needs. Whether through advanced technology or value-oriented applications of proven technology, Beckman Industrial gives you the right features at the right price, with service test instruments built to rigorous standards of quality and reliability.

Visit your Beckman Industrial distributor today and find out how the ruggedly reliable Scopemate 2 and the 9020 Oscilloscope can meet your needs. And why they offer the best value around. By comparison.



*In Service
Instruments,
We're The One.*


Beckman IndustrialTM

Beckman Industrial Corporation, Instrumentation Products Division
A subsidiary of Emerson Electric Company
630 Puente Street, Brea, CA 92621
(714) 671-4800 • FAX: (714) 671-4874 • TLX: 188790
© 1986 Beckman Industrial Corporation

Circle (1) on Reply Card



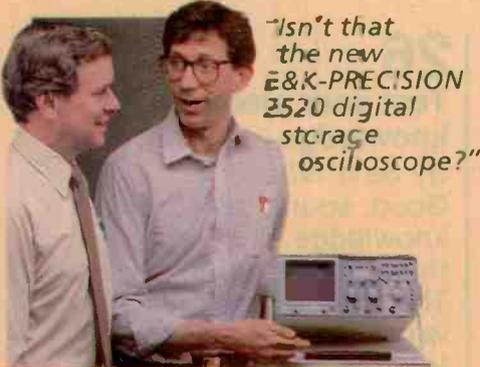"I thought a DSO that did all that would cost a fortune..."



"Isn't that the new E&K-PRECISION 2520 digital storage oscilloscope?"

"Right, Jim... It's quite a performer, with dual-channel real-time and digital operations, 2 megasample per second sampling and 1024 x 8 bit per channel storage. It's even got an analog output for a plotter."

"Those specs sound pretty good, Bob, but why a DSO? Won't your analog scope do the job?"

"This DSO really opens new doors... For instance..."



Let's say I need to look at a non-repetitive waveform..."


"Like our mechanical stress tests?"

"Exactly... or a one-shot pulse, or even a power line glitch... Looking at those on a regular scope is darn near impossible, even with a camera. On the 2520, I can pretrigger at 0%, 25%, 75%, or 100%. When the event pops, it's frozen on the screen. I can also compare test results from one event to the next."



"I see, Bob. Freeze one event on one channel, look at the new events on the second channel, and zoom in for a closer look. What other jobs will it simplify?"

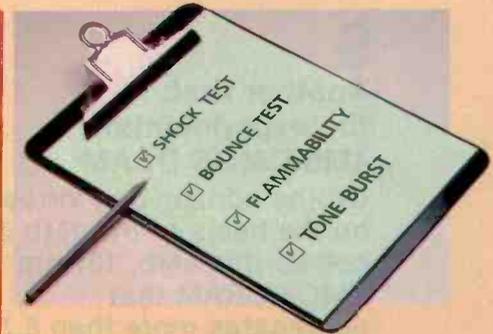"Here are just a few ideas: Shock testing — without trigger data loss; Bounce testing on switches and breakers; capturing a PCM tone burst; and flammability tests using two thermocouples... Our bio lab can even use it for



nerve response tests... Best of all the 2520 costs just \$1990."

"\$1990? I thought a DSO that did all that would cost a fortune. Where do I get mine?"

You can get your own 2520 from your local B&K-PRECISION distributor. Also ask about the new 2521 with automatic time and voltage measurements and optional 2502 waveform processor. For complete details and a free list of DSO applications contact:



BK PRECISION

DYNASCAN CORPORATION

6460 W. Cort and St. • Chicago, IL 60635


312-889-8870

International Sales, 6450 W. Cortland St., Chicago, IL 60635

Canadian Sales, Atlas Electronics, Ontario

South and Central American Sales, Empire Exporters, Plc/Inview, NY 11803

Circle 3) on Reply Card

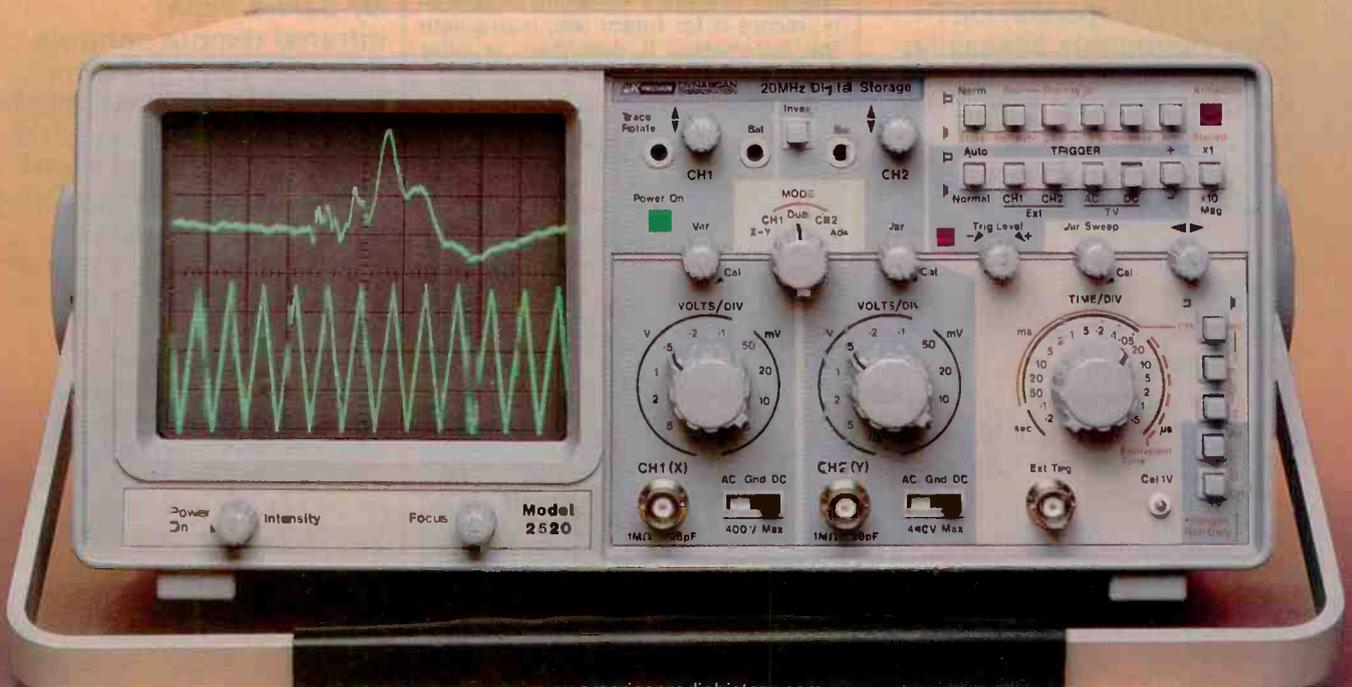

ELECTRONIC

Servicing & Technology

9

Another first: the experimental 4Mb CMOS DRAM

On the horizon and virtually on the heels of the 1Mb chip comes this 4Mb, 137mm² CMOS DRAM that aggregates more than 8.7 million circuit elements. A Technology article.

10

Oscilloscope: the eyes of the technician

By Conrad Persson

"See" into circuits as far as your oscilloscope will allow. Late-model scopes permit increased visual perception even though the scope, itself, may be smaller, lighter weight, even battery powered.

16

From the test bench: model AR-460-D LCR meter

By Carl H. Babcoke, CET


After thoroughly assessing the various features of this small, hand-held meter, the author reports that it is a valuable adjunct to other test equipment.

24

Learning from a tough dog repair


By Max Goodstein

Taming tough dogs leads to knowledge for the future because the lessons were learned the hard way.

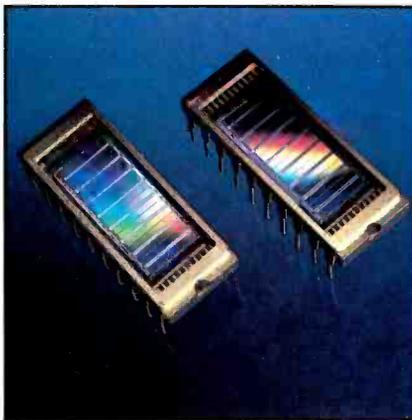

page 9

In less than two years since the 1Mb chip was introduced, these experimental 4Mb chips have been developed, promising four times as much dynamic access memory. (Photo courtesy Toshiba Corporation)

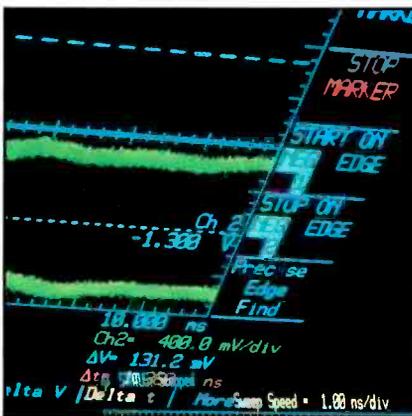

page 11

A digital storage oscilloscope allows the operator to store a waveform indefinitely, record it for future use, manipulate the information it describes, or print paper copy. (Photo courtesy Hewlett-Packard)

Departments:

- 6 Editorial
- 7 Feedback
- 8 News
- 9 Technology
- 54 Video Corner
- 56 Computer Corner
- 58 Audio Corner
- 60 Literature
- 60 Books
- 62 Readers' Exchange
- 63 Products
- 65 Photofact

26

Test your electronics knowledge

By Sam Wilson

Good, sound background knowledge should pull you through this month's quiz. The questions represent the variety of electronics information that a technician may need, unexpectedly, at any time.

43

Troubleshooting horizontal ICs, Part 2

By Homer L. Davidson

Concluding an article that began in the February issue of *ES&T*, the troubleshooting case histories detailed on these pages provide specifics that also should be useful in generalized applications.

50

What do you know about electronics? – Infrared remote controls

By Sam Wilson

Infrared remote controls have so much going for them that they are expected to replace both wired and ultrasonic controls ASAP. Best part: whereas jangling keys, for instance, can trigger ultrasonic, not even other infrared sources can fool infrared!

(Please note: to prevent duplication of effort, the author has decided to withdraw his promised serial presentation of CD circuits, theory and practice, leaving future discussions to Kirk Vistain's Audio Corner.)

LEADER

**NOW
Battery
Powered!**

Choose the New LBO-315 for ac/dc,
or the current LBO-325 for ac only.

**Sometimes it's hard to
go back for a scope!**

**60-MHz full-function
field-service Attache Case
Oscilloscope is so light and
small it will be taken
everywhere, every time.**

LBO-325 packs all the power and performance of a cumbersome, backbreaking, 60-MHz workbench oscilloscope into an easy-to-carry, ultra-compact, featherweight unit. Although its 3½-inch CRT is as big and clear as screens on large field-service scopes—LBO-325 weighs only 9 lbs. So it won't weigh field-technicians down, no matter how far afield they go! LBO-325 is so small it fits inside a 3-inch deep attache case with room to spare for a multimeter, service manuals and some tools. The ideal full-function scope for a cramped work area or crowded bench.

**Reduces the cost of
service calls.**

Time is money. A scope left in the vehicle takes time to retrieve. One kept in the shop causes repeat service calls. The LBO-325

For information Circle (4) on Reply Card




Attache Case Oscilloscope is so easy to carry and use, techs will take it everywhere, every time. And the time saved translates into extra profits for years to come.

Outperforms all other portables:

- 60 MHz • Dual channel • ALT TIME BASE simultaneously displays main waveform and any expanded portion
- ALT TRIG for stable display of 2 asynchronous signals • Bright, sharp 12-kV trace • Large 3½-inch PDA CRT • Illuminated graticule
- Comprehensive triggering • TV-V and TV-H sync separators • Variable trigger hold-off • Delay line shows sharp leading edges • CH-1 output drives low-sensitivity instruments
- Measures only 3 x 9 x 11½ inches • Weighs 9 lbs.

Two-year warranty.

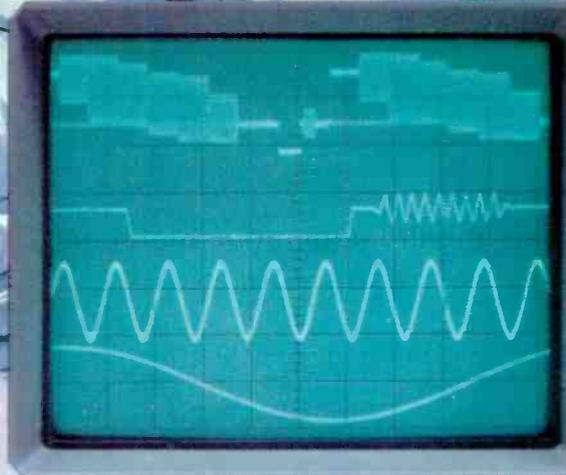Built tough to provide long use, LBO-325 is backed by Leader's 30-year reputation for reliability and by factory service depots on both coasts.



LBO-325 CRT is shown actual size.

Call toll-free
(800) 645-5104
In NY State
(516) 231-6900

Request an evaluation sample, our latest Test Instrument Catalog with over 100 outstanding products, the name and address of your nearest "Select" Leader Distributor, or additional information.

For professionals
who
know
the
difference.

LEADER
Instruments Corporation

380 Oser Avenue
Hauppauge, New York 11788
Regional Offices: Chicago, Dallas
Los Angeles, Boston, Atlanta
In Canada call Omnitrax Ltd.
(514) 337-9500

For Demonstration Circle (5) on Reply Card

Simplify

About 100 years ago, Henry David Thoreau left the life of society and went to dwell in the woods near Walden Pond in Concord, MA. "I went to the woods because I wished to live deliberately, to front only the essential facts of life, and see if I could not learn what it had to teach..."

His exhortation to the readers of Walden is "Simplicity, simplicity, simplicity! I say let your affairs be as two or three, and not a hundred or a thousand: Instead of a million count half a dozen, and keep your accounts on your thumbnail."

What would Thoreau think if he could see the world today? Far from becoming simplified since that time, life in general has become increasingly complex. Why, the technology of electronics alone has gotten so burdensome that we have to rely on acronyms and abbreviations just to communicate economically. Unfortunately, the proliferation of acronyms and abbreviations lends itself not only to economy but to confusion.

Take *pc*, for example. If you're going to be talking a lot about printed circuits, it helps to abbreviate it in speech or writing. Unfortunately, if you're not quite explicit, someone might get the idea that you're talking about a personal computer or a programmable calculator. And let's say you were in fact talking about a personal computer, how is the listener to know if you're talking about a *pc* in general or IBM's *PC*.

But that's just for starters. TVs and scopes have CRTs. And digital readouts are based on LEDs and LCDs. And modern circuits may be based on MOSFETS: PMOS, NMOS or CMOS. A rolling stone gathers no MOS, so they say.

But hold on. There's more. Lots more. And part of the problem is

that these abbreviations and acronyms get into the lingo but almost no one knows or remembers how, or precisely where they came from or what they mean. For example, many months ago we asked readers where the term "aquadag" (the conductive coating on a CRT) comes from. For those of you who missed it, we learned that it's a water-based (hence the "aqua" part) solution of Deflocculated Acheson Graphite. Aquadag was, and perhaps still is, a trademark of the Acheson Graphite Company.

And the unfamiliar and sometimes unintelligible acronyms and abbreviations continue to flow from the pens and tongues of the scientists and engineers, often to the increased confusion of us mere mortals. And we at *ES&T* have been as guilty as anyone.

Here's a modest suggestion. Any time you hear a term or abbreviation you're not familiar with (wait until LCDs get more popular and people begin tossing around beauts like "smectic" and "cholesteric"), don't be afraid to ask what it means and where it came from. And if you catch us bandying such terms about, let us know. And by all means, if you have a favorite abbreviation, acronym or obscure electronics term that you are familiar with, write and let us know. If you have a favorite whose meaning you're *not* familiar with, write and we'll try to find out what it means.

While Thoreau's idea of going back to the woods to simplify and live life in its elemental form won't work for most of us, at least we can make a stab at simplifying by clearing away some of the clutter in our working vocabulary.

Nile Conrad Pearson

Feedback

Mechanics also are technicians

I must take exception to Mr. Gus Robino's use of the phrase "...either reckless or auto mechanics" in his letter to July's Feedback. I am fortunate enough to have a friend who not only serves as the chief technician of a large multisystem cable TV operation, but who is also a highly competent mechanic. After watching him accomplish in an hour repairs which would have taken me a full weekend (and cost a crunched knuckle or two!), I've developed a healthy respect for qualified automotive technicians.

I doubt if Mr. Robino intended to belittle anyone, but my point is this: If we in the electronics servicing industry can put down so unthinkingly a profession whose contributions to our technological society are at least as vital as our own,

what right do we have to take offense when someone ignorant of electronics wrinkles his/her nose at the mention of "TV repairmen?"
Michael W. Moran, CET
Waupun, WI

ES&T is glad to be of service

Just wanted to express appreciation for the Reader's Exchange column. I have purchased several items from advertisers in this column. Thank you also for dividing the ads into the two categories: Wanted and For Sale. That was a significant improvement!

Garth Fisher

Assistant Professor Electronics
Walla Walla College
College Place, WA

This reader says "Go for it!"

...About the letter to Wallace Harrison from Robert J. Horsley (February 1987 *ES&T*): In considering a business in electronics, I would jump in and do it; the opportunities are there. Sure, the product is getting cheaper, but the

technology is changing and service methods are, too.

I do agree that just repairing televisions, solely, would be devastating, so diversify and service televisions, stereos, VCRs, CDs, to name a few. And what about industrial servicing of items such as alarms, closed circuit camera systems and 2-way communications. The service is out there; all you have to do is market your skills.

I have a business servicing (*the above equipment*) and also electrical wiring, and it looks better than anything I ever have thought of doing before....

A person could find another shop to purchase to acquire an already established clientele and foothold. To start from scratch, a person could do it for \$6,000 to \$8,000, easily, plus good contacts.

Because I felt that those letters in the February issue were so discouraging, I feel compelled to write my opinion.

Mike Shelton Sr.
Burlington, NC

ES&T

Fluke breaks the old mold.



Dollar for dollar the Fluke 37 breaks into the market with more features for the money than any other bench DMM. It's bold new design includes built-in handle and storage compartment, and it has all the high performance features of the world's best, most reliable 3½-digit DMMs.

Autoranging, to eliminate guesswork. Audible Continuity, so you don't have to look at the display. An exclusive analog and digital display. Superior EMI shielding. Plus a two-year warranty.

And, how many other bench/portable meters give you these features? Min-Max recording, for monitoring signals. 38 components dedicated exclusively to input protection. Relative mode, to help you calculate changes in readings. And Fluke's patented Touch Hold, to give you an extra set of hands when you're taking critical measurements.

None. Only the Fluke 37.

For more information call 1-800-426-0361.

FLUKE
®

© 1986, Fluke

Circle (6) on Reply Card

April 1987 *Electronic Servicing & Technology* 7

Car audio installation tape now available from EIA/CEG

A videocassette training tape, "Basic Car Audio Installation," has been prepared by EIA's Consumer Electronics Group (CEG) and is now available through its product services department.

This 30-minute videotape introduces you, the electronics technician, to the increasingly complex subject of car audio installation. It guides you in the correct layout and design of a car stereo installation facility, covering basic as well as specialized tools needed for the installation.

Among key topics covered in this training tape are safety in the shop; how to treat the car, from pre-installation checkout to demonstrating the completed job; the technical resources available for information about specific types of vehicles, dashboard dismantling, speaker sizes and antenna locations; and types of speaker wiring found in the automobile.

For additional information on this videocassette, which is priced at \$30, contact the CEG Product Services Department, Electronic Industries Association, 2001 Eye Street NW, Washington, DC 20006 (202-457-8782).

Permanent injunction prohibits Certification scheme

In December 1986, Stan Haring of Olympia, WA, agreed to a permanent injunction by the state of Washington that prohibits him from offering a certification program under the auspices of an organization he called the American Association of Certified Electronics Technicians (AACET).

In a consent decree signed by both parties, Haring, who has been an instructor at Olympia's Puget Sound Community College, agreed to pay a civil penalty to the state of Washington and to desist from any future violation of state law.

The office of the International Society of Certified Electronics Technicians (ISCET) became aware of AACET when some industry people mistook AACET's policies for those of ISCET. ISCET members and certification administrators advised ISCET of the AACET plan to offer certifica-

tion for a fee without qualifying examinations to instructors, military and other technicians working in the industry.

The test offered by Haring, was reviewed by both ISCET and Don Hatton, the Director of Product Services for the Consumer Electronics Group of the Electronics Industries Association (EIA/CEG). In the opinion of both, it was in no way an adequate measurement of the complexities of professional servicing.

ISCET made the initial inquiry to the Washington Attorney General and cooperated fully in the ongoing investigation. Jim Parks CET, ISCET Chairman from Winter Springs, FL, points out that, "ISCET recognizes the right of other organization to offer certification programs. . . However, they have an obligation to ensure that their testing procedures are meaningful and that the designation instills public assurance of a minimum level of technical competence."

ISCET, a non-profit society headquartered in Fort Worth, TX, has certified more than 21,000 technicians as ISCET Certified Electronics Technicians since the program's inception in 1965. **ES&T**

The how-to magazine of electronics

ELECTRONIC

Servicing & Technology

Editorial, advertising and circulation correspondence should be addressed to: P.O. Box 12901, Overland Park, KS 66212-9981 (a suburb of Kansas City, MO); (913) 888-4664.

EDITORIAL

Nils Conrad Persson, *Editor*
 Carl Babcoke, *Consumer Servicing Consultant*
 Dan Torchia, *Group Managing Editor*
 Marjorie Riggan, *Associate Editor*
 Joy Culver, *Editorial Assistant*
 Darryll Fortune, *Editorial Assistant*
 Ailsa Carter, *Editorial Assistant*
 Ramona M. Vassar, *Editorial Assistant*

CONSULTING EDITORS

Homer L. Davidson, *TV Servicing Consultant*
 Christopher H. Fenton, *Circuit Fabrication Consultant*
 Bud Izen, *Computer Servicing Consultant*
 Victor Meeldijk, *Components Consultant*
 Kirk G. Vistain, *Audio Consultant*
 Sam Wilson, *Electronics Theory Consultant*

ART

Kevin Callahan, *Art Director*
 Tim Lynch, *Graphic Designer*

BUSINESS

Cameron Bishop, *Group Vice President*
 Eric Jacobson, *Publisher*
 Greg Garrison, *Sales Manager*
 Stephanie Fagan, *Promotions Manager*
 Kelly Hawthorne, *Promotions Coordinator*
 Dee Unger, *Advertising Supervisor*
 Julie Chilson, *Advertising Coordinator*

ADVERTISING

Regional advertising sales offices are listed in classified pages.

ADMINISTRATION

R. J. Hancock, *President*
 Doug Riemer, *Circulation Director*
 Jo Ann DeSmet, *Circulation Manager*
 Dee Manies, *Reader Correspondent*

ELECTRONIC SERVICING & TECHNOLOGY is the "how-to" magazine for technicians who service consumer electronics equipment. This includes service technicians, field service personnel and avid servicing enthusiasts, who repair and maintain audio, video, computer and other consumer electronics equipment.

SUBSCRIPTION PRICES: one year \$18, two years \$30, three years \$38 in the USA and its possessions. Foreign countries: one year \$22, two years \$34, three years \$44. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks delivery for change of address. Allow 6 to 8 weeks for new subscriptions.

PHOTOCOPY RIGHTS: Permission to photocopy for internal or personal use is granted by Intertec Publishing Corp. for libraries and others registered with Copyright Clearance Center (CCC), provided the base fee of \$2 per copy of article is paid directly to CCC, 21 Congress St., Salem, MA 01970. Special requests should be addressed to Eric Jacobson, publisher. ISSN 0278-9922 \$2.00 + 0.00



Member, Audit Bureau of Circulation



Member, American Business Press



Member, Electronic Servicing Dealers Association

INTERTEC
 PUBLISHING CORPORATION

©1987 All rights reserved.

Another first: the experimental 4Mb CMOS DRAM

Make way for the 4-megabit CMOS dynamic random access memory.

Just 21 months ago (July 1985 issue) *Electronic Servicing & Technology* brought you news of the then-awesome 1Mb chip developed by Toshiba. In May, 1986, *ES&T* reported that the access time for this semiconductor chip—previously headlined as “Faster than a speeding bullet...” —had been accelerated further by Toshiba integrating refresh operation circuits directly on the chip. Now this.

Toshiba's 4Mb DRAM incorporates more than 8.7 million circuit elements on a 137mm² chip. A single chip can hold information equivalent to approximately 16 pages of a metropolitan newspaper, a volume that would require 16 256K DRAMS currently in use. Such high integration makes it possible to make microcomputers, personal computers and office automation devices even more compact than they are today.

The 4Mb DRAM features low power consumption, high speed and enhanced reliability. Power consumption is only 300mW during operation, and 2.5mW in standby mode, despite the fast access time of 80ns.

Formidable hurdles were overcome to make this chip a reality. First, microlithography must achieve 1.0μm minimum feature size (minimum feature sizes used for the 256K DRAM and 1Mb DRAM were 1.8μm and 1.2μm, respectively).

Next, the chip's basic capacitor had to be minimized, but reliability is jeopardized when the quantity of charge that can be stored in a capacitor is reduced. Toshiba solved this problem by digging a groove into the silicon substrate and turning the side wall of the groove into a capacitor, making it possible to store sufficient electric charge in the small memory-cell area.


To make this possible, however, a new technique had to be devel-

oped using arsenic glass in order to evenly disperse impurities at a high density and suitable depth into the groove side walls.


Another problem associated with such large-scale memories is “soft errors” that can alter the information: alpha particles coming from radioactive contaminants in the packaging material and in the chip, itself, that cause fluctuation in the amount of charge stored in the capacitor. This was solved by altering the impurity concentration in the substrate.

The CMOS structure was chosen to permit low power consumption and high operating speed. Power consumption was reduced even further by engineering a method of activating only one-fourth of the circuitry, instead of the entire chip.

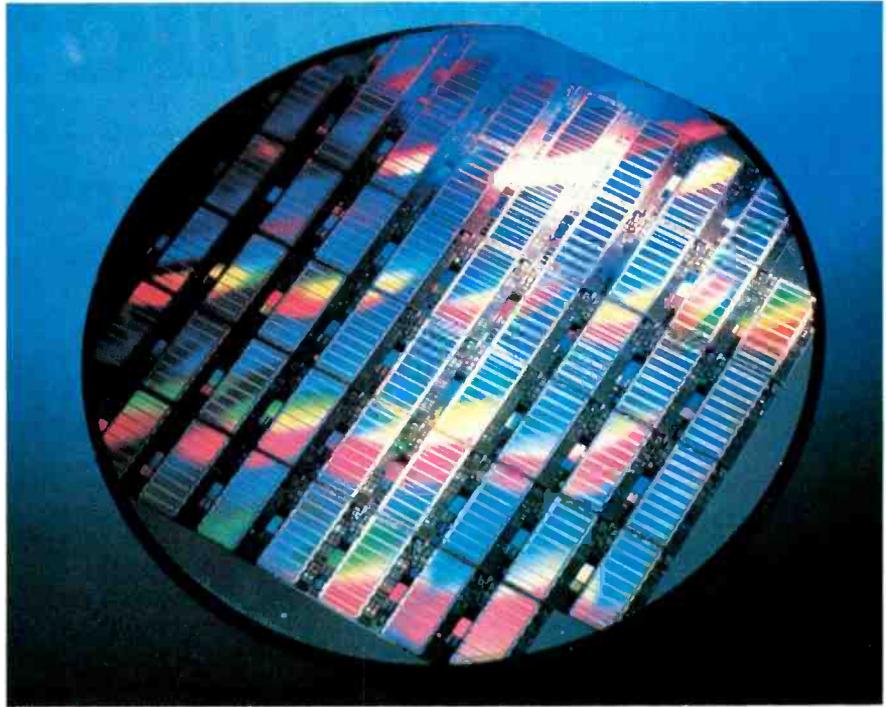Editor's Note: The devices and technological advances that *ES&T* reports in this department may take months, even years to reach



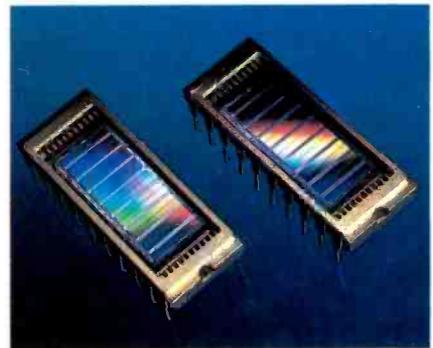There are approximately 50 4-megabit DRAMs fabricated on this silicon wafer—more than 435 million circuit elements. (Photos courtesy Toshiba Corporation)



Four-megabit dynamic RAM (DRAM) can hold the equivalent of 16 newspaper pages of information.

the servicing bench as part of consumers' improved or more compact electronic equipment. (Some may prove impractical to manufacture or to market and, therefore, will never be a servicing concern.) We believe, however, that our readers, with their technical orientation, are interested in all the exciting developments that may ultimately impact the electronics industry.

Oscilloscope: the eyes of the technician

By Conrad Persson

The oscilloscope is the servicing technician's electronic "eyes." You can't directly observe what's going on in a circuit, but you can attach the probes of the oscilloscope and look at the screen and observe just exactly what's going on.

The ability of a technician to use an oscilloscope to see what's going on in a circuit is limited by the limitations of the oscilloscope, its ease of use, and the skill of the technician in using the oscilloscope.

Improvements in modern scopes

All of the electronics technological innovations that are being developed are being incorporated into today's oscilloscopes. Integrated circuits are cramming so much into such small packages that instrument manufacturers are able to increase the sophistication and capabilities of their scopes while at the same time reducing their overall size. The reduced power consumption of these units makes battery-operated portable oscilloscopes practical. Digital circuitry makes possible digital storage oscilloscopes that can cap-

ture and hold waveforms indefinitely. Microcomputer control simplifies setup and operation.

Some other improvements in scope sophistication that have been introduced in recent years are such things as oscilloscopes with LCD readout, which are so small that you can almost put them in your pocket. Yet another development is the addition of a digital readout on the front of the scope (or sometimes to the screen itself). With this, you can read the value of amplitude or period directly in digital numbers so you don't have to count graticule markings, check the knob settings and calculate these values.

Digital storage oscilloscopes

One of the most exciting developments in oscilloscopes in recent years is the digital storage oscilloscope (DSO). It offers a number of significant advantages beyond the capabilities of analog oscilloscopes.

One of the primary advantages of digital storage oscilloscopes is their ability to store the signal being observed. In fact, this one

capability results in several advantages. For one thing, the capability to record a waveform makes it possible to capture a waveform, store it and compare the stored image to the same waveform from the same point in another unit.

Manipulating the information

Many digital storage oscilloscopes have other capabilities that can help simplify the troubleshooting task. Some DSOs, for example, have a printout capability so that you can print out any portion of the waveform you've captured and take it with you to examine at your leisure, or to make marks on or write your comments on. Sometimes this kind of activity with the thinking process it encourages helps you figure out what the problem is.

Still another capability that some DSOs offer is interface connections. If you have a personal computer, depending on the kind of computer it is, you can transfer the recorded information to the computer to record the waveform permanently on floppy disk, or to manipulate the information in any



number of ways, again stimulating the troubleshooting thinking process. Just think: If you were ever working on the same unit, or a similar unit with a similar problem, you'd have a record of what you discovered the first time you ran into the problem.

Multichannels make it easier

Most DSOs have more than one channel available. Just think of the implications of that. Let's say you're monitoring an intermittent problem as discussed previously, but you have a strong suspicion that it's related to or caused by another condition, say a sag of the 120V line voltage. With a multichannel DSO, you can put one set of probes on the testpoint of the unit under test and another set on the incoming power line and record both signals. Then when the intermittent occurs, you can look at both waveforms at the same time and compare them.

If the waveform at the test point starts doing funny things at about the same time as the power line voltage drops, you have a strong reason to suspect that the low

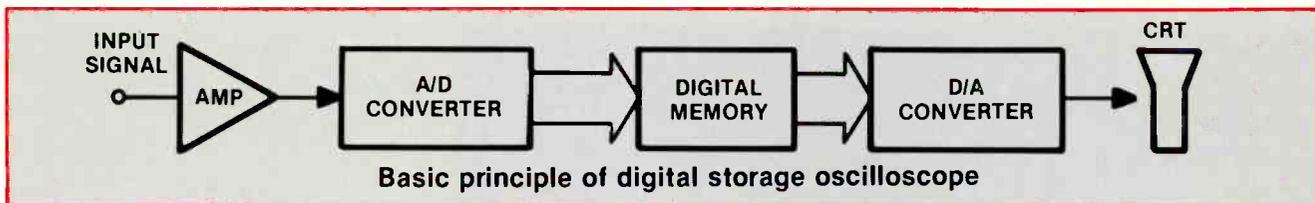


Figure 1. Simplified diagram of digital storage oscilloscope.

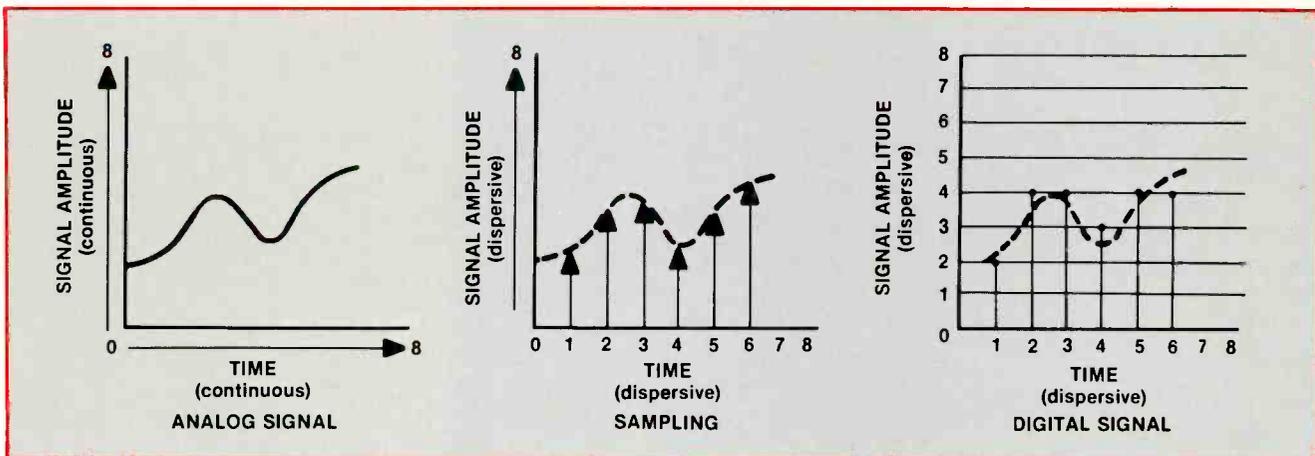


Figure 2. Each sampled analog signal is quantized to digital.

| | | | | | | |
|------|---|---|---|---|---|---|
| TIME | 1 | 2 | 3 | 4 | 5 | 6 |
| DATA | 2 | 4 | 4 | 3 | 4 | 4 |

Table 1. Signals quantized into digital are stored in memory.

voltage is the cause, and you can take corrective measures.

DSO operating principles

Until the introduction of the DSO, the term *storage oscilloscope* was applied to an oscilloscope that uses a storage CRT. This type of oscilloscope stores the displayed waveform as a trace on the scopeface.

The digital storage oscilloscope makes possible the storage of waveforms as bits in a digital memory circuit. Take a look at Figure 1, a simplified block diagram of a DSO. Instead of being amplified and applied directly to the deflection plates of the CRT, the waveform in a DSO is first converted into its original equivalent

and stored in memory. To reproduce the waveform on the CRT, the data stored in the memory is sequentially read and converted back into an analog signal.

The A/D (analog to digital) converter converts the analog signal into a sequence of digital bits, in which form it is stored in memory. The amplitude of the analog signal varies continuously in time. In order to be converted into a digital signal, the analog signal is sampled at intervals. The analog value of the signal at each sample point is converted into a binary number (quantized) and stored. See Figure 2 for an idea of how the A/D process proceeds.

In order to be displayed as an analog signal on the scopeface, the

digital data representing the signal must be converted back to an analog signal. This is accomplished through a digital to analog (D/A) converter.

DSO circuit structure

The circuit structure of one DSO, the DSS 5040 manufactured by Kikusui, is shown in the block diagram in Figure 3. Its features are largely typical of digital storage oscilloscopes. The major blocks are the vertical deflection circuit, the horizontal deflection circuit, the data acquisition and processing circuit, the CRT circuit, the CAL circuit and the power supply circuit.

Vertical deflection circuit

The purpose of the vertical deflection circuit is to provide the voltage signal that deflects the beam spot vertically on the CRT screen. The input signal is impedance-matched and amplified by the CH1 or CH2 pre-amplifier to a level suitable for driving the subsequent stage of the circuit. Under the control of the oscilloscope's microcomputer the channel selector chooses the channel to

IN THE FUTURE...



TECHNICIANS WILL HAVE TEST EQUIPMENT YOU MAY DREAM ABOUT TODAY...

A Technician may probe with just two test leads, an amplifier, TV, or cellular telephone, and his test equipment may read out:

**"LEAKY SINGLE JUNCTION NPN TRANSISTOR,
BREAKING DOWN AT 15.3 VDC"**

Imagine, if you will, that even an average technician would be able to locate, **IN SECONDS**, defective components in a blown amplifier, a lightning-damaged TV, anything with transistors, diodes or capacitors;

EVEN MAJOR DISASTERS WITH MULTIPLE DEFECTIVE COMPONENTS...

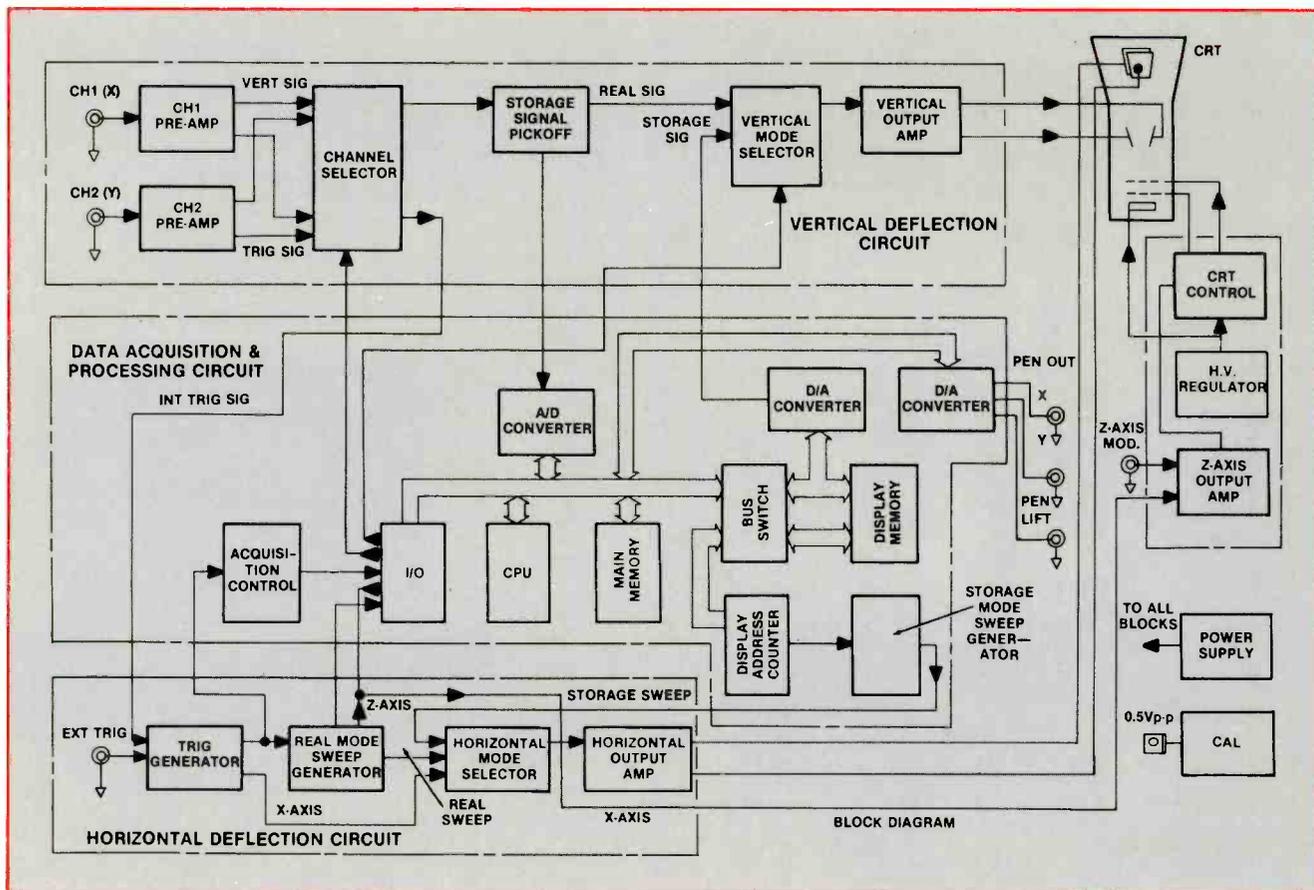


Figure 3. This complete block diagram traces signals' I/O, conversion, memory and reconversion process.

be used. Then the signal is fed to the STORAGE SIGNAL PICK-OFF circuit. The signal picked off is fed to the A/D converter. The vertical mode selector picks either the storage signal or the real signal. The selected signal is fed to the vertical output amplifier that amplifies the signal to a sufficient level for vertically deflecting the CRT beam.

Horizontal deflection circuit

The purpose of the horizontal deflection circuit is to provide the voltage signal that deflects the beam spot horizontally on the screen. The circuit includes a trigger circuit and a sweep circuit. It also acts as an X-axis deflection circuit for X-Y operation.

The trigger generator selects either the signal fed from the channel selector or the EXT TRIG signal, and generates a triggering signal for sweep and an AUTO signal to indicate the presence or absence of the triggering signal.

When in the X-Y mode or EXT HOR mode, the circuit operates as an X-axis amplifier.

The real mode sweep generator,

which is synchronized with the triggering signal, generates a sweep signal for operation in the real mode.

The horizontal mode selector selects the storage mode sweep signal, the real mode sweep signal, or the X-axis signal. The selected signal is amplified by the horizontal output amplifier to a sufficient level for horizontally driving the CRT beam.

Data acquisition and processing circuit

This circuit converts the analog input signal into a digital signal for storage, and provides interpolation on the stored data for reproduction of the analog signal on the CRT screen. The various data items fed through the I/O port are read by the CPU, which provides the control signals for the various circuits. The waveform data fed from the A/D converter is stored in the main memory. The CPU provides interpolation and other processing on the data. The processed data is transferred to the display memory. Except during the transfer periods, the con-

tents of the display memory are constantly sent to the D/A converter and displayed on the CRT.

The CRT circuit

The CRT circuit provides the high voltages for the CRT and controls the Z-axis of the CRT. The Z-axis amplifier amplifies the Z-axis signal to a sufficient level for controlling the brightness of the CRT beam spot. The HV regulator provides a high voltage for the CRT. The voltage is controlled by the CRT control circuit via the Z-axis output amplifier, to control the CRT beam spot intensity and focus.

The CAL circuit and the power supply circuit

The CAL circuit provides a reference signal for calibration of the probe and for operation of the amplifiers in the non-calibrated state. The reference signal is a square wave of 0.5Vp-p, with voltage accuracy better than 2%.


The power supply circuit provides supply voltages (145V, 12V, -12V, and 5V) for the various circuits of the oscilloscope. **55T**

WELCOME TO THE FUTURE

INTRODUCING A NEW IDEA IN TEST EQUIPMENT;
SO REVOLUTIONARY IN FACT, IT HAS TWO PATENTS (pending).
ELECTRONIC DESIGN SPECIALISTS, INC.

E05-59C
SEMIANALYZER[®]

\$489

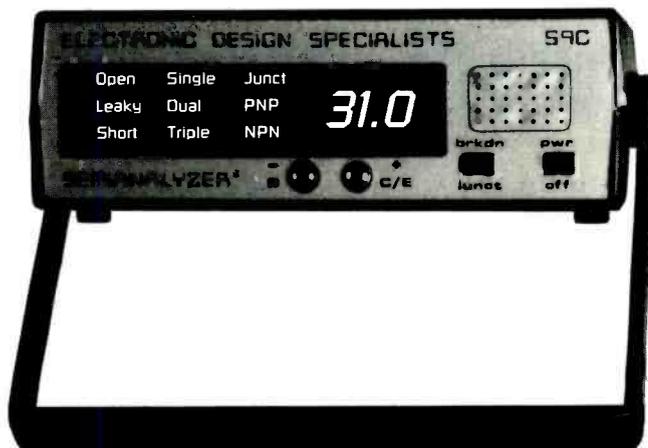

- Reads condition (OPEN LEAKY SHORTED), polarity (NPN PNP), and number of junctions (SINGLE DUAL TRIPLE) of semiconductors.
- Uses only TWO test leads, not three.
- Measures junctions IN CIRCUIT with circuit turned off.
- Audible beep tones for circuit conditions; keep your eyes on your work.
- Displays voltage breakdown (non-destructive) of semiconductors AND CAPACITORS up to 175 Volts DC; finds leaky components FAST!
- LISTEN to junction breakdown with built-in amplifier; FINDS NOISY DIODES, TRANSISTORS AND CAPACITORS.
- Displays Zener diode voltages IN CIRCUIT!
- Made in U.S.A. with TWO YEAR limited warranty on PARTS AND LABOR.

Designed in cooperation with technicians who make their living on commission, the SEMIANALYZER[®] 59C is designed to make you a faster, less frustrated "Supertech". We're so sure, we are offering this money-back guarantee: Use the 59C on your most difficult "dogs" for 60 days, and if it hasn't earned its keep, ship it back for a full refund.

LIMITED SPECIAL OFFER: Semianalyzers ordered before June 30 will receive a free pair of specially designed Pomona adjustable length, curved tip test probes (a \$20.00 value).

VISA or MASTERCARD ORDER TOLL FREE 24 Hours/Day—7 Days/Week:
1-800-544-4150 (Florida 305-726-7416) or send check or money order to:

ELECTRONIC DESIGN SPECIALISTS, INC.

P.O. Box 9609
Coral Springs, FL 33065

Please include \$7.50 to cover P&H. Florida residents add 5% sales tax.

Circle (7) on Reply Card

Model AR-460-D hand-held LCR meter

Model AR-460-D from American Reliance is a small, hand-held digital LCR meter that can test resistances, inductances and their dissipations as well as capacitances and their dissipations. A large center knob selects any of five inductance ranges providing full-scale readings between $200\mu\text{F}$ and 2H , any of seven capacitance ranges allowing full-scale measurements between 200pF and $200\mu\text{F}$, or any of six resistance ranges providing 200Ω to $20\text{M}\Omega$ full-scale readings.

The $3\frac{1}{2}$ -digit readout has sharp $\frac{1}{2}$ -inch LCD black-on-white numbers with automatically placed decimal, automatic minus sign and *LO BAT* battery-condition annunciators. *LO BAT* is displayed during the last 5% of the battery life. An alkaline 9V battery is needed, but is not supplied with the meter. Operating life of the 9V battery is estimated at 100 hours of operation. Or, an external ac-to-9Vdc adapter (not supplied with the meter) can be plugged in for ac-line operation. A spare 2A fuse is provided. The test leads are only about five inches long, because excessive lead length can produce incorrect inductance and capacitance readings. Sampling time is fast, about 0.4s, or more than two per second.

Model AR-460-D is small, officially measuring $17.2\times 8.7\times 3.4\text{cm}$ and weighing 350 grams (approximately $6\frac{7}{8}\times 3\frac{1}{2}\times 1\frac{1}{2}$ inches) with a weight of less than a pound with battery and probes.)

Overrange for any function or range is indicated by a single, non-flashing *1* at the left when none of the other digits is showing.

A feature in the AR-460-D that was new to me is a switch position for *D* or dissipation of inductors




Model AR-460-D from American Reliance is a small meter for hand-held or bench use. It tests resistances, inductances and dissipations, also capacitances and dissipations.

and capacitors during their tests. The dissipation reading is said to be an indication of the *Q* of the inductance or capacitance. For example, a dissipation reading of 0.01 divided into 1 (the reciprocal of the number) equals a *Q* of 100. A dissipation of 0.10 divided into 1 shows a *Q* of 10, and a poor dissipation (*D*) reading of 0.50 divided into 1 calculates to a *Q* of only 2; a very low reading. This example probably is not accurate, but it serves as an illustration.

Also, the manufacturer states the *D* factor for out-of-circuit inductors and capacitors is based on the internal parallel leakage of capacitors and the internal series resistance of inductors.

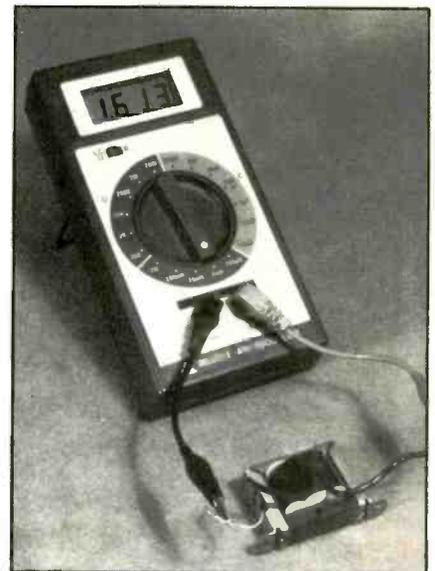Dissipation appears on the readout up to 19.99 before overrange begins. However, I have not been



Model AR-460-D indicates the filter choke has a 1.613mH inductance. This choke has a core made of laminated iron. The LCR/D switch is in the LCR (left) position.

able to find out if the dissipation reading is displaying voltage, current, resistance or something else. It is not a simple thing to produce a high dissipation reading by using series or paralleling resistances. This complex subject will be discussed later.

Measuring inductances

To test inductances, you only have to connect two test leads, select an appropriate range, and read the meter for inductance and dissipation.


To include in-circuit tests and establish good safety habits, you should follow a few preliminary steps that have nothing to do with inductance tests. First, unplug the ac power to the unit under test and short the B+ dc voltage to ground for a few seconds. Next, make cer-

EFFECTS OF FLYBACK SHORTED TURNS

The AR-460-D's 5-inch test leads alone were connected to flyback pins 3 and 9 during the following tests, which were performed out-of-circuit.

| Defect | Inductive value | Dissipation |
|--------------------------|-----------------|-------------|
| No defect; Normal | 108.7mH | 0.00 |
| Rect filament shorted | 106.6mH | 0.07 |
| 4 turns shorted | 51.9mH | 0.82 |
| AGC winding shorted | 67.9mH | 0.11 |
| HV winding shorted | 17.3mH | 0.38 |
| 1 turn of solder shorted | 104.6mH | 0.17 |
| pin 3 shorted to pin 4 | 04.5mH | 2.82 |

Table 1. When the AR-460-D was connected to the *primary* of an old TV flyback and several windings were shorted in sequence, the primary inductance changed in unpredictable ways, as explained in the text.

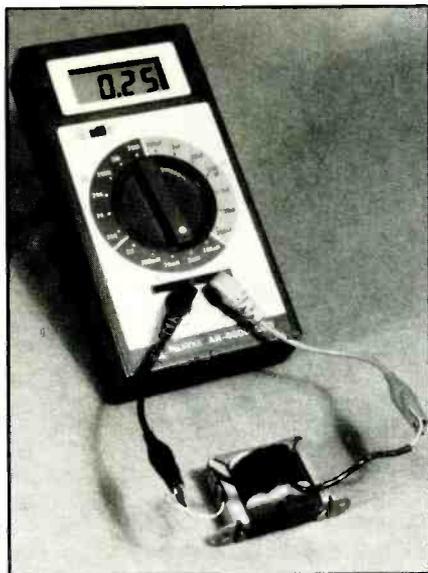

The same filter choke is being tested again, but now the LCR/D switch has been moved (to the right) to the D or dissipation position, showing a readout of 0.25.

tain the ac and dc loads across the inductance are not too low (refer to later discussion) for valid readings. Finally, use a test lead to short across the inductance to be sure no dc voltage is stored there in the associated circuit.

Now attach the two AR-460-D test leads to the inductor. (Use only the two short test leads, if possible. If not possible, use the shortest that will reach). Turn on meter power with the side-mounted sliding switch. Starting with the 2H range, rotate the large knob toward lower inductances until a usable reading with several digits is obtained. For this, the panel sliding switch should be in the LC position. Slide the LC-Ω/D to the right or D position for dissipation reading. A low reading around 0.01 is best, but it probably

will be much higher in-circuit because of circuit loading. If the inductor is a television flyback, write the reading at the edge of the schematic for future use. Remember, of course, that the flyback primary will measure much lower (usually) in-circuit vs. the out-of-circuit inductance. Both readings should be recorded for future use.

Dissipation—No doubt you are wondering if the dissipation reading can indicate shorted turns or an excessive load on a transformer. The specific answer depends on the type of transformer. The general answer is *yes*, usually. Table 1 shows the primary inductance of an old-type flyback along with the dissipation readings for various simulated, massive shorts.

Shorted turns in some windings affect the primary inductance and dissipation very little, while others produce large changes. Of course, a flyback (especially an old type) does not have the same tight magnetic coupling to every turn in every coil from the source winding. In a theoretically perfect transformer, a short across *one* turn in any winding would reduce the inductance of all windings to zero. Late-production flybacks more nearly approach the ideal than the one used as example, but the old one is better for some measurements.

Flyback analysis—Some of the

EFFECTS OF SHORTS IN A POWER TRANSFORMER

| Defect | Inductive value | Dissipation |
|----------------------------|-----------------|-------------|
| Normal; No defect | 1.099H | 0.18 |
| 6Vac winding shorted | .047H | 2.60 |
| Either B + winding shorted | .024H | 1.23 |
| Both B + windings shorted | .016H | 1.76 |

Table 2. With a small power transformer connected, a short across any secondary winding reduced the primary inductance to almost zero. That is evidence of tight magnetic coupling.

readings in Table 1 make sense to me; others do not. For example, the HV rectifier-tube filament winding (I told you it was old!) consists of two turns of highly insulated wire loosely looped around the flyback's insulated core. It seems rather obvious that shorting it out should make little difference in the primary inductance, and that was true. I was surprised that one turn of solder around the core

near the windings reduced the inductive value so little. I experimented with several locations and could not find one that reduced the first reading very much. Perhaps the *doughnut* covering over the coils was too large or not shaped right, preventing the solder *wire* from being near the original windings.

Although I can't explain why some of the shorts gave the inductance and dissipation readings that are recorded, there is a good explanation for the very low inductance and very high dissipation when pin 4 was shorted to pin 3. This winding has pins 9 and 3 at the ends, with pin 4 at a tap and pin 8 (not tested) as another tap. Shorted turns anywhere in the 9/8/4/3 pins' total winding produces a very low inductance with a very high dissipation reading. This might not be true of other windings because they are not located with the 9/3-pin winding, either physically or magnetically.

Power-transformer analysis—Table 2 shows the inductance and dissipation readings of a 60Hz laminated-core small power transformer. All secondary loads have been disconnected to simulate out-of-circuit operation.

Notice in Table 2 that any shorted winding reduces the primary inductance virtually to zero as it increases the dissipation reading far above normal. Evidently all windings have tight magnetic coupling with all other windings, which explains why a shorted secondary winding (or a shorted secondary load) can cause the primary winding of a power transformer to overheat and possibly burn out.

Conclusion: With 120Vac 60Hz transformers, the inductance and dissipation readings made by model AR-460-D are accurate and dependable.

Other tests—A variety of chokes and transformers were checked for inductance, with good results. One indicator, evidently intended for use in a speaker crossover network, tested 1.908mH with a dissipation of 0.03. With opportunities for in-circuit tests limited, other tests were made to simulate in-circuit loading problems.

Paralleling errors—Table 3 shows

THE EFFECTS OF PARALLEL CAPACITANCE AND RESISTANCE ON INDUCTANCE READINGS.

| Inductance in parallel with: | Resulting Inductance | Dissipation |
|------------------------------|----------------------|-------------|
| 0.00 | 108.9mH | 0.00 |
| 0.005 μ F | 112.1mH | 0.00 |
| 0.01 μ F | 114.9mH | 0.01 |
| 0.025 μ F | 120.9mH | 0.01 |
| 0.05 μ F | 144.0mH | 0.01 |
| 0.10 μ F | 192.6mH | 0.01 |
| 0.15 μ F | 347.4mH | 0.07 |
| 0.22 μ F | OVERRANGE | 0.63 |

| Inductance in parallel with: | Resulting Inductance | Dissipation |
|------------------------------|----------------------|-------------|
| OPEN | 108.9mH | 0.00 |
| 50k Ω | 108.7mH | 0.01 |
| 10k Ω | 108.1mH | 0.07 |
| 5k Ω | 106.1mH | 0.14 |
| 2.5k Ω | 98.0mH | 0.32 |
| 1100 Ω | 72.8mH | 0.68 |
| 470 Ω | 23.1mH | 1.43 |
| 220 Ω | 2.4mH | 5.29 |

Table 3. The first table shows the effects on the inductance of the test flyback's primary winding when capacitances of increasing values are paralleled. Notice that larger capacitances increase the inductance readings. In the second table, resistors are paralleled across the primary winding. Low-value resistances reduce the reading excessively. In summary, best accuracy of in-circuit inductance readings can be obtained when the combined loads are 0.001 μ F (or smaller) and 10k Ω (or larger).

the changes of inductance when the same flyback was paralleled by various values of capacitors and resistors. Values of the loading resistors and capacitors were not tested precisely; high accuracy was not needed here.

One conclusion from the *paralleling* of various capacitors across an inductance is that they *increase* the reading, with even a 0.005 μ F producing a noticeable increase. Stray capacitance of the wiring and most small ceramic capacitors can be tolerated in-circuit without increasing the reading sufficiently to produce significant errors.

The meter is more tolerant of *paralleling resistances*, showing virtually no change down to 10k Ω . Below 10k Ω , each step of decrease reduced the inductance reading. *Resistors reduce the reading.*

Therefore, the in-circuit recommendations for paralleling an inductor are for less than 0.001 μ F and more than 10k Ω . Larger capacitances and lower resistances will produce incorrect readings of unacceptable magnitude. Remember, these figures apply only to inductances in the range near 100mH. Possibly lower inductances can tolerate larger paralleling capacitances and lower resistances; the combinations are endless.

Series errors—Table 4 shows similar readings of the inductance when capacitors and resistors of various values were connected *in series* with the inductor. No value of capacitor could be found that gave a correct reading when connected in series. Values of 0.22 μ F and smaller produced near-zero

THE EFFECTS OF SERIES CAPACITANCE AND RESISTANCE ON INDUCTANCE READINGS

| Inductance in series with: | Resulting inductance | Dissipation |
|----------------------------|----------------------|-------------|
| A SHORT | 108.9mH | 0.00 |
| 0.22 μ F | 0.35mH | OVERLOAD |
| 0.15 μ F | 49.2mH | OVERLOAD |
| 0.10 μ F | 139.3mH | OVERLOAD |
| 0.068 μ F | 352mH | OVERLOAD |

| Inductance in series with: | Resulting inductance | Dissipation |
|----------------------------|----------------------|-------------|
| A SHORT | 108.9mH | 0.00 |
| 33 Ω | 108.2mH | 0.06 |
| 100 Ω | 108.1mH | 0.18 |
| 470 Ω | 107.6mH | 0.69 |
| 4.7K | 102.1mH | 7.40 |
| 10K | 90.2mH | 17.86 |

ANY VALUE CAPACITOR IN SERIES WITH AN INDUCTOR PRODUCES A WILDLY INACCURATE READING. A SERIES CAPACITOR IS NOT RECOMMENDED.

SMALL VALUES OF RESISTANCE IN SERIES WITH AN INDUCTOR DO NOT AFFECT THE INDUCTANCE GREATLY.

Table 4. Listing one shows the results when capacitors of various values are placed in series with the test yoke's primary winding. Some of the readings that resulted were higher, some were lower, but none was correct. During your tests, therefore, make certain there are no coupling capacitors between the inductance and the meter. Listing two shows the gradual decrease in reading according to an increase of resistance in series with the primary winding. In summary: There should never be a capacitor in series with an inductor during inductance tests; and do not allow more than 100 Ω in series with the inductance during these tests.

readings, while progressively larger capacitances gave increasingly larger readings (some far above the correct one). But most important: all values produced dissipation overrange. Do not knowingly connect any capacitor in series with an inductor being tested by the AR-460-D.

It is strongly suggested that any inductance being measured should be direct coupled (no series capacitor) to the meter and have 100 Ω or less of resistance in series with the inductance.

Specifications - Full-scale accuracies of the five inductance ranges are specified as $\pm 2\% + 1$ digit for the 200 μ H range, $\pm 1\% + 1$ digit for the 2mH, 20mH and 200mH ranges, and $\pm 2\% + 1$ digit for the 2H range. These accuracies apply only when the dissipation is lower than two.

Measuring capacitances

Capacitor measurements are just as easy as inductor measurements. For in-circuit tests, unplug all ac power from the unit being tested and make certain the paral-

Lose weight fast



TEST INSTRUMENTS, LOGIC PROBES, OSCILLOSCOPE PROBES, AND SOLDERING STATIONS FOR SERVICE ENGINEERS

Light weight reliable instruments and tools: portable enough to be a help, not a hindrance; affordable enough to turn a profit not a loss. If your solution calls for ultra-portable test instruments, universally adaptable oscilloscope probes or test lead kits, logic probes or solder/desolder equipment, call OK Industries today. We serve the U.S. with a network of over 750 distributors.

CALL OK TODAY

800 523-0667

IN NEW YORK STATE DIAL (914) 969-6800


BEING THE BEST IS A MATTER OF BEING OK.




4 Executive Plaza, Yonkers, New York 10701 USA
Telex 126091 OK NYK. Telex 232395 OK NY UR
Phone (914) 969-6800
Fax (914) 969-6650



Circle (8) on Reply Card

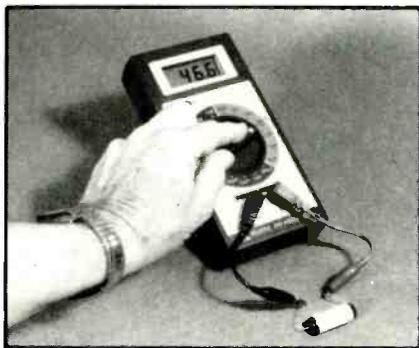

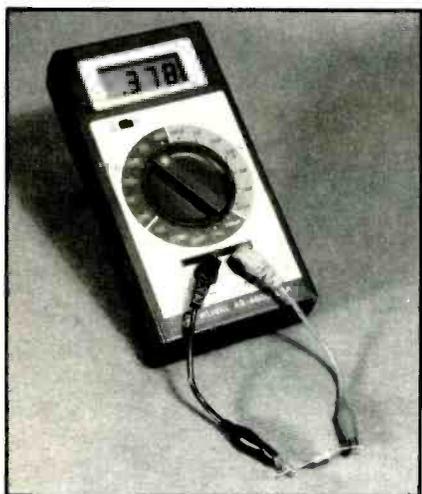On the 200nF range, the capacitor tests 46.6nF (or 0.0466 μ F) with a dissipation of 0.01. The small size of the instrument is shown in comparison to an operator's hand.



As shown, a resistor measured 0.378M Ω (or 378k Ω) on the 2M Ω range of resistance. Resistors do not have dissipation factors, and the correct resistance reading is obtained on both settings of the LCR/D switch.

lel ac and dc loads across the suspected capacitor are not too low in value, and no ac or dc components are in series with the capacitor. Use a test lead to short across the capacitor for a couple of seconds to drain all voltage that might be stored in the capacitor or in the associated circuits.

Attach the AR-460-D's two short test leads to the capacitor. If these are not long enough, use the shortest leads that will reach. Begin with the front panel switch moved to the left in the LC position. Rotate the bar knob to the capacitance sector and to a range believed to be higher than needed. When a reading is obtained, turn to a lower range to obtain more active digits (three or four preferred) on the readout, and then slide the

front-panel switch to the D or dissipation position. Evaluate the condition of the capacitor from these two readings. If the readings raise questions, disconnect one end of the capacitor from the circuit and repeat the tests. Out-of-circuit tests usually are more accurate.

Dissipation (D) readings will identify capacitors that have excessive internal leakage. Most small capacitors should read no higher than 0.02. Many tested 0.00. Electrolytics produce much higher readings. One 12 μ F read 0.20, and a 38 μ F gave a reading of 0.24. Experience soon will show you what is acceptable with these as starting points.

Load resistances across capacitances—When a capacitance is being measured by the AR-460-D, paralleling a resistor across the capacitance reduces the meter reading. *The amount of meter-reading error depends on the capacitance value vs. the resistance value.* In a sense, therefore, it is impossible to assign a single resistance and call it a minimum in-circuit load resistance if accurate capacitor readings are essential.

In Table 5, for example, three capacitors of decaded values were subjected to a series of decreasing resistances. From the mass of data, three examples were chosen for each capacitor value. The largest value shows the highest resistance that reduced the capacitance reading perhaps 2% to 5% (enough accuracy for many uses) with increased dissipation. The next lower resistance value provides for a comparison, while the lowest resistance value reduced the capacitance reading too much, thus producing unacceptable readings with very high dissipations. These show the limits for in-circuit capacitance tests.

As you probably have guessed, larger capacitance values can tolerate lower resistance values. Two examples showed such limited effects that they were not placed on a table. Here is number one: A 12.36 μ F electrolytic capacitor had a dissipation of 0.06. With a 40 Ω load resistor, it measured 12.31 μ F with 0.38 dissipation.

Number two: Similarly, a 38.6 μ F electrolytic capacitor having a dissipation of 0.20 was paralleled by a 40 Ω resistor, changing the readout to 38.5 μ F with a dissipation of 0.31. The answer is clear. If the circuit and capacitor are properly discharged first, it should be possible to test most power-supply capacitors in-circuit. There are always some reservations according to the specific circuits.

Measuring resistances

Resistances are measured in six decaded ranges exactly as is usual with digital multimeters. Be certain the probes are not connected to any circuit with ac or dc voltages.

Five of the resistance ranges (200 Ω , 2k Ω , 20k Ω , 200k Ω , and 2M Ω) are rated at accuracies of $\pm 0.5\%$ plus one digit. The 20M Ω range is rated at $\pm 1\%$ plus one digit.

All ranges are the low-power type. Only 3.13V was measured across the open test leads. However, any reading that does not produce overrange measures only slightly above 0.2V, which is not sufficient to cause conduction in solid-state junctions (except perhaps some germanium).

In the absence of any Bureau of Standards test resistors, the AR-460-D and a digital multimeter were used almost simultaneously to measure many resistances, with both showing almost identical readings, which implied that the AR-460-D's accuracy was good. Of course, there is no dissipation factor when resistors are tested.

Miscellaneous facts and comments

Perhaps some technicians are not familiar with the prefix *nano* as used to identify three capacitance ranges on the AR-460-D. (By using nano, the capacitance ranges can be decaded easily.) Remember, nano is located between micro and pico in the complete sequence: UNITS, MILLI, MICRO, NANO and PICO.

There are simple rules for converting a reading in one prefix to another. For example:

- Change the reading in nano to micro by moving the decimal *three places to the left.*

RESISTANCES PARALLELED ACROSS CAPACITORS SIMULATE IN-CIRCUIT LOADING

| Parallel defect | Capacitance reading | Dissipation factor |
|-----------------|---------------------|--------------------|
|-----------------|---------------------|--------------------|

NOMINALLY 0.001 μ F

| | | |
|---------------|-----------------|-------|
| NONE | 0.00124 μ F | 0.02 |
| 100k Ω | 0.00122 μ F | 1.18 |
| 15k Ω | 0.00104 μ F | 9.31 |
| 10k Ω | 0.00095 μ F | 14.67 |

NOMINALLY 0.01 μ F

| | | |
|----------------|----------------|-------|
| NONE | 0.011 μ F | 0.01 |
| 10k Ω | 0.010 μ F | 1.32 |
| 2.3k Ω | 0.0097 μ F | 6.84 |
| 1,000 Ω | 0.008 μ F | 17.13 |

NOMINALLY 0.10 μ F


| | | |
|----------------|----------------|-------|
| NONE | 0.094 μ F | 0.01 |
| 1,000 Ω | 0.0921 μ F | 1.63 |
| 700 Ω | 0.090 μ F | 2.07 |
| 100 Ω | 0.076 μ F | 17.26 |

Table 5. Extensive experiments showed that paralleling a resistance across a capacitor reduced the capacitance reading and increased the dissipation factor. However, the amount of capacitance decrease depended on the capacitance-value vs. the resistance-value. Study these three examples. Notice that lower resistances can be used when the capacitances are larger.

- Change the reading in nano to pico by moving the decimal *three places to the right*.
- Change the reading in pico to micro by moving the decimal *six places to the left*.

A complete listing of all the combinations for all five prefixes is extensive, and probably would cover an entire page. Basically, remember that all adjacent prefixes are separated by three decimal places. The biggest problem is remembering whether the decimal is moved to the left or to the right. Incidentally, between units and pico there are 12 decimal places.

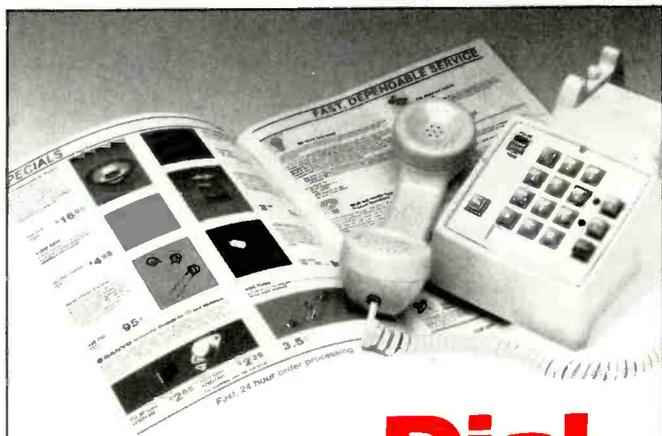Color coding is used on the AR-460-D's front panel. Around the large black selector knob are three areas where the ranges are marked. A black sector with light gray lettering identifies the five inductance ranges. Higher at the left, a brown segment with light gray lettering identifies the six resistance ranges, and at the right of the large




Dial -n- Deliver

MCM's "Dial & Deliver" Service is nothing new — we've been doing it for years!

We discovered it takes more than a wide selection of quality products at low prices to keep you satisfied. It takes performance! And performance means fast, courteous service and quick delivery.

Discover the difference MCM can make. The parts and equipment you need are only a phone call away. We know you'll like our selection and prices. You'll be even more impressed with how well we perform!

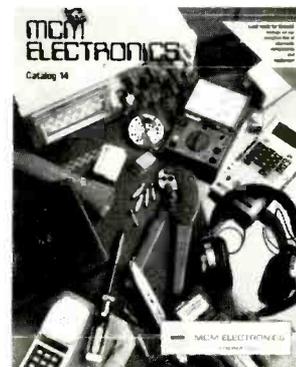Catalog #14
Now Available
Call TODAY for
your FREE copy



**Call TOLL-FREE
1-800-543-4330**

(In Ohio call 1-800-762-4315)
(In Hawaii or Alaska 1-800-858-1849)





MCM ELECTRONICS
858 E. CONGRESS PARK DR.
CENTERVILLE, OH 45459
A PREMIER Company

Source No. ES-20

Circle (11) on Reply Card

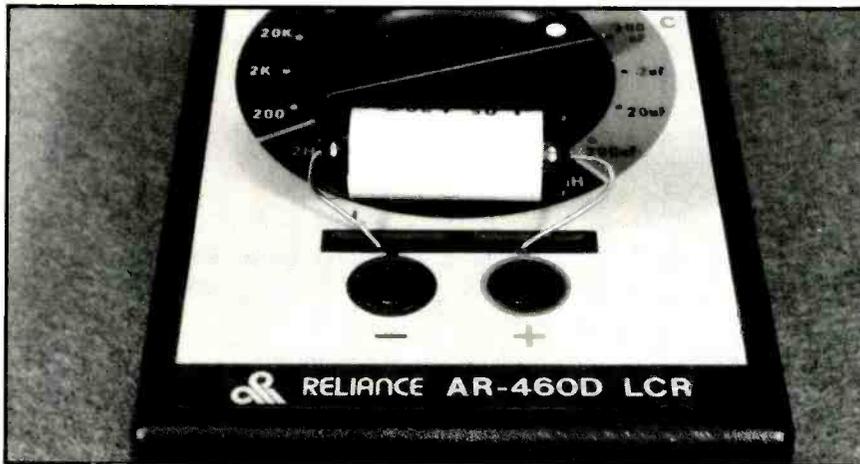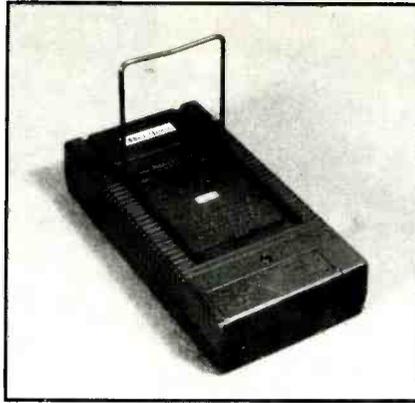The multipurpose wire on the meter's back can be used as a tilt stand, as a carrying bail or as a hanging point for suspension. The latter two uses are performed with the wire bail in the holes nearer the top; while the lower holes are used when the bail functions as a tilt stand or for storage and transportation. In the photograph, the bail is extended to form the tilt stand.



One spring-loaded slit-type connector is located above each input jack, and they are connected to the input jacks. Lightweight components with short leads can be plugged into the slit connectors during tests. A capacitor is shown here being checked, but small chokes or resistors can be connected the same way.

knob is a red segment with black lettering and the seven capacitance ranges marked.

Another feature causing model AR-460-D to closely resemble many small digital multimeters is the two input jacks for banana plugs. In addition, these input jacks are connected to two long narrow spring clips inside the meter just above the two jacks, thus allowing an out-of-circuit capacitor, for example, to be plugged into the two clips for testing. For components that can be connected that way, the tests are much faster.

Another useful feature is the loop of heavy wire on the back side that can be stored in a groove of the plastic cabinet and secured by a plastic catch. When desired, the wire can be extended from the meter body and used as a stand. It can be used to hang the meter from above as a carrying bail.

It is important that technicians who operate the AR-460-D understand the normal readouts for in-

ductance, capacitance and resistance when the test leads are shorted and open. For example:

- **Inductance**—With test leads shorted together, the readout showed almost zero inductance with excessive dissipation. In fact, the 200 μ H and 2H range dissipations overranged. With the test leads open, overrange is indicated for all ranges with very low dissipation readings of approximately 0.01 to 0.02.

- **Capacitance**—With the test leads shorted together, the 200pF, 20 μ F and 200 μ F ranges indicated overrange with excessive dissipation and varying readings, while the remaining ranges indicated near zero with varying dissipation. With an open circuit at the test leads, the capacitance ranges read 0.00 but the dissipation readings jumped constantly high or low erratically. The operation manual states this is normal.

- **Resistance**—When the test leads were shorted together during resistance tests, the readout indi-

cated near zero for all ranges. With the test leads open, all ranges activated the overrange readout. These resistance functions are the same as those in digital multimeters.

What is a dissipation factor

In the American Reliance model AR-460-D, circuit operation of the dissipation factor is a mystery to me. Neither the literature nor the operation manual gives the basic principle of operation or states what is being measured or how.

The instruction sheet says the D factor evaluates the internal leakage of capacitors or the internal series resistance of inductors, but it does not explain why the primary inductance of a power transformer is reduced to near zero when one of the secondary windings is shorted.

The operation manual says a 1,000Hz signal is used for capacitance and inductance measurements. Oscilloscope tests showed 1,000Hz sine waves continuously at the test probes when capacitance and inductance tests are selected.

Many experiments were tried in efforts to discover how the dissipation factor was measured. For example, when the meter range was not changed but a capacitance box produced capacitances from very small to 0.22 μ F, the ac current certainly increased with each increase of capacitance. Problem: The current change did not track with the dissipation readings made simultaneously. Many other tables were made involving other parameters, but none pointed to a reasonable explanation.

Comments

In just a few weeks, American Reliance Model AR-460-D has become a valued part of my bench test equipment. Of course, it does not replace a digital multimeter, but an AR-460-D and a good DMM work very well together.

Model AR-460-D sells for \$199.95. Therefore, in many shops, each bench man can have one permanently without sharing it with several technicians. It is a meter that in the first few months will save more than the meter's cost in time saved.

ES&T

Philips ECG



Unveiling America's best value in Multimeters!

Now at your Philips ECG Distributor the best-performing, competitively priced new line of ECG Multimeters.

Now your multimeter dollars buy you the best values when you invest them in our new line of ECG multimeters. Whether you need one or fifty, for bench work or on-site testing, Philips ECG gives you accuracy, performance and quality features at a very competitive price. Call your Philips ECG distributor today. He has the widest range of best alternatives in multimeters.

Your opportunity to get the best alternative at competitive prices is repeated again and again in a wide range of electronic replacement parts from Philips ECG. And there are hundreds of Philips ECG distributors nationwide who offer you fast service and great prices on over 4,000 different types

of ECG devices that meet or exceed original equipment specs and replace more than 240,000 industry types.

From Multimeters to micro-processor ICs, your local Philips ECG distributor has the equipment, replacement parts and cross-reference manuals you need. He'll put them in your hands fast. Call him today.

If it's ECG, it fits. And it works!

Philips ECG

*A North American Philips Company
Dedicated to Excellence.*



CALL 1-800-225-8326 FOR YOUR NEAREST PHILIPS DISTRIBUTOR

Circle (12) on Reply Card

www.americanradiohistory.com

**ELENCO PRODUCTS
AT DISCOUNT PRICES!**



**20 MHz Dual Trace Oscilloscope
\$349.95 MO-1251**

Two 1x, 10x 100 MHz probes, diagrams and manual included. Write for specs.
35 MHz \$499.95 MO-1252



**GF-8016 Function Generator
with freq. counter**


\$219.95

Sine, Square, Triangle
Pulse, Ramp, .2 to 2 MHz
Frequency .1 thru 10 MHz

GF-8015 without freq. meter \$169

Triple Power Supply XP-660

0-20V @ 1A
0-20V @ 1A
5V @ 5A

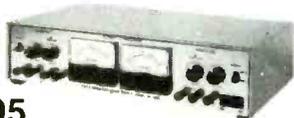

\$149.95

Fully regulated, short circuit protected
with 2 limit cont. 3 separate supplies

3 Amp Power Supply XP-650



\$119.95

0-40V @ 1.5A
0-20V @ 3A
Fully regulated, short circuit protected
current limit control

**Color Convergence Generator
SG-200**



\$69.95

Finest in the industry
10 rock steady patterns

**Multimeter with Capacitance
and Transistor Tester**

Model CM-1500

\$64.95

Reads volts, ohms, current,
capacitors, transistors, diodes



Digital LCR Meter

\$148.95



Model LC-1800
Measures: Inductors
Capacitors, Resistors
Inductors .1uH to 200H
Capacitor .1Pf to 200uF
Resistor .01 Ohms to 20M Ohms
Ranges 6 Ind, 7 cap, 7 res

C&S Sales, 8744 W North Ter.
Niles, IL 60648 800-292-7711
312-459-9040 ASK FOR CATALOG
Add 5% P&H (\$10 Max per item)
IL Res. add 7% sales tax



Circle (13) on Reply Card

Learning from a TOUGH DOG TV repair

By Max Goodstein


In every technician's life, one difficult troubleshooting incident makes him wish he had chosen another profession! For me, the problem television was a Panasonic CT9000 (Photofact 2046-1).

The television receiver lost horizontal hold after 30 minutes. By spraying the horizontal-oscillator components with a cooling spray, I hoped to identify the heat-sensitive one. Cooling IC401, the horizontal-oscillator integrated circuit, appeared to help, so I replaced it. The problem was unchanged.

All components of the horizontal oscillator were tested in-circuit

and a few tested out-of-circuit, but no defects were found. Then I noticed transistors Q554 and Q553 in a system called horizontal-oscillator disable circuit, with a direct connection to the horizontal oscillator in IC401 at pin 14. When the HV current, or the HV amplitude or both become excessive, the circuit operates to force the oscillator far out of frequency where the hold control cannot achieve locking.

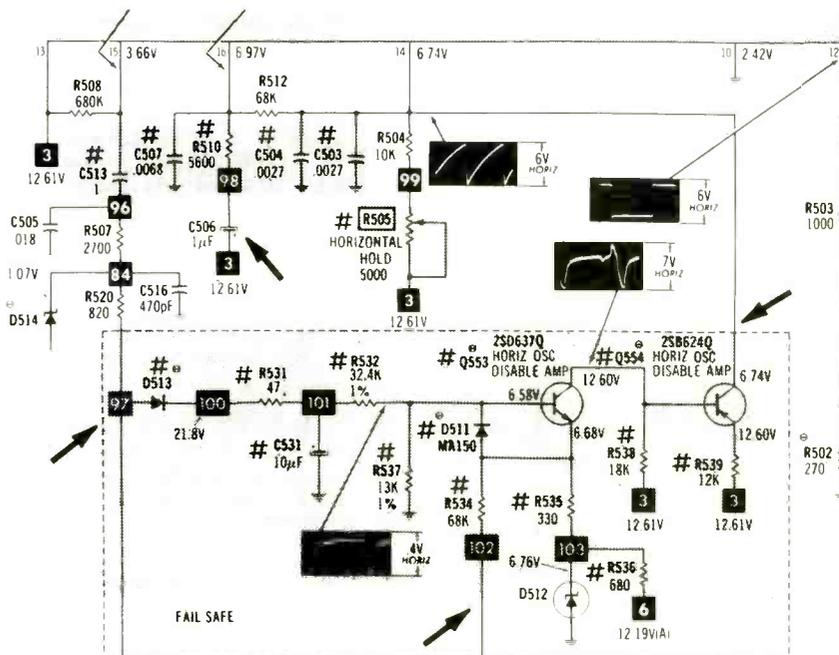Evidently, the disable circuit was being triggered. But the question remains: Was the high voltage actually excessive, or was the



In the fail-safe horizontal-oscillator *disable* circuit, excessive amplitude of flyback pulses at D513 produces dc voltages at the Q553 base that exceed the emitter voltage, which is stabilized with a zener. The resulting Q553 collector current lowers the Q554 positive base-to-ground voltage. This is forward bias for PNP Q554, which saturates Q554, causing nearly zero volts E/C. Therefore, the +12.6V source is connected through 12kΩ R539 direct to the oscillator pin 14 in IC401, forcing the oscillator far out of frequency. The same action occurs when a less-positive voltage from the low end of the HV winding reduces the Q553 emitter voltage, thus producing C/E current in Q553 that in turn triggers Q554, etc. Horizontal frequency problems also can be caused by components in the *frequency-control* section. C503, C504 or C507 might produce loss of locking if it had heat-sensitive leakage. C506, an electrolytic, might cause picture instability if open, or locking problems if leaky or shorted. Don't forget these are part of the oscillator circuit, also.

disable circuit defective? At B+ fuse F002, the voltage was higher than the required +123V, and the base voltage of Q801 was about +150V when +124V was called for. Evidently the excessive low-voltage supply was increasing the flyback pulse's amplitude, in turn triggering the disable circuit.

Ohmmeter tests of resistors, capacitors and diodes in the low-voltage power supply around Q801 soon located a shorted D802.

Diode D802 was replaced, but the horizontal hold still could not be locked. I removed the Q801 regulator transistor from its mounting to check the forward and reverse resistances with my VOM. There seemed to be base/emitter leakage in the 2SD692 Q801 transistor. The ECG substitution manual suggested an ECG243 as replacement for the 2SD692, which is a Darlington type. Because I didn't have an ECG243 in stock, I substituted an ECG284 NPN type with disappointing results. The picture showed a 60Hz weave, and the audio had hum. *Installation of the proper ECG243 cured the horizontal-hold problem.* Incidentally, the schematics show Q801 as a conventional bipolar type, but the one removed and the new replacement both were Darlington.

More problems

About a week later, the customer called me. The repaired receiver had stopped all operations except for a periodic loud thumping sound from the speaker.

Back at the shop, I found the voltage at B+ fuse F002 varying from 50V to 55V in step with the slow motorboating sound. When fuse F002 was removed, the voltage rose to about +120V. I removed the horizontal-output transistor (Q551) and checked it for leakage. There was no leakage, but I replaced it for a test anyway. The condition did not change.

Next, I scoped Q501 horizontal-driver transistor's base for horizontal pulses from IC401. Nothing but *hash* could be seen, even with maximum scope gain. The IC401 horizontal oscillator IC and Q801 regulator were replaced (for the second time), but the problems were unchanged.

Then I realized that the +123V supply (through R455) powers the horizontal and vertical oscillator sections of IC401, and because of the very low B+, the IC401 horizontal oscillator would not function. With the receiver power unplugged, I connected an external 12V supply to pin 13 and ground, and was rewarded with beautiful horizontal square waves at pin 12.

But now I'm confused. What is causing the low B+ voltage? Is it

leakage? The resistance of the B+ 12V supply as measured from the Q552 emitter to ground was about 380Ω. According to the schematic, the +12V source returns to ground through 680Ω R751 and a winding of T751, the pincushion transformer. Where is the additional load? I substituted +12V (from my modified old CRT checker) to the +12V source at Q552's emitter, but the voltage dropped to +8V.

Continued on page 57

... Over 3,000,000 Sold and Still The Best General Purpose Multimeter! ...



The Reason Is Clear...

Simpson 260[®] VOM
Has Features No Digital Can Match!



Latest 260[®] Series 7 \$124.00

- "Instant" null, peak, trend and continuity indications
- **High immunity** to transients, RF interference
- **dB measurement** capability at no extra cost
- **Resistance indication** from zero to infinity
- **Self-powered** voltage, current and dB ranges—no batteries to fail
- **Reliable, accurate performance** even under extreme environments
- **Easy, low-cost maintenance**—no expensive "chips" to fail
- **UL Listed** per UL-1244 Standard for Safety—Electrical and Electronic Measuring and Testing Instruments
- **Complete line** of UL recognized accessories
- **Options** include mirrored scale, extra overload protections, roll top carrying case

See the World Famous 260 Series 7, the 260-6XL, the 270 and the Pocket-Size 160[®] at Leading Electronics/Electrical Distributors

Simpson
INSTRUMENTS THAT STAY ACCURATE

SIMPSON ELECTRIC COMPANY

853 Dundee Avenue, Elgin, IL 60120
(312) 697-2260 • Telex 72-2416 • Cable SIMELCO
Canada: Bach-Simpson Ltd., London, Ontario
England: Bach-Simpson (U.K.) Ltd., Wadebridge, Cornwall

Circle (10) on Reply Card

Test your electronics knowledge

By Sam Wilson

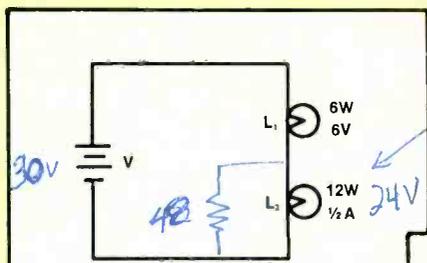


Figure 1.

$R = \frac{V^2}{P}$
 $= \frac{24^2}{12}$
 $R = 48$

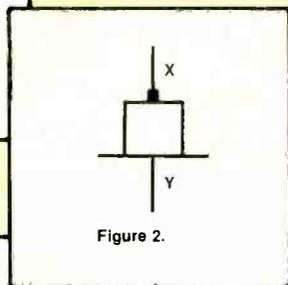


Figure 2.

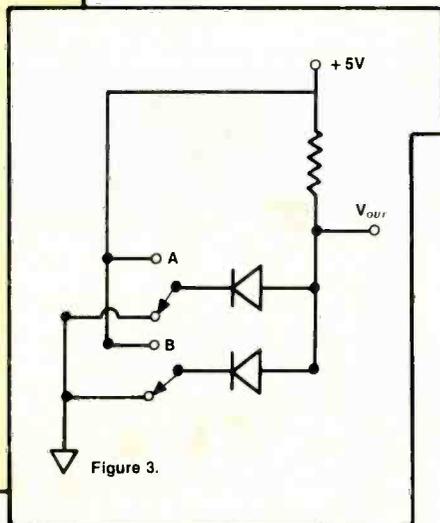


Figure 3.


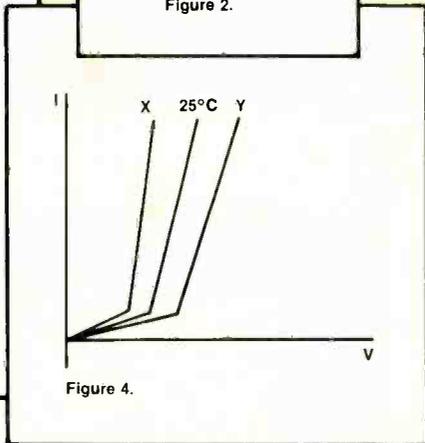



Figure 4.

- Show how you connect one resistor in the circuit of Figure 1 so that the rated current can flow through each filament. What is the resistance of the resistor?
- What battery voltage is required for the circuit of Figure 1?
- Which end of the diode in Figure 2 is the cathode?
 - The one marked X.
 - The one marked Y.
- Assume that +5V represents logic 1 and 0V represents logic 0. (Disregard any voltage drop across the diodes.) The circuit of Figure 3 operates as
 - an AND.
 - a NAND.
 - an OR.
 - a NOR.
- Which of the following is NOT a requirement for an operational amplifier?
 - Differential input
 - Zero volts input and output (with no signal)
 - Linear rolloff
 - A positive and negative (long-tail) power supply voltage
- Comparing 3-layer diodes and 4-layer diodes, which is unilateral?
 - 3-layer diode
 - 4-layer diode
- Which of the diode characteristic curves in Figure 4 is for temperature above 25°C?
 - The curve marked with an X.
 - The curve marked with a Y.
- Which of the circuits in Figure 5 is correct for a minimum loss pad?
 - The one shown in (a).
 - The one shown in (b).
- For the inverting operational amplifier of Figure 6, the value of R should be slightly over _____.
- The circuit of Figure 7 is
 - useless.
 - an inverting voltage amplifier.
 - a current-to-voltage converter.
 - a differentiating amplifier.

Answers are on page 61

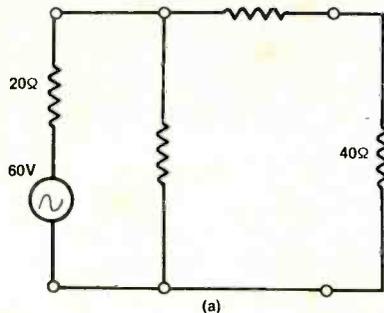

(a)

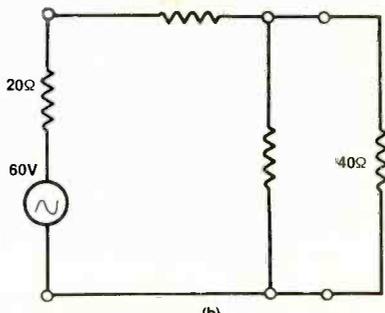

(b)

Figure 5.

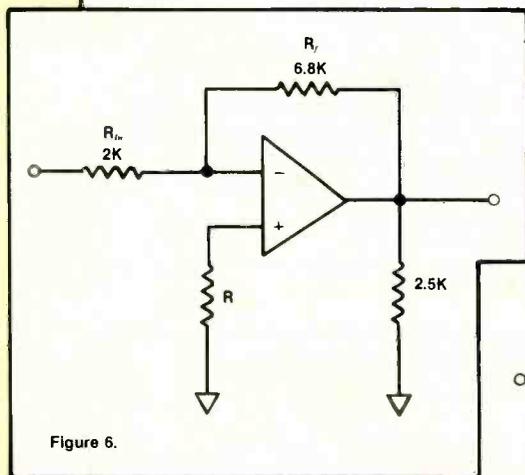


Figure 6.

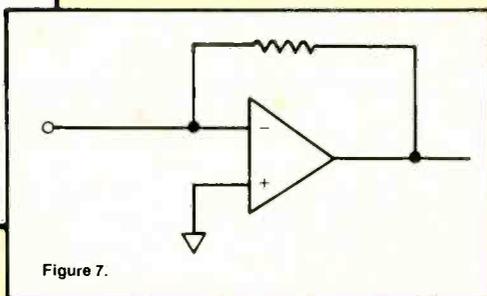


Figure 7.

TROUBLESHOOTING Horizontal ICs

By Homer L. Davidson

No vertical or horizontal locking

The picture on a Sharp 13D38 (Photofact 1934-2) was moving horizontally and vertically. It could not be locked with the vertical-hold control or the horizontal-hold control. I checked the dc voltages of all IC501 pins, comparing the readings against the schematic. Pin 10 (vertical hold) and pin 2 (horizontal hold) measured slightly less than called for by the schematic—not enough for concern.

Normal horizontal-sync pulses were scoped at pin 16. A 470 μ F 25V electrolytic capacitor was paralleled across the +11.9V supply because hash from poor filtering has been known to cause erratic sync in some previous repairs. The parallel capacitor did not change the unstable picture.

Finally, we replaced IC501 (with SK3921) and the problems were solved; both vertical and horizontal then could be locked correctly.

Circuit analysis—Figure 3 shows very little except those four voltages and waveforms that are so important for IC oscillator troubleshooting. Incoming horizontal sync at pin 16, +9.9V supply at pin 15 and horizontal near-square waves from pin 4 for the horizontal-driver transistor are all self explanatory. The sawteeth (ramps) needed for pin 1 are formed from flyback horizontal pulses by series resistance R602 and paralleling capacitor C601 (nearby components do not change the basic sawtooth shape).



Pin 2 obviously can be called the oscillator pin because it has the hold control. Not so obvious are the factors that determine the

PART 2

unlocked horizontal frequency. Capacitors and resistors make up an RC time constant. R608 plus R606 vs. C604 plus R607 form the basic time constant. However, there is one more important factor determining frequency: the dc voltage present. This is the element that is varied to accomplish locking; the dc voltage is varied in two ways. Variable voltage from R608 hold control is the most obvious. But there is another source not shown in Figure 3. In reality, R604 connects to R603 with fast and slow time constant filters between the junction and ground. If the horizontal attempts to drift, the correction voltage from pin 1 is filtered and applied to the oscillator pin 2 where it corrects the frequency. Pin 1 appears to be the only entrance for phase-comparison sawteeth, meanwhile doing double duty as exit for the dc error-correction voltage. The horizontal sync pulses entering at pin 16 comprise the other signal for the phase-comparison circuit.

The quality of C604, C607 and R606 must be excellent, especially regarding performance when heated. Substituting ordinary ceramics for C604 and C607 is almost certain to cause horizontal-frequency drift problems.

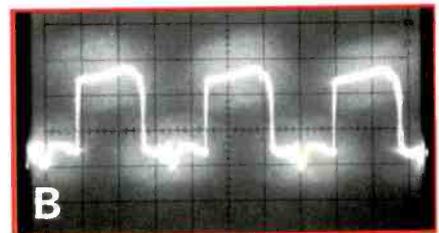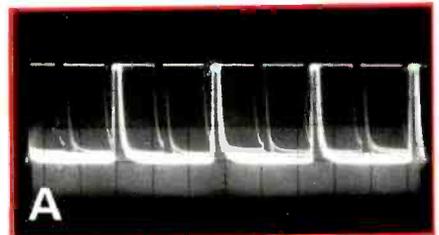This is Part 2 of a 2-part article. "Troubleshooting horizontal ICs" began in the February 1987 issue of *ES&T*.



These waveform photographs are typical of those found in many of the solid-state color TV receivers. (A) Horizontal sync pulses typically have faint lines in between the pulses. They are caused by interlaced scanning. (B) Horizontal pulses (almost square waves) at the IC output pin might have this appearance, although not all look the same. (C) This is the waveform from the IC vertical-output pin in one model. Again, not all receivers have the same waveform.

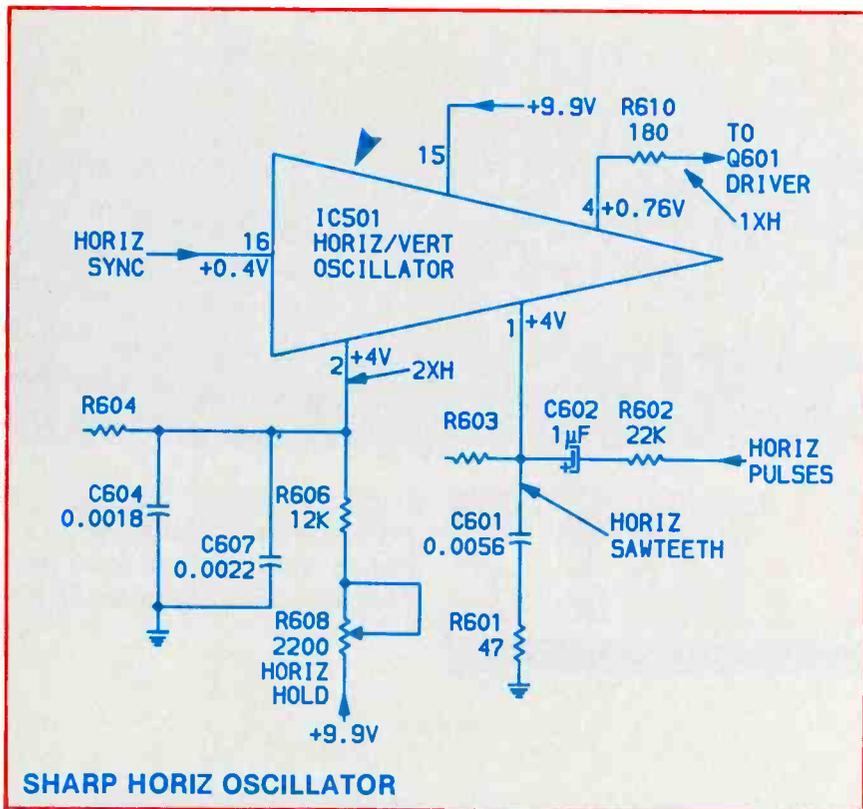


Figure 3. The horizontal oscillator of this Sharp 13D38 (Photofact 1934-2) is typical of many from Japan, except for details. The oscillator output, sync input, horizontal pulses and sawteeth input and the B+ supply are all identified. One thing is different from some: The oscillator operates at double horizontal (31,468H) and a single divider provides the essential 15,734Hz where the signal emerges at pin 4. Critical components here are C604, C607 and R606.

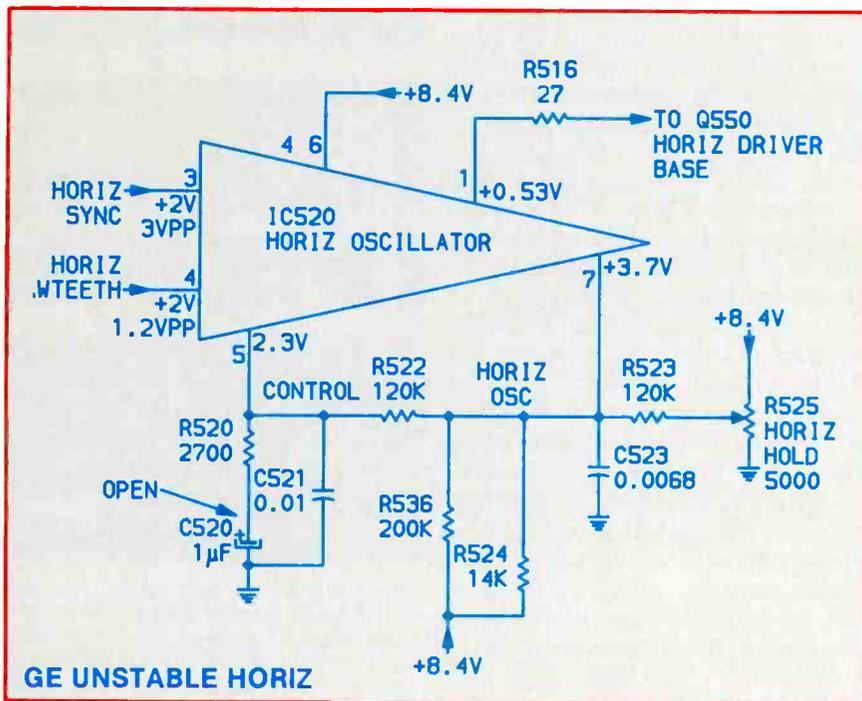


Figure 4. Again the three important waveforms and the B+ voltage are identified in the General Electric 10AA-A receiver (Photofact 1757-1). R524 (14K) and 0.0068μF C523 are critical for thermal drift in this model. Also, R523 and C520 can present problems at times. All are in the oscillator circuit, except C250 that is in the frequency-control circuit (where sync and sawteeth are compared). In this case, C520 was open and erratic.

One other thing about the circuit is unusual: IC501 has a divider internally, so the oscillator operates at 31,468Hz and the divider provides the required 15,734Hz for the driver transistor.

Erratic horizontal locking

After a General Electric 10AA9406 (Photofact 1757-1) was operated for a few minutes, the horizontal frequency would drift. Resetting the hold control restored the locking for a time. But after about half an hour the maximum horizontal-hold adjustment could not bring the picture into lock.

Because the oscillator pin 7 (Figure 4) changed only from +3.83V when locked to +3.88V when out-of-lock, we decided the IC might be at fault, and replaced IC520. Unfortunately, the performance was not improved. The next suspects with drift problems are resistors or capacitors that change from the heat of operation. And, of course, electrolytics cause more problems than do those that are wound in plastic. The only electrolytic in the oscillator circuit is the 1μF C520. When tested with a digital-readout capacitance meter, it showed only 0.07μF.

Replacing C520 with a good-quality 1μF capacitor stopped all the horizontal-frequency drifting and brought stability to the R525 horizontal-hold adjustments.

No sound or picture; one resistor hot

While testing dc voltages in a JC Penney 685-2069 color receiver, I measured +158V at the collector of the Q551 horizontal-output transistor and a complete loss of horizontal sweep. Scope waveforms showed no drive signal at the Q551 base.

When tests were made around horizontal-driver transistor Q502, the most obvious symptom was the smoking heat of 1,200Ω resistor R516 (Figure 5). Except for such rare problems as an errant solder splatter or a winding-to-core short in the driver transformer, the only component that can draw ex-

cessive current through R516 is Q502. Two defects involving Q502 can cause excessive collector current through R516. The transistor can be leaky, or Q502 might be getting too much positive base voltage from IC401 pin 1. The +2.5V collector voltage could indicate either.

However, when the Q502 base was grounded, R516 ran hot no longer, and the collector voltage was very high, indicating good transistor action without any serious collector leakage. The base ground was removed, and the tests moved to IC401. Pin 1 had no horizontal pulses. More important, pin 11 voltage checked only about +1V where +12V is normal. The resistance from pin 11 to ground was tested and the reading was very low. Pin 11 was unsoldered from the circuit board and checked again. Now it measured 87Ω to ground. There could be no question: IC401 was defective.

An IC401 HA11235 (obtained from JC Penney or Goldstar) was installed and *normal operation was restored*. To prevent a delayed failure, resistor R516 (that had been overloaded so much) was replaced and the receiver given a long heat run.

Intermittent raster

After a Sylvania with a E05-1 chassis (Photofact 1420-2) was operated for about two hours, the raster would collapse. I suspected some component was breaking down from heat. But the question was: which component?

An excellent first step in troubleshooting is to connect a dc voltmeter to the low-voltage B+ power supply and a scope to the horizontal-output pin of the oscillator IC. Then after the raster leaves, read the meter and observe the scope waveform and amplitude. Very often the changed voltage or waveform will indicate the problem area, or show where the next tests should be done.

There was one result from using that method with the Sylvania: the +24.5V supply source was lowered severely when the blackout

Exclusive, triple patented dynamic cap and coil analyzing . . . guaranteed to pinpoint your problem every time or your money back



with the all new LC75 "Z METER 2"
Capacitor Inductor Analyzer
Patented \$995

The "Z METER" is the only LC tester that enables you to test all capacitors and coils dynamically — plus, it's now faster, more accurate, and checks Equivalent Series Resistance (ESR) plus small wire high resistance coils.

Eliminate expensive part substitution and time-consuming shotgunning with patented tests that give you results you can trust every time. Test capacitor value, leakage, dielectric absorption, and ESR dynamically; with up to 600 volts applied for guaranteed 100% reliable results — it's exclusive — it's triple patented.

Save time and money with the only 100% reliable, in- or out-of-circuit inductor tester available. Dynamically test inductors for value, shorts, and opens, automatically under "dynamic" circuit conditions.

Reduce costly parts inventory with patented tests you can trust. No more need to stock a large inventory of caps, coils, flybacks, and IHVTs. The "Z METER" eliminates time-consuming and expensive parts substituting with 100% reliable LC analyzing.

Turn chaos into cash by quickly locating transmission line distance to opens and shorts to within feet, in any transmission line.

Test troublesome SCRs & TRIACs easily and automatically without investing in an expensive second tester. The patented "Z METER 2" even tests SCRs, TRIACs, and High-Voltage Diodes dynamically with up to 600 volts applied by adding the new SCR250 SCR and TRIAC Test Accessory for only \$148 or FREE OF CHARGE on Kick Off promotion.

To try the world's only Dynamic LC Tester for yourself, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

SENCORE

3200 Sencore Drive
Sioux Falls, SD 57107
605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

Circle (14) on Reply Card

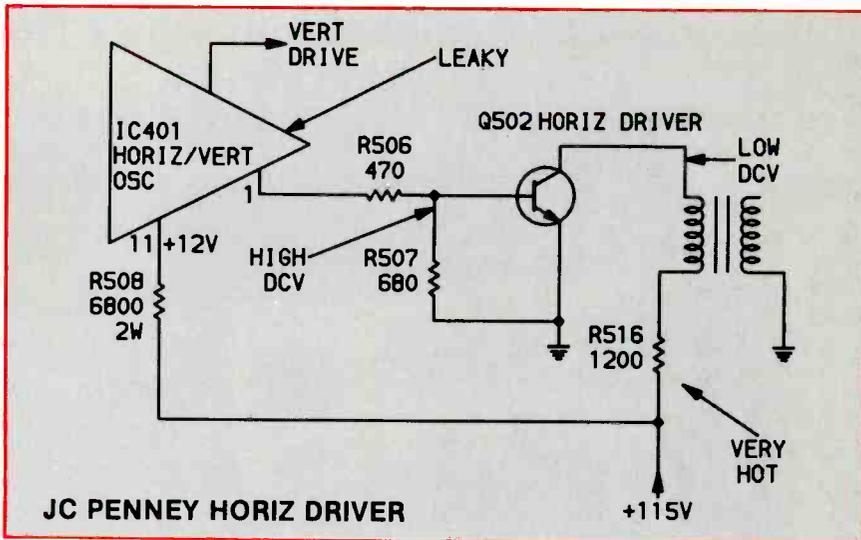


Figure 5. With model 685-2069 JC Penney television (Photofact 2239-1), the burning heat of R516 was the most prominent symptom. Q502's collector voltage was almost zero (which accounted for the R516 heat), although its base voltage was too positive, as was IC401 pin 1. However, pin 11 measured a very low resistance to ground. Therefore, IC401 was replaced. Horizontal deflection and HV were restored.

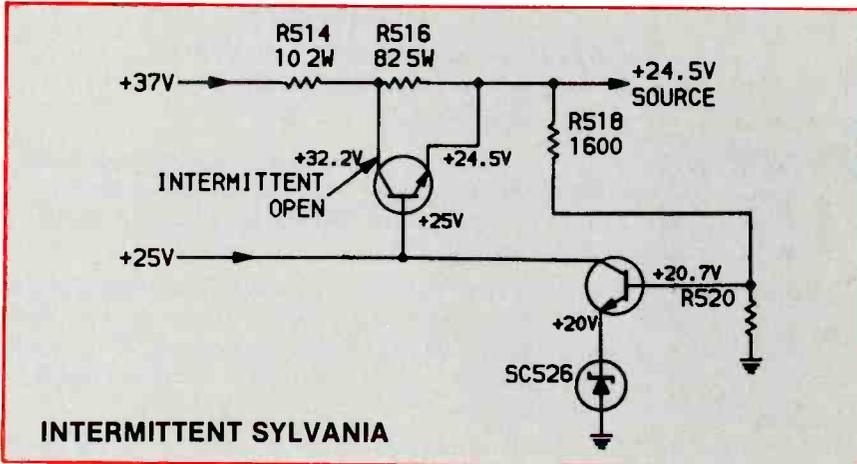


Figure 6. After the EO5-1 chassis Sylvania (Photofact 1420-2) was operated for two hours or more, the raster would disappear. After electronic, visual and mechanical tests, the problem was discovered to be a bad joint at the collector terminal of regulator transistor Q502.

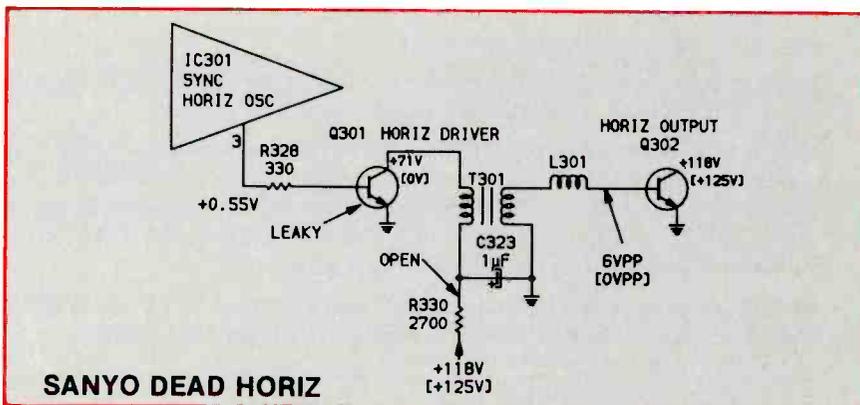


Figure 7. Schematic dc voltages in Sanyo chassis 91C610 (Photofact 2170-1) are shown in the usual way, but the voltages actually measured are shown in brackets. And the dc voltages at R330 input and the Q301 collector indicate that R330 is open. R330 had all the appearances of being too hot, so Q301 must have had excessive collector current. Q301 was tested and found to have high leakage. Replacement of Q301 and R330 brought normal operation; the IC301 pin 3 signal also was normal.

occurred. That clue led to a more detailed examination of the complete low-voltage supply. By moving the circuit board downward, the blackout occurred more often. A combined mechanical and visual series of tests finally located a bad soldered connection at the collector terminal of regulator transistor Q502 (Figure 6).

Removal of the old solder and application of new solder (being certain all areas were tinned properly) stopped the intermittent loss of raster.

No raster — no sound

Many technicians say a dead receiver is easier to repair than an intermittent one. Certainly that was true of the previous intermittent Sylvania vs. the next case, a model 91C610 Sanyo (A2V-61000 chassis in Photofact 2170-1). Nothing worked on the Sanyo. At the Q302 horizontal-output, the collector was measured about +125V without pulses instead of +118V with pulses. Q302 also had no base signal. Pin 3 of IC301 (Figure 7) had a very low amplitude signal when scoped. But most important, zero voltage was measured at the collector of Q301 horizontal-driver transistor, although about +125Vdc was at the other end of resistor R330 where +118V is normal. Of course, R330 was open and Q301 tested very leaky, which, with the usual +70V applied to it, would probably have become a dead short. The excessive transistor current ruined R330.

Q301 was replaced by a universal ECG399, and a new 2,700Ω R330 was installed, bringing normal operation.

Problems! Problems! Problems!

After a leaky Q100 horizontal-output transistor was replaced in an RCA CTC99E chassis (Photofact 1895-1), we heard a continuous arcing sound in the flyback transformer (Figure 8). Immediately, the circuit went into shutdown. After the ac power was off, we found that the new Q100 was leaky and ruined.

Analyze defective waveforms faster, more accurately, and more confidently — every time or your money back

It was obvious now that the receiver must be operated on reduced line voltage until the problems are solved.

The defective T102 flyback output transformer was replaced with a 154493, and another Q100 part number 146823 output transistor was installed. Resistors 1.2Ω R104 and 0.18Ω R109 showed signs of overheating, and they were replaced also.

A variable-voltage transformer was connected to supply the receiver's ac, and operation was started at about 40Vac with slow increases to about 80Vac without any indication of overload or high voltage. Remember, the CRT heaters are operated from the flyback, so even if a television does operate at low line voltage it is difficult to see a picture.

With an ac input of 80Vac, the Q100 collector voltage was about +140V. This indicated either a total lack of Q100 drive signal or a shorted SCR regulator that had forced the horizontal into shut-down. SCR100 was checked and replaced but those conditions did not change. Evidently the main problem was the loss of Q100 drive.

Then I remembered that the RCA CTC99 has a pulse-type of start-up. That brought another important thought to mind: An inductance in series with the 120Vac line can reduce the amplitude of the starting rush of current and cause intermittent start-up in some receivers that have pulsed-B+ start-up. And a variable-voltage transformer for obtaining any line voltage between zero and 120Vac certainly has considerable inductance when adjusted to about half rotation. Also, the C106 charging current is lower when the line voltage is reduced, and that contributes to the start-up failures.

Therefore, start-up usually will not occur when the receiver has line voltage lower than about 90Vac.

However, there is a solution. With proper precautions and an external power supply, the CTC99



with the SC61 Waveform Analyzer
Patented \$2,995

If you value your precious time, you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you. 10 times faster, 10 times more accurate, with zero chance of error.

End frustrating fiddling with confusing controls. Exclusive ultra solid ECL balanced noise cancelling sync amplifiers, simplified controls, and bright blue dual trace CRT help you measure signals to 100 MHz easier than ever.

Accurately and confidently measure waveforms from a tiny 5 mV all the way to a whopping 3,000 V without hesitation with patented 3,000 VPP input protection — eliminates expensive "front end" repairs and costly equipment downtime.

Make only one circuit connection and push one button for each circuit parameter test: You can instantly read out DC volts, peak-to-peak volts and frequency 100% automatically with digital speed and accuracy. It's a real troubleshooting confidence builder.

Confidently analyze complex waveforms fast and easily. Exclusive Delta measurements let you intensify any waveform portion. Analyze glitches, interference signals, rise or fall times or voltage equivalents between levels; direct in frequency or microseconds.

Speed your digital logic circuit testing. Analyzing troublesome divide and multiply stages is quicker and error free — no time-consuming graticule counting or calculations. Simply connect one test lead to any test point, push a button, for test of your choice, for ERROR FREE results.

To see what the SC61 can do for your troubleshooting personal productivity and analyzing confidence, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

SENCORE

3200 Sencore Drive
Sioux Falls, SD 57107
605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

Circle (15) on Reply Card

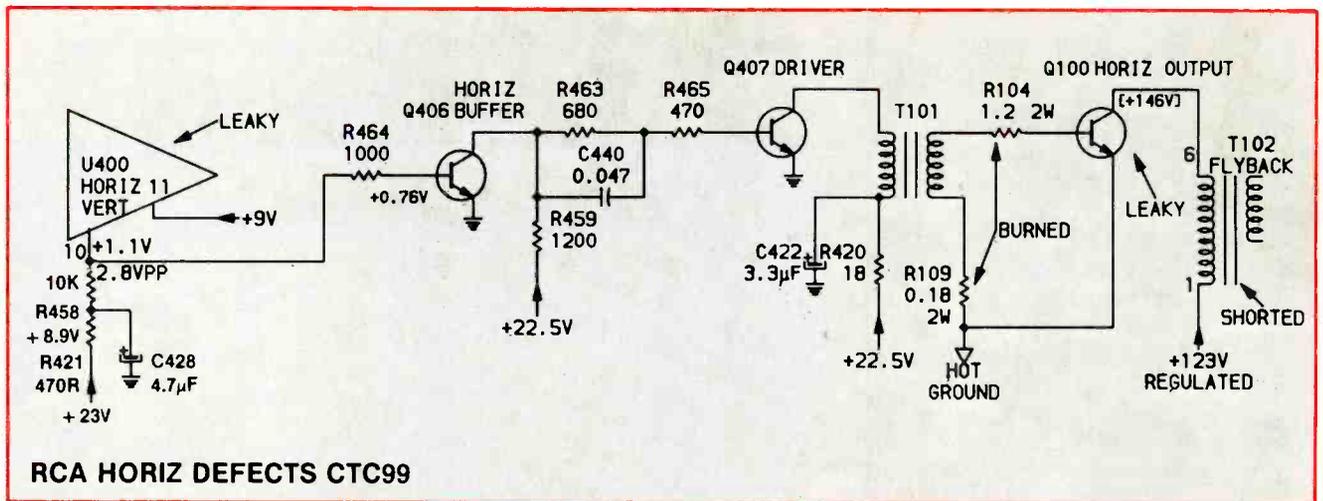


Figure 8. Only the last four horizontal-deflection stages are shown here in simplified form for the RCA CTC99 (Photofact 1895-1). Notice the *hot* and *cold* grounds. For some tests, both can be connected together. But be careful; *all grounds are hot* and become a shock and damage hazard when you try to connect test equipment (that has the third-wire ground) to *any* receiver ground. Sparks probably will fly. Use an isolation transformer on the CTC99. All details of this repair are given in the text plus an 8-point method of using an external voltage supply for the oscillator so the remainder of the chassis can be operated at about 35Vac when a higher voltage would cause damage to transistors or other components.

horizontal system can be made to operate with low power when the line voltage is reduced to only about 35Vac. This ability is particularly valuable in a receiver that does not produce HV or pass all of the sequential waveform tests (to be described) because the horizontal-sweep system has serious defects that could cause extensive and expensive damage if operated at 120Vac.

Operating an RCA CTC99 from lower line voltage must be done carefully. These are the steps I use:

1. With ac plug removed, connect the rear chassis rail (cold ground) to the C106 negative terminal (hot ground). Operate the receiver from an isolation transformer to prevent shocks and shorts.
2. Connect a regulated 200mA, +20V external power supply to TP-13 and cold ground. TP-13 also is at the CR422 cathode and the CR421 anode. Voltages down to about +9V work, but not so well. A +16V to +21V range of steady voltage is satisfactory. Higher voltages produce better waveforms.
3. Adjust the variable-voltage transformer (variac) for about 30Vac, and then fine-tune the line voltage by adjusting for +40V across C106 (near Q100).
4. Apply dc and ac power to the receiver, then turn on the receiver. It is not necessary to disable the

SCR regulator.

5. Check the waveform and frequency (repetition rate) of the oscillator at pin 12. Expect almost-sawteeth of about 31,468Hz frequency at about 2Vp-p amplitude. Look for near-square waves at the Q407 collector (metal mounting tab) at about 80Vp-p and 15,734Hz. Finally, the Q100 output-transistor collector should have flyback pulses of perhaps 350Vp-p to 400Vp-p. These pulses should be normal in appearance.
6. Examine the Q100 collector pulses for incorrect waveshapes. Look for narrow ringing on the pulses or an extra-wide pulse midway or so between the normal pulses. The ringing on pulses and a high peak-to-peak reading might indicate an open C117. Broad extra pulses between the normal ones indicate a heavy load on the flyback.
7. If the waveforms stop in the center of the horizontal path, the problem is likely to be in the next one following the last stage having a correct waveform. Perform the usual tests, particularly the B+ voltages and the various signals, keeping in mind that only the oscillator, buffer, driver and output stages have voltage. The IF, chroma, video, sound, sync and all the rest are without B+. When repairs and replacements have provided normal clean 380Vp-p 15,734Hz flyback pulses at the

Q100 collector, without sharp ringing or extra pulses, it is safe to unplug the ac power cable and remove the jumper wire between cold and hot grounds. Also, disconnect the external dc-voltage supply.

8. While watching the horizontal section, apply normal 120Vac to the receiver. If all defects have been found and all repairs properly made, the receiver should work normally. Finally, test the safety shutdown operation by connecting XT to XT1. The receiver should go into shutdown. If it doesn't, you must repair the X-ray latch and detector circuits.

When first turned *on* with the 120Vac power, if the receiver operates but not correctly, it is necessary to do more troubleshooting. But do not connect the external jump-start power supply unless necessary to substitute for a start-up circuit that is not working at all, or (as detailed previously), to permit operation of the Q100 stage with very-low dc voltage.

Meanwhile, at the CTC99— When the 8-step testing sequence was applied to the CTC99, all went well until step 5. No 31,468Hz sawteeth were scoped at pin 12 and no 15,734Hz square waves for the buffer were scoped at pin 10. Several more tests indicated U400 was defective, therefore, we replaced the U400 oscillator/count-

Now test and restore every CRT on the market . . . without ever buying another adaptor socket or coming up embarrassingly short in front of your customer . . . or your money back

down IC with a part number 145803. Afterward, strong horizontal-drive broad pulses came from pin 10 to Q406 base. Sufficient amplitude horizontal pulses without ringing or other smaller pulses were scoped at Q100's collector, so we assumed the receiver was ready for higher voltage. Q100's collector at that time measured +40V.

The external dcV supply was removed and the line voltage increased to 90Vac for a trial run. Sound and picture started just as they should. When the line voltage was increased to the rated 120Vac, performance was excellent. When terminals XT and XT1 were shorted together, the receiver instantly went into shutdown, as it should. Reset of shutdown for full operation occurs when the receiver is turned *off* for a short time (or longer) and then switched back *on*. The reason for the short delay is that C106 must completely discharge before its next charging current can supply sufficient voltage for dependable start-up operation.

Some of the components mentioned here are not part of Figure 8, but can be found in Photofact 1895-1. For example, C106 is the large metal-can filter capacitor mounted vertically near the horizontal-output transistor. We suggest you use the Photofact during troubleshooting, along with the 8-step sequence.

Finally, the CTC99 operated correctly, and I breathed a sigh of relief. Few color receivers require so much intricate testing and such an unusual number of replacement components. Therefore, I operated it for several extra hours on the time-test bench before delivery.

Comments

Although these are genuine case histories, they were chosen primarily for the opportunities they offered for discussing general troubleshooting methods. We sincerely hope this approach has been helpful to our technician readers.



with the new improved CR70 "BEAM BUILDER"™
Universal CRT Tester and Restorer
Patented \$995

Have you ever?

Thrown away a good TV CRT, data display CRT, or scope CRT that could have been used for another two or three years because you had no way to test or restore it?

Lost valuable customers because you advised them that they needed a new CRT when another technician came along and restored the CRT for them?

Lost the profitable extra \$35 or more that you could have gotten for restoring a CRT while on the job and locked in the profitable CRT sale later?

Avoided handling profitable trade-ins or rentals because you were afraid you'd have to replace the picture tube when you could have restored it?

Had a real need to test a CRT on the job, but didn't have the right adaptor socket or setup information in your setup book?

If any of these things have happened to you, **CALL TODAY, WATS FREE, 1-800-843-3338**, for a **FREE 15 day Self Demo**.

"BEAM BUILDER" is a trademark of Sencore, Inc.



Call Today Wats Free 1-800-843-3338

SENCORE

3200 Sencore Drive

Sioux Falls, SD 57107

605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

Circle (16) on Reply Card

What do you know about electronics?

Infrared Remote Controls

By Sam Wilson

To avoid the possibility of duplication of information between this column and Audio Corner, which has recently been discussing digital audio, I will now leave the subject of compact discs in Kirk Vistain's capable hands and proceed with other subjects.

In this issue, I will discuss some of the basic components and circuits used in infrared remote controls.

Infrared remote controls

I wish to thank the Fisher Corporation for much of the information that follows.

I have been informed that wired remote controls still are being used for air conditioners and VTRs, but those units will soon be using infrared remote controls.

Ultrasonic remote units require

a tuned circuit for each function. This limits the number of functions that can be included in their design. Too many functions result in an overweight and oversized unit.

Another problem with the ultrasonic controls is that they can be fooled by jangling keys and other high-pitched noises.

Infrared remote controls are the logical answer to the problems of the other types. They are portable and lightweight. They use coded signals that cannot be fooled by other infrared sources (such as a hot fireplace).

The wavelength of the most efficient infrared diodes is 940nm. (A nanometer is 10^{-9} meter.) Figure 1 shows the relationship between various wavelengths and the optimum infrared frequency for remote controls.

Figure 2 shows a simplified block diagram of the remote control system.

The viewer's hand-held transmitter is battery operated. This requires special attention because of the high current demanded by the infrared LED.

A pulse modulator is used to chop the LED current (and light output) into pulse combinations that represent binary digits. A different code is used for each function controlled.

The PIN diode in the receiver converts the received infrared pulses into electric impulses. These pulses are amplified and shaped before being decoded.

Depending upon the code received, the output of the decoder circuitry controls the appropriate function in the receiver.

The infrared LED

The infrared LED works like any ordinary LED. You will remember from a previous article that the energy level of electrons can be raised or lowered. One way to do this is to supply an electric field that attracts the electrons.

In the case of the LED, the applied electric field is used to get the electrons across the junction. This is illustrated in Figure 3. The positive field supplies enough energy to electrons to get them across the depletion region.

After the electron gets across the junction depletion region, it

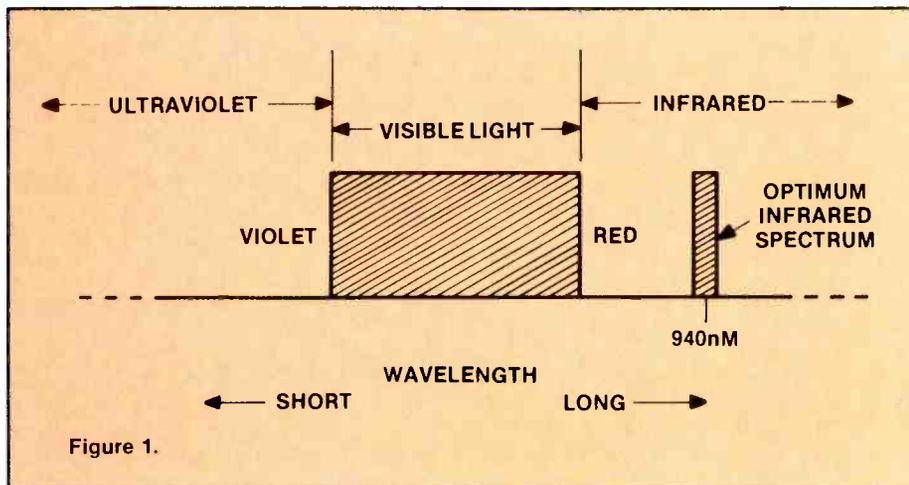


Figure 1.

Walk "tough dog" troubles out of any TV & VCR in half the time . . . or your money back



with the exclusive, patented,
VA62 Universal Video Analyzer . . . \$3,295

Would you like to?

Reduce analyzing time: Isolate any problem to one stage in any TV or VCR in minutes, without breaking a circuit connection, using the tried and proven signal substitution method of troubleshooting?

Cut costly callbacks and increase customer referrals by completely performance testing TVs & VCRs before they leave your shop? Own the only analyzer that equips you to check all standard and cable channels with digital accuracy? Check complete, RF, IF, video and chroma response of any chassis in minutes without taking the back off the receiver or removing chassis plus set traps dynamically right on CRT too? Simplify alignment with exclusive multiburst pattern?

Reduce costly inventory from stocking yokes, flybacks, and other coils and transformers, for substitution only, with the patented Ringing Test. Run dynamic proof positive test on any yoke, flyback, and integrated high voltage transformer . . . in- or out-of-circuit?

Protect your future by servicing VCRs for your customers before they go to your competition? Walk out "tough dog" troubles in any VCR chrominance or luminance circuit — stage-by-stage — to isolate problems in minutes? Have proof positive test of the video record/play heads before you replace the entire mechanism?

Increase your business by meeting all TV and VCR manufacturers' requirements for profitable warranty service work with this one universally recommended analyzer?

To prove it to yourself, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE Self Demo . . . or learn how the VA62 works first by calling for your free simplified operation and application instruction guide, worth \$10.00.



Call Today Wats Free 1-800-843-3338

SENCORE

3200 Sencore Drive

Sioux Falls, SD 57107

605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

Circle (17) on Reply Card

April 1987 *Electronic Servicing & Technology* 51

gives up the extra energy in the form of light energy. That light is delivered to the outside world through a very small window.

The thing that makes the infrared diode different from other LEDs is the type of materials used for its construction. Ordinarily, an infrared diode requires between 300mA and 500mA for a continuous emission. That would seriously limit the battery life of the remote control. However, in this application the LED is pulsed so that the current drain is less than 10% of the continuous emission value. This gives a very satisfactory battery life.

The result is a sufficiently average light power (about 5mW) to operate the receiver from a distance of 7M to 10M.

The pin diode

At the receiver, the received signal produces a signal of about $50\mu\text{Vp-p}$.

The receiver PIN diode gets its name from the fact that it is made with P-type material, Intrinsic material and N-type material. The intrinsic material is a very lightly doped section between the N and P materials.

To understand the PIN diode operation, refer to the model shown in Figure 4. Observe that the diode is reverse biased. Ordinarily, this would mean that no current is flowing. This is especially true because of the intrinsic layer

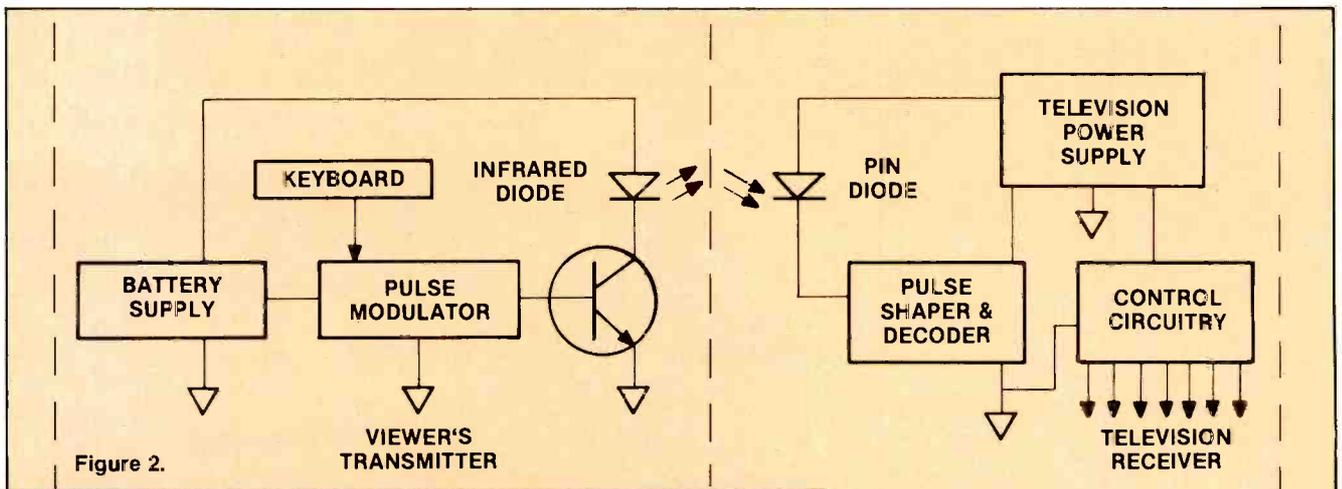


Figure 2.

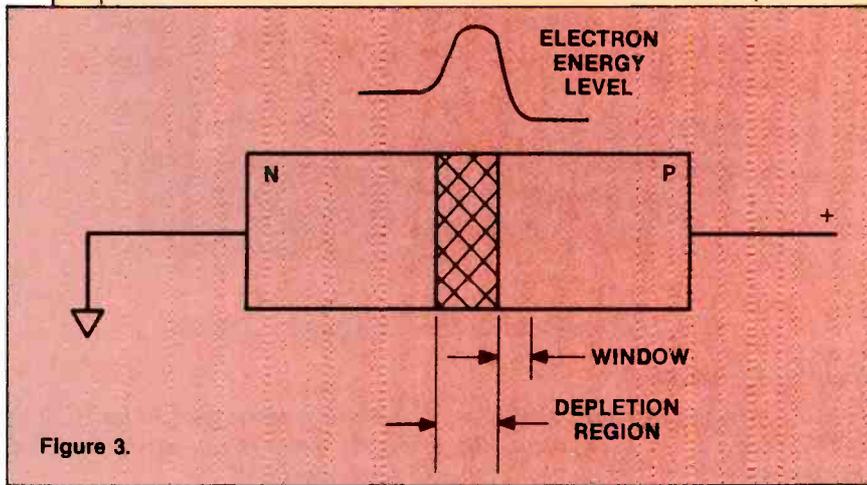


Figure 3.

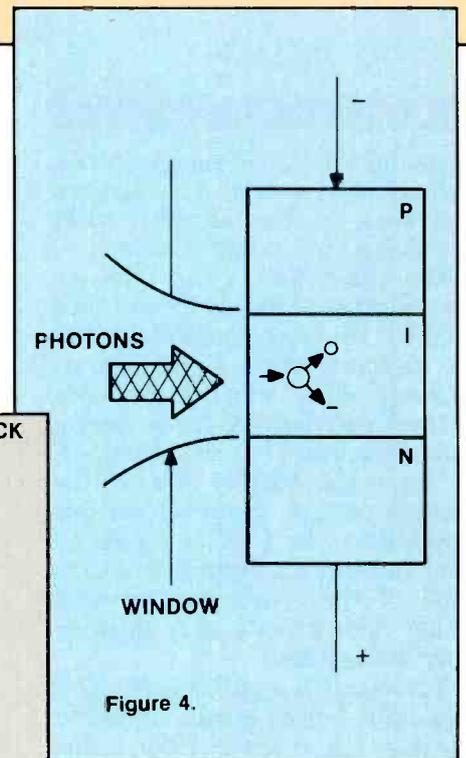


Figure 4.

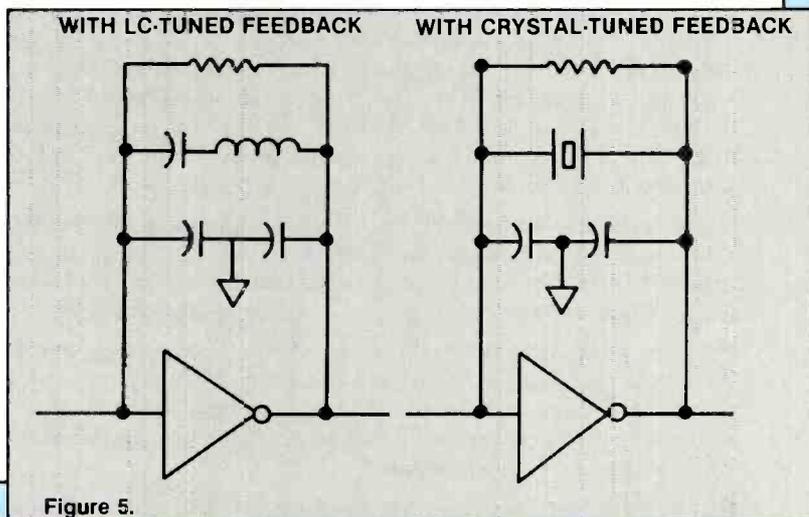


Figure 5.

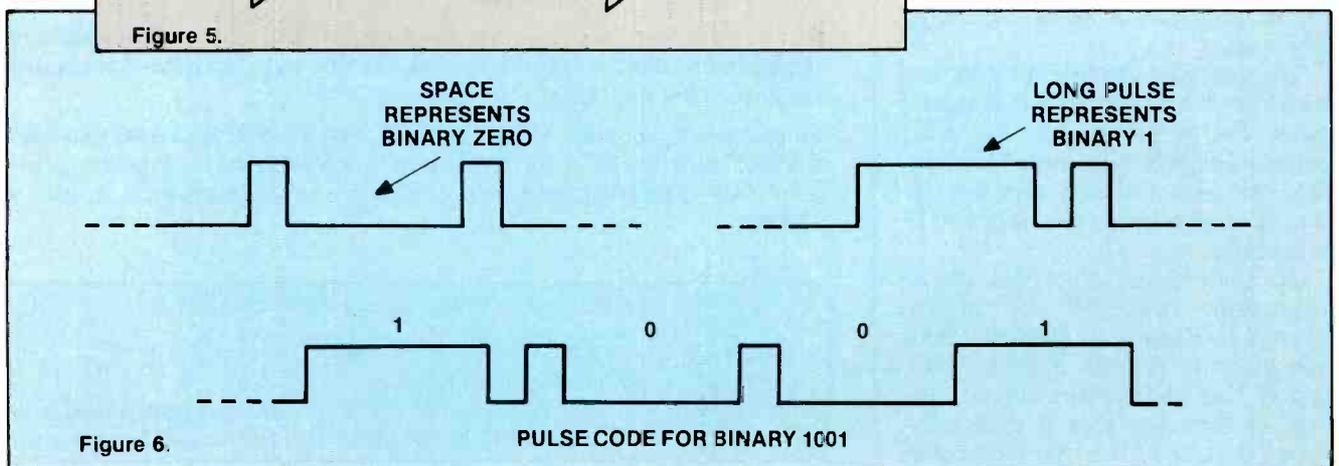


Figure 6.

PULSE CODE FOR BINARY 1001

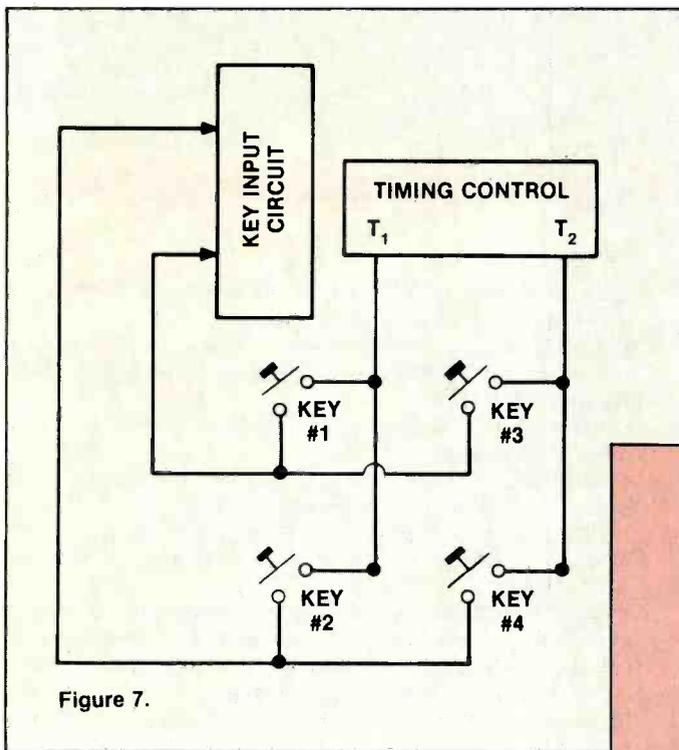


Figure 7.

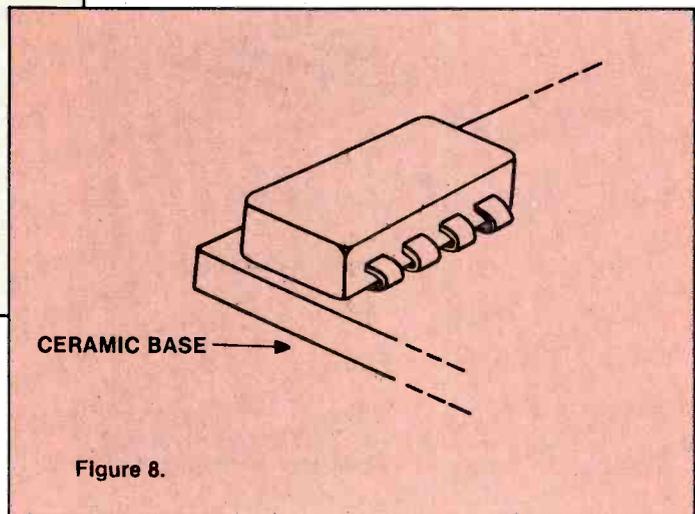


Figure 8.

that is much like an insulator.

When the infrared light strikes the intrinsic layer, the photons strike the atoms and release electron-hole pairs. This converts the intrinsic layer into a conductor, and reverse current flows through the diode.

PIN diodes have other applications in microwave systems, but the action just described explains how they work as infrared sensors.

The oscillator

An oscillator is used in the transmitter. It is needed for pulsing the infrared LED, and also for providing pulses to the modulator.

The oscillator can be made with an inverter as shown in Figure 5. A common cathode, emitter or source amplifier has an output that is 180° out of phase with the input. So, any of those amplifiers can be used as an inverter.

The simplest inverter oscillator is made with an inverter as shown in Figure 5. As with all oscillators, it is an amplifier with tuned regenerative feedback. The tuned circuit may be either an L-C type or a crystal.

An example of a pulse code

There are many different ways to use pulses for representing the binary numbers 1 and 0. The method shown here is for the Fisher REM-885.

As shown in Figure 6, a wide space represents logic 0, and a wide pulse represents logic 1.

In this unit there are two ways to send signals. A *single-burst signal* contains only two cycles of coded information and then stops. An application might be using the remote to turn the controlled system *on* and *off*. You wouldn't want the system to turn *on* and *off* repeatedly, so, a single burst signal would be used.

A *hold signal* repeats the coded transmission over and over—as long as the key is depressed. That would be useful for increasing or decreasing the sound volume of the controlled system. You continue to depress the volume key (using the *up* or *down* position) until the sound is at the desired level.

The keys on the remote unit determine whether the transmitter output is a single-burst or a hold signal. Figure 7 shows how this is done for four keys.

Keys 1 and 2 complete the pulse control circuit to T₁. That is a single-burst connection.

Keys 3 and 4 complete the pulse control circuit to T₂. That is a continuous output (hold) connection.

In the next issue, I will continue the discussion of infrared remote controls.

More on surface mounts

You can learn a lot by studying how manufacturers of surface-mount circuits work with their products.

Figure 8 shows a surface-mount component mounted on a ceramic base. To solder the component in place, first attach it to the ceramic with a paste. The complete unit then is heated to the point where the paste turns to melted solder. Cooling is the final step.

To remove the component, the board again is heated to a temperature just below the melting point of the solder. Then, a hot air stream is directed to a point directly below the component to be removed.

The additional heat melts the solder making it easy to remove the component.



Azimuth recording: the way to eliminate crosstalk between VCR video tracks


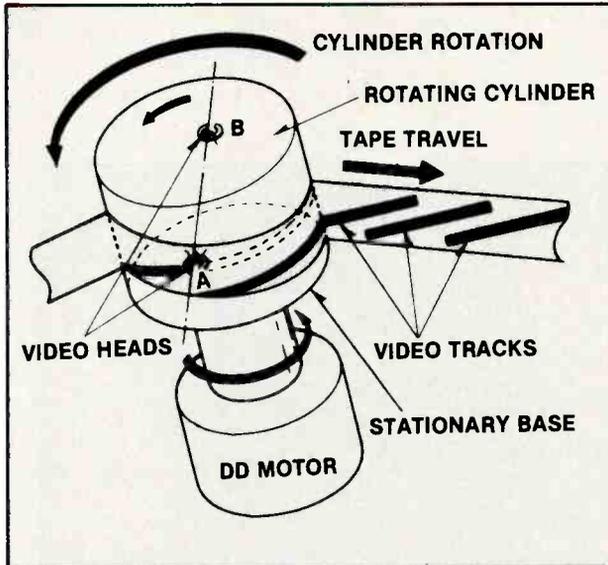


Figure 1. The video heads of a VHS VCR are moved across the tape, while the tape is moved past the head cylinder.

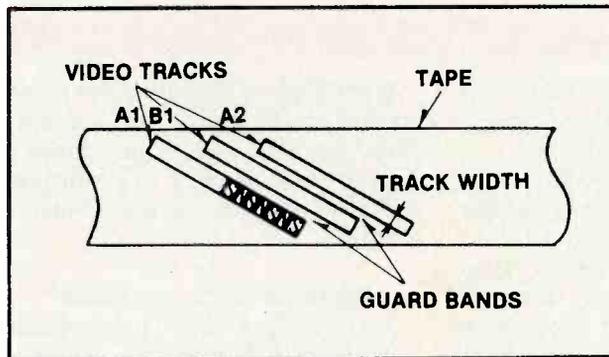

The designers of VHS VCRs for use in the home were faced with a nice set of requirements:

- First of all, of course, a home VCR had to have picture and sound quality at least as good as, if not better than, broadcast television.
- It had to be small enough to fit into the average living room unobtrusively.
- It had to be capable of playing back a tape that was long enough to hold an average-length movie.

This, of course, is far from a complete set of requirements, but it gives an idea of what the designers were up against.

One consequence of the size requirement was reduction of the size of the head cylinder compared to those found in existing professional and broadcast video recorders. And, in order to pack enough program material onto a reasonably sized cassette tape, it was necessary to make the recorded tracks narrow and close together. All of these things taken together resulted in a VCR with extremely small heads, having narrow gaps (0.3×10^{-6} meters). That's three-tenths of a micron or 12 millionths of an inch. Just by way of comparison, a typical human hair is three thousandths of an inch thick or about 250 times the dimension of a VHS VCR head gap.

Even though the recorded tracks are narrow, when you're recording in SLP mode the tracks are not just close together, they're overlapping slightly. If some steps were not taken to avoid it, the crosstalk would be crosstalk—that is each frame of the TV picture would contain some of the information from the previous frame and from the next frame. This crosstalk is avoided by using a technique called azimuth recording.

The term *azimuth* can be traced back to its Arabic and

Figure 2. Because of the heads' motion relative to the tape motion, the video tracks are laid down on the tape as a series of slanted bands with unrecorded areas (guard bands) in between. In SLP mode, because the tape moves slowly past the heads, the guard bands disappear; the video tracks overlap.


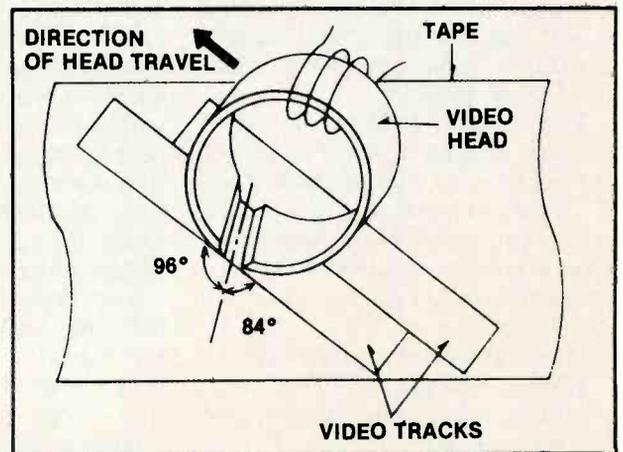


Figure 3. In azimuth recording, the video heads are set at an angle of 12° relative to each other (one head is at $+6^\circ$ to the perpendicular, one is at -6° to the perpendicular). With this system, even though alternate tracks overlap, there is no crosstalk.

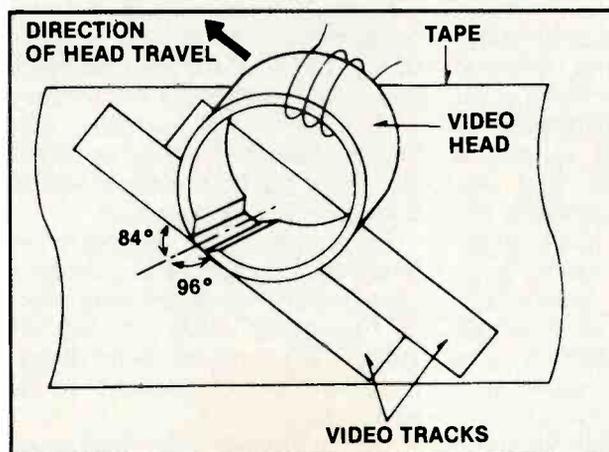

The term *azimuth* can be traced back to its Arabic and Latin origins in words meaning, more or less, "the way."

Latin origins in words meaning, more or less, "the way." In ordinary speech it means an angular distance from a fixed point, usually due south. The term was borrowed by audio engineers to describe the angular deviation of an audiotape recorder head gap from the perpendicular, that is, any deviation from a right angle to the direction of tape motion. That usage of the word azimuth has been extended to video heads.

If a recorded track is laid down with the head at one azimuth angle and played with the head at another azimuth angle, the reproduced signal is attenuated. Depending upon the magnitude of the angle, the frequency of the recording and other considerations, the signal will be attenuated to a greater or lesser degree.

This characteristic is used to advantage in VHS VCRs by installing one video head at an azimuth of +6° and the other video head at -6°. By doing this, alternate tracks are recorded at an angle of -12° to each other. Therefore, in the SLP mode, even though the head that is actively

playing back a track also is traveling across the portions of the two adjacent tracks that overlap it, little signal is generated by the overlapping tracks because they are at the wrong azimuth angle.

This article is adapted from, and the illustrations taken from, the GE Videocassette Recorder Service Manual for the model 1CVP2020X VHS VCR.

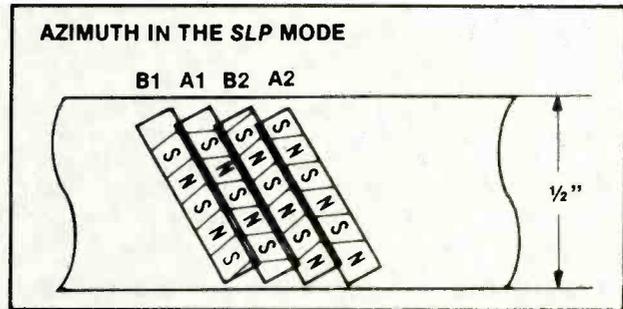


Figure 4. This representation of the video tracks in SLP mode shows the overlap of the tracks. Note, however, that the alternating north and south magnetic poles are at an angle to those of alternate tracks. This is the result of azimuth recording, and eliminates crosstalk from track to track.

TEST INSTRUMENTS High Quality Lowest Prices Off-The-Shelf

New! **MINI-METERS w/MAXI-SPECS**

SCOPE 3 1/2 Digit LCD with 8 Full Functions

Model DVM-632 \$4495

Deluxe test leads included • 0.5% accuracy • Transistor gain test • Audible continuity checking & diode test • 10 Amp measurement

SCOPE 3 1/2 Digit LCD Multimeter

Model DVM-630 \$2995

Test leads included • 0.5% accuracy • 6 functions, 19 ranges • Automatic zero adjust • Low battery indication • Measures 5" x 2 3/4" x 7 1/8"

B & K 20 MHz Dual Trace

Model 2120 \$37995

Probes included • 20 and 26 MHz band widths • TV V and TVH • X-Y operation • Trace rotation: adjustable front panel • Channel 1 output

SCOPE 3 1/2 Digit Capacitance

Model DCM-602 \$6995

Test leads included • 8 ranges with full scale values to 2000 uF • LSI circuit • Crystal time base • Frequency range 800 Hz to 8 Hz

SCOPE 3 1/2 Digital Multimeters

Model DVM-638 \$7995

Test leads included • 11 function, 38 ranges • Logic level detector • Audible visual continuity • capacitance and conductance measurement.

Model DVM-634 \$4875 **Model DVM-636 \$6275**

- 7 function, 32 ranges
- Transistor measurement
- 8 function, 37 ranges
- Capacitance measurement

SCOPE Pocket Sized Audio Signal Generator

Model RC-555 \$6995

Test leads & 9V battery included • Low distortion sine-wave signal • 46 step selected frequency • x1 range 20 Hz to 1.5 KHz/x100 range 2KHz to 150 KHz

HITACHI 35 MHz Dual Trace Oscilloscope

Model V-355 \$59995

(Reg. \$899.95)

Probes included • Thin, lightweight, compact • Large 6" rectangular, internal graticule CRT • Autofocus

FORDHAM Sweep Function Generator

Model FG-801 \$21995

(Reg. \$289.95)

Test leads included • 7 frequency ranges, 0.2 Hz to 2 MHz • Accuracy to ±5%

FORDHAM 550 MHz Frequency Counter

Model FM-8 \$16995

(Reg. \$249.95)

Completely assembled, pre-tested, precalibrated • High intensity 8-digit LED display

New! **SCOPE 4 1/2 Digit LCD Bench Digital Multimeter**

Model DVM-6005 \$19995

Test lead set & 6 "D" size batteries included • 0.4" high characters • Conversion period: 500 milliseconds • Automatic, negative polarity

Phone orders accepted.

Fordham TOLL FREE **800-645-9518**
 260 Motor Parkway, Hauppauge, NY 11788
 In New York State 800-832-1446

Service & Shipping Charge Schedule Continental U.S.A.

| FOR ORDERS | ADD | FOR ORDERS | ADD |
|------------|---------|----------------|---------|
| \$25-100 | \$4.50 | \$751-1,000 | \$12.50 |
| \$101-250 | \$6.00 | \$1,001-1,500 | \$16.50 |
| \$251-500 | \$8.00 | \$1,501-2,000 | \$20.00 |
| \$501-750 | \$10.50 | \$2,001 and up | \$25.00 |

Circle (18) on Reply Card

More about getting started in computer repair

TIPS

- Major brands are easy to service.
- Needed: schematics, diagnostic software.
- Smartest to work on brands sold locally.
- Get friendly/closest authorized dealer.

The last installment of *Computer Corner* covered some of the aspects of getting started in microcomputer repair. This installment completes that task. One thing that is nice about servicing the major brands of computers is that most are easy to service. For example, the top of the Tan-

One thing that is nice about servicing the major brands of computers is that most are easy to service.

dy line, the 3000 series (HD and HL), come apart by removing only three identical Phillips head screws off the back. Inside, one size Phillips head screw is used for all purposes, both holding peripheral cards in place and for holding sub-chassis to the main chassis. As far as I am concerned, that rates an A+ for serviceability!

Computers are made to be serviceable, but you will still need schematics and, more often than not, diagnostic software. Schematics, in many cases, can be obtained from either Sams or the manufacturer. Diagnostic software can be obtained from many sources, including the manufacturer, computer users' groups, and independent sources like Norton Utilities. I will be devoting a future column or two to using disk-based utilities.

Some computer manufacturers have gone out of their way to help the service technician.

Some computer manufacturers have gone out of their way to help the service technician. Zenith Data Systems, for example, has "burned" diagnostic routines, both high and low level, right into their monitor ROM. By changing one jumper on the circuit board in some models, all these utilities become available. This, too, will be covered in a future article.

Regardless of the size town or city you live in, there is probably a computer retailer somewhere near you. If you are smart, you will start out by confining your labors to working on brands that are sold locally. There is one very crucial reason for this: parts availability.

As in all types of repair work, doing the diagnosis is not much good if you can't replace the defective parts afterwards. Now, depending upon the type of computer as well as the specific part needed, parts procurement varies from easy to impossible. For example, with regard to most IBM "clones," which are machines functionally equivalent to a

specific IBM counterpart such as the PC, XT, or AT, just about every part is a standard one, available "off the shelf" from any digital parts mail order or wholesale house. On the other hand, if you are working on a Commodore 64, just about everything except the memory chips is going to be a special IC, available to my knowledge, from nowhere other than a Commodore authorized dealer.

I am sure you are a bit ahead of me at this point. Your best bet is to get friendly with the closest authorized sales dealer for the computer or computers you want to repair. This arrangement can be mutually profitable. Most individual dealers neither have the inclination or the know-how to run a profitable service department. If you can meet with the owner and figure out an arrangement, that

Meet with the owner (of a sales dealership) and figure out an arrangement.

person can act for you with the manufacturer to obtain parts and service literature. Then, the dealer can give you the repair work, either by referral or (more likely) by accepting the work directly and giving it to you on an independent contractor basis. That way, you can make money efficiently and the dealer can resell your repairs, making something as well.

What happens if you cannot get cooperation from your local computer dealers, as sometimes happens? Well, what I would do then is to do what one of my associates did. He called around the region until he found an out-of-town dealer who did not feel threatened by a repair dealership over 30 miles away, and now my associate gets his parts through the mail. Slower service is still better than no service.

... don't be afraid to tackle IBM personal computers. They work the same way all the rest do, using mostly standard parts.

By the way, don't be afraid to tackle IBM personal computers. They work the same way all the rest do, using mostly standard parts. The only exception is the ROM, available from IBM only, although again you may be able to find an authorized IBM sales dealer or even a service dealer to sell you one on some type of exchange basis.

Next time, I'll be talking about basic repairs to Commodore 64s, and the following month on disk drive diagnosis on IBM PC-compatible machines. In between now and next month, I'm giving you a homework assignment: Go out and find at least one source of generic computer parts and ICs, and at least one dealer, preferably Commodore, who will sell you parts.

COMING

- May—basic repairs to Commodore 64s
- June—disk-drive diagnosis for the IBM PC compatible machines


Continued from page 25

I started disconnecting all jumper links on the +12V source and found that many ICs were connected to it, each having a resistance of around 1,000Ω. The R751 pincushion resistor paralleled with all the ICs combined to give the low reading of 380Ω.

I called the Panasonic information line and asked one of the engineers if this was normal. After checking his notes, he said that the +12V source resistance can show as low as 200Ω.

Then I disconnected pin 4 of the flyback from the circuit and the low voltage increased to about 85V with some pulsing. When the vertical output transistors (Q451 and Q452) were disconnected from the circuit board, the low voltage increased to about +110V without the *motorboating*. I concluded that the flyback probably was defective. The symptoms were the same.

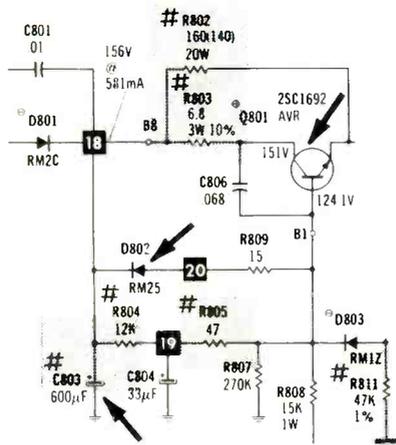Finally, I concluded that I had been troubleshooting the wrong end; the problem must be in the power supply. After a few other



D801 is the ac line-voltage rectifier and C803 is the peak-reading filter capacitor for the +156V supply that is the input for the Q801 voltage regulator which produces +123V for the horizontal-output transistor. In the first repair, a shorted D802 is applied +156V to Q801's base, attempting to raise the +123V to +156V. Of course, Q801 became shorted and ruined. In the second repair, an open C803 produced a low B+ voltage and a pulsing or motorboating symptom.

things were tried without improvement, I paralleled an electrolytic capacitor across C803 in the power supply, causing the B+ to skyrocket. Suddenly there was high voltage with audio but without motorboating. (C803 is the peak-reading capacitor for the +156V source, and it is the *only* +156V filter capacitor.)

Measuring the B+ fuse voltage confirmed that the voltage now was the required +123V at the lowest setting of R812, the regulator control. What confused me was the tremendous drop in voltage from +123V to +55V; a 125% change in voltage.

Thinking back on my procedure, I realized if I had started by connecting a 100W bulb across the open fuse terminal, I would have seen the bulb barely lit, proving there wasn't a short or severe leakage. Therefore, the power supply would have been indicated. Sometimes the things we learn the hard way are valuable to us in the future.



NARDA ELECTRONICS REPAIR FORMS

Compare our prices
and variety
before
you buy
elsewhere!


In and out of warranty repair forms approved by all electronics manufacturers. Supplying the service industry's needs since 1973.

| | Form 101 | Form 515 | Form 520 | Form 525 | Form 923 | Form 950 |
|----------------------------|--|------------------|---|---|---------------------------------------|---|
| | SIX-PART ZIP SET Approved for State of California | SIX-PART ZIP SET | SIX-PART CONTINUOUS No carbon required | SIX-PART CONTINUOUS No carbon required Approved for State of California | FIVE-PART CONTINUOUS Bonded carbon | FIVE-PART CONTINUOUS Bonded carbon Approved for State of California |
| Quantity | | | | | | |
| 100 | \$21.00 | \$14.00 | Not available | Not available | Not available | Not available |
| 500 | \$49.00 | \$41.00 | \$115.00 | \$125.00 | \$34.00 | \$38.00 |
| 1,000-4,000 | \$75.00/M | \$62.00/M | \$94.00/M | \$99.00/M | \$56.00/M | \$60.00/M |
| *5,000-9,000 | \$63.00/M | \$51.00/M | \$89.00/M | \$94.00/M | \$51.00/M | \$55.00/M |
| *10,000-19,000 | \$61.00/M | \$46.00/M | \$84.00/M | \$89.00/M | \$50.00/M | \$51.00/M |
| *20,000-49,000 | Special quote | Special quote | \$80.00/M | \$84.00/M | \$49.00/M | \$50.00/M |
| *50,000 & up | Special quote | Special quote | Special quote | Special quote | Special quote | Special quote |
| *Shipped freight collect | | | | | | |
| Imprint Cost Four lines | \$15.50/M | \$15.50/M | \$15.50/M | \$15.50/M | \$15.50/M | \$15.50/M |
| Set-up Charge | \$13.00 | \$13.00 | None | None | None | None |

Send
all orders
& inquiries to:

NARDA, Inc.
Attn: Forms Dept.
10 E. 22nd St.
Lombard, IL 60148

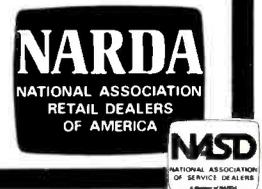or call toll-free
1-800-621-0298
(in Illinois, 312-953-8950)



Illinois residents add applicable sales tax

Circle (19) on Reply Card

CD player servicing: testing RF amp and optics

Every time a new type of product arrives on the scene, we're shelling out more money on some jig, test appliance or generator. It seems the folks who are responsible for all this new technology are seldom familiar with field repair, working as they do, in the rarefied atmosphere of an engineering lab. A telling example of this occurs in the adjustment manual for a name-brand VCR. The recommended method for adjusting the FM modulator requires a spectrum analyzer. All to align a \$300 VCR! It's just not practical. Change is great, but we all need help learning how to use the few grand worth of test equipment that's already depreciating on the bench.

The RF amp section gives pause to many techs, so that's where I started. Typically the RF amp is tested by observing the waveforms at test points, while the disc is playing. The problem occurs when the player is so messed up it won't play a disc to begin with. With many CD players, the microprocessor shuts the unit down when almost any failure occurs, making it difficult to isolate the cause. Some manufacturers provide a test mode, which disables shutdown, but implementations vary widely, and sometimes you still can't get an *eye* pattern or other waveform to monitor. So we need a method that allows us to check quickly the front end, even if the player is in shutdown or standby mode.

RF amp & optics

For the purpose of testing gain, all you need is a sine wave. A precise simulation of the complex RF waveform (*eye* pattern) is unnecessary. Figure 1 shows a simple bench setup. The resistor in series with the signal source serves to decouple generator impedance from the amp and eliminate it as a gain determinant. Without it, you'll get different gain readings depending on the generator. I used a Leader LAV-192, which has a top frequency of 1MHz. Although well below the nominal 4.3218MHz of the CD signal, I found it generally adequate.

Figure 2 is a simplified RF amplifier section. In some, this is in one IC; in others, several are used.

A quick way to avoid setting up the test rig is to *buzz* the circuit with your finger. Actually, pins on the prevalent surface-mount devices are rather small, so a sharp-pointed metal probe would be better. Buzzing the AC or BD input should produce clipping at the RFO (RF output) or FERR (focus error) test point. This proves the RF amp is live. Likewise, check the EF (tracking) amp; observe the output at the TERR (tracking error) test point.

If you want numbers, feed a 2mV, 1kHz sine wave into the input to be tested. Figures derived from one particular unit are outlined in the following table. Machines will differ somewhat, so keep that in mind when reviewing the figures. You will probably want to keep test results for the types of CD players you usually service.

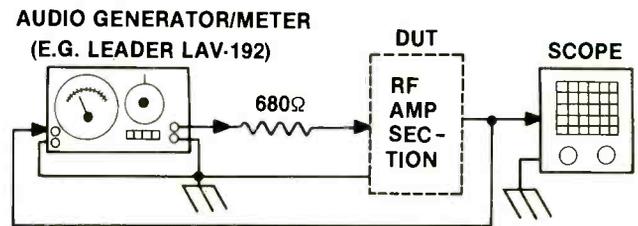


Figure 1. Test rig for RF amp gain check

Testing the optical block


Typical output level for AC, BD, E, or F detectors is roughly 2mV to 4mV p-p. Ironically, this is similar to the signal level produced by the *old-fashioned* phono cartridge that the laser replaces.

The low output amplitude of the photodetectors makes it difficult to measure without a scope having a 1mV vertical sensitivity. Even then, close attention must be paid to grounding for best results. Those of you whose scopes are equipped to subtract channel B from A usually can eliminate 60Hz noise from the waveform with a little trick. (By the way, most oscilloscopes that I've used accomplish subtraction by offering an Add mode and an inversion switch on one or the other channel, usually B. Adding an inverted signal is equivalent to subtraction.) Connect channel A to the test point, channel B to a source of 60Hz that is in phase with the noise on the desired signal. This usually is available on the power transformer secondary. With the mode switch set to Add, invert channel B and adjust vertical gain until the 60Hz noise on A is minimized, and all you have is the desired signal.

You can test for proper alignment of EF detectors with the scope set for an X-Y display. One channel of the scope is connected to RF amp, pin 9, the other to pin 10. At these points, the E and F signals already have gone through one stage of amplification, so are easily displayed. Adjust scope gain for equal amplitude on both channels and switch to X-Y. You should see an out-of-phase Lissajous display: a flattened oval with the top end about 45° to the left of vertical.

Disabling shutdown circuits

As I mentioned before, most CDPs have circuitry that shuts them down if they don't get the proper data from the disc. Sometimes disabling them is a simple matter of grounding a test pin on the microprocessor, but sometimes you need to get creative, and *force* certain flags, such as FOK (focus OK), LDON (laser diode on), or GFS (guarded frame sync) to their normal level in order to perform tests. This procedure varies greatly from unit to unit, and the only answer is a thorough understanding of the particular machines you service. There are other parts of the servo that can be broken and tested. Maybe we'll cover that in a future column.

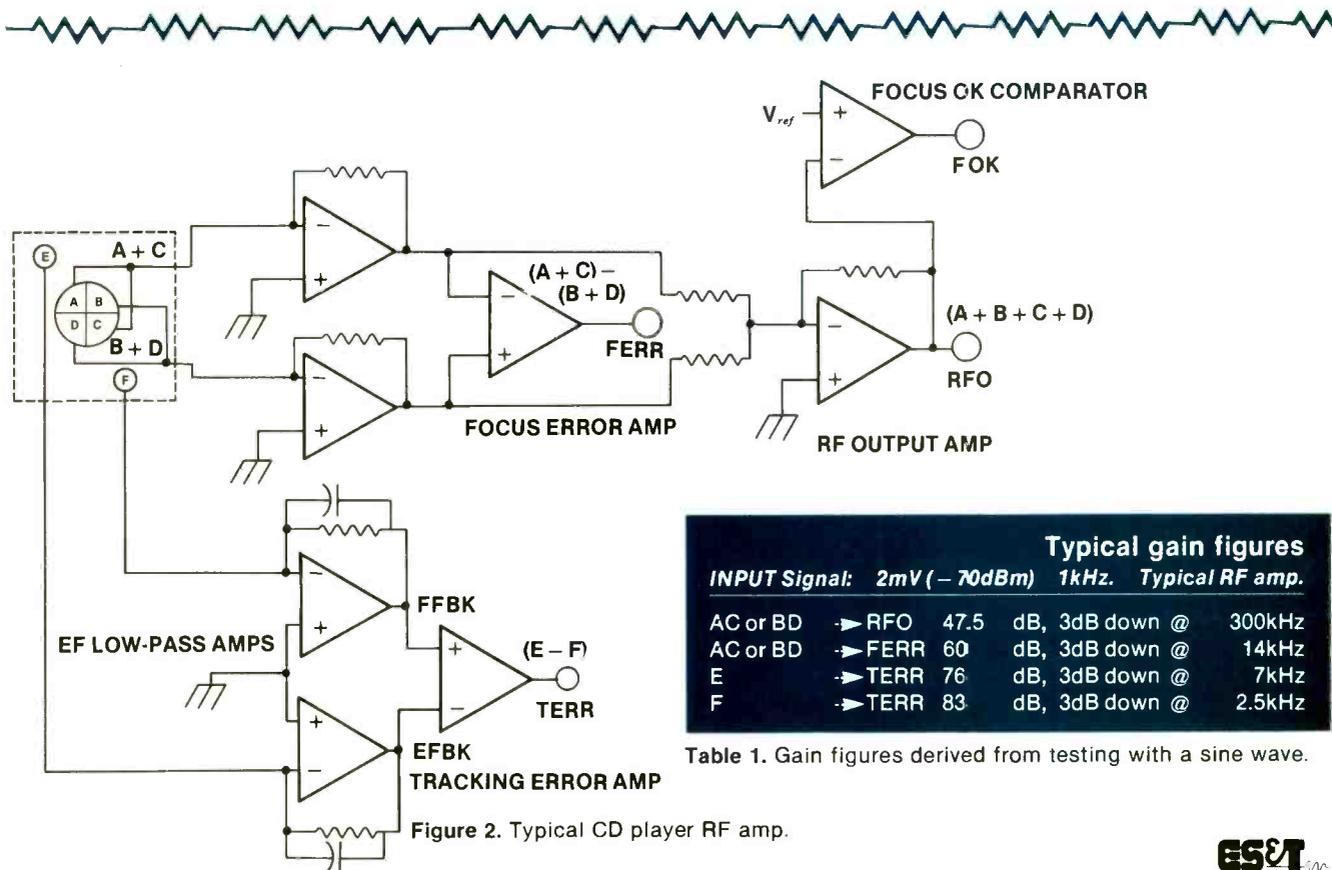


| Typical gain figures | | | |
|--|--------|---------------------|--------|
| INPUT Signal: 2mV (-70dBm) 1kHz. Typical RF amp. | | | |
| AC or BD | → RFO | 47.5 dB, 3dB down @ | 300kHz |
| AC or BD | → FERR | 60 dB, 3dB down @ | 14kHz |
| E | → TERR | 76 dB, 3dB down @ | 7kHz |
| F | → TERR | 83 dB, 3dB down @ | 2.5kHz |

Table 1. Gain figures derived from testing with a sine wave.



NESDA Computer Group

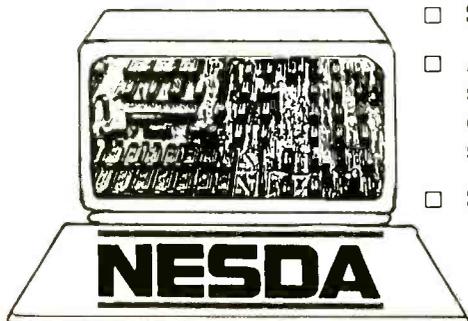COMPUTER SALES AND SERVICE DEALERS
WORKING TOGETHER



- Service training.
- Assistance in selecting in-house equipment and software.
- Specialized software for service management.

- Factory contacts for service literature and parts.
- Involvement in a stable and productive national trade association.

FOR MORE INFORMATION SEND BUSINESS CARD TO:
NESDA COMPUTER GROUP, 2708 WEST BERRY STREET
FORT WORTH, TEXAS 76109; PHONE (817) 921-9061

New Precision Duster Ultra-Filtered To <0.2 Microns



ULTRAJET... a new generation ultra-pure duster with powerful jet action. A compact, portable tool for safe, non-abrasive cleaning of sensitive electronic systems, computers, optical grade surfaces and precision mechanisms. Ultrajet comes with a variable control trigger valve in 3, 8 and 14 oz. sizes, ideal for field service and bench work. Complete Ultrajet System includes reusable, surgical-grade chrome valve, 12 oz. refill can and 36-inch extension hose. Economical refills available in 12 oz. and 20 oz. sizes.



Chemtronics
681 Old Willets Path
Hauppauge, NY 11788
800-645-5244
in NY 516-582-3322

© Copyright 1987 Chemtronics Inc.

Circle (20) or Reply Card

Literature

Source book, technical supplies

Contact East's comprehensive product guide for 1987 features a full line of tools and instruments, including many new products. Highlighted are static-control devices, an expanded tool kit line, state-of-the-art fiber-optic equipment, test instruments (DMMs, oscilloscopes, counters, power line monitors, disk drive testers, for example), hand tools such as screwdrivers, pliers, wrenches and crimpers, and soldering supplies. All products are described in detail with price specifications and color photos.

Circle (125) on Reply Card

Repairing Atari products?

Replacement parts for Atari products are described in the *Best Electronics* catalog. According to Best, the once-dwindling Atari re-

pair business again is lucrative. Along with a full stock of the most common replacement parts, Best offers repair/technical information to service centers confronted with an Atari-related, hard-to-solve problem.

Circle (126) on Reply Card

Full-line mail order

Global Specialties, an *Interplex Electronics* company, has announced establishment of a mail order division to market the company's complete line of electronic testing and prototyping equipment. A full-line catalog, including ordering instructions, an order form, and a postage-paid return envelope has been mailed to a selected list of potential end-users throughout the country. An 800 number for direct telephone orders also is featured.

Circle (127) on Reply Card

New or reconditioned equipment

A 20-page electronic test equipment catalog and price list from

Accutest Instruments features thousands of off-the-shelf items, both new and custom-reconditioned, at up to 70% off original list prices. All custom-reconditioned equipment is checked and precision-calibrated by trained technicians for performance that is recommended by the company as both accurate and reliable.

Circle (128) on Reply Card

MTS Simplified Guide

Sencore Electronics announces the MTS Simplified Guide that is intended to give the reader the background needed to analyze stereo televisions quickly and accurately. The MTS Simplified Guide will teach many aspects of TV stereo, and show you many tips to use in servicing MTS chassis. An extensive, yet simplified theory section is included.

There are a number of servicing aids including a simplified block diagram, trouble tree, and many quick test procedures.

Circle (129) on Reply Card

Books

Editor's note: Periodically *Electronic Servicing & Technology* features books dealing with subjects of interest to our readers. Please direct inquiries and orders to the publisher at the address given, rather than to us.

Electronic Connections, Home and Car Entertainment Systems, by Martin Clifford, Prentice-Hall, 414 pages, \$24.95, hardbound.

Electronic connections have reassumed their importance in the servicing industry. In the recent past, each consumer electronics product was designed as an independent entity neatly packaged in its own cabinet, with only a power cord and/or downlead exposed. Came stereo components, sound amplifiers, multiple televisions in many households, VCRs, and computers and their peripherals: The

once-integrated (now-fragmented) units became only as good as their cables, ports, jacks, adapters and other connections. This book covers the subject thoroughly, with many easy-to-follow schematics, diagrams and other illustrations. Order No. 250498.

Published by Prentice-Hall, Inc., Englewood Cliffs, NJ 07632; 1-800-223-2336.

VCR Troubleshooting & Repair Guide, by Robert C. Brenner and Gregory R. Capelo; Howard W. Sams, 256 pages, \$19.95, paperback.

A preventive maintenance and troubleshooting reference for VCRs, this guide may be used by electronics enthusiasts with limited experience. The servicing technician will appreciate the more sophisticated service and repair functions that also are included. Among the topics covered:

- Introduction to VCR maintenance
- Basic troubleshooting
- Routine preventive maintenance
- Specific troubleshooting and repair
- Magnetic recording theory

- VCR operating theory
- Advanced troubleshooting

When ordering, specify No. 22507.

Published by Howard W. Sams & Company, 4300 W. 62nd St., Indianapolis, IN 46268; 1-800-428-SAMS.

Electronics Math, by R. Jesse Phagan; Tab Books, 256 pages, \$15.45, paperback, \$22.95 hardbound.

This guide to electronics math comes right to the point in showing how to use mathematics as a practical electronics tool. The author avoids the overly theoretical approach in favor of leading readers logically from the basics of scientific notation through the principles of ac and dc circuit math and on into transformers, inductive and capacitive reactance. Within this framework, the reader is introduced to using the oscilloscope for measuring phase shift, the theory and applications of time constants used in R-L circuits, and a short course in understanding power supplies: how to measure them and make any necessary modifications. These subjects and more are fully illustrated.

Published by Tab Books Inc., Blue Ridge Summit, PA 17214; 717-794-2191.

ES&T

ANSWERS to the QUIZ

By Sam Wilson

Questions are on page 26

1. 48Ω. Figure A shows the connection for the resistor. Current through first lamp:

$$I = \frac{P}{V} = \frac{6W}{6V} = 1A$$

Because the second lamp only can conduct 1/2A (given), it follows that

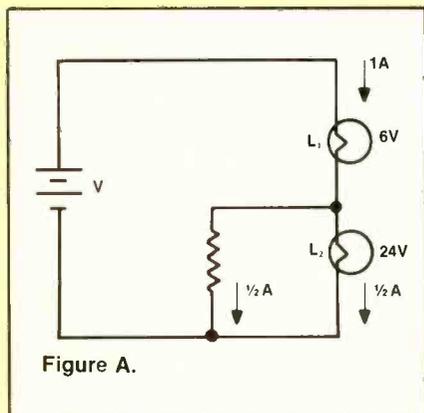


Figure A.

the resistor must provide a path for the remaining 1/2A.

$$\text{Voltage across second lamp: } V = \frac{P}{I} = \frac{12}{1/2} = 24V$$

$$R = \frac{V}{I} = \frac{24}{1/2} = 48\Omega$$

2. 30V. The voltages across the lamps are 6V and 24V. The battery must supply the total voltage drop, or, $6 + 24 = 30V$

3. A. The cathode of the diode is always marked in some way. Note the thick section on the cathode lead.

4. A. If either or both inputs (switches) are grounded (logic 0) the output is zero. Only when the two switches are in the logic 1 position (+5V) will the output be

+5V. The truth table looks like this:

| A | B | Vout |
|---|---|------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

The truth table shows that the circuit is an AND

5. D. Operational amplifiers that require only a positive supply voltage are in use.

6. B. Both are breakover diodes. The diac will conduct in either direction if a sufficiently high voltage is connected across it. The 4-layer diode conducts readily in one direction but not in the other.


7. A. The curve marked with an X shows a higher current for a given voltage. That occurs when the temperature is higher.

8. A. A minimum loss pad is designed like a T pad. However, the T resistor closest to the lower resistance being matched is removed.

9. 1.5Ω. The resistance value is calculated by the equation:

$$R = \frac{R_f \times R_{in}}{R_f + R_{in}}$$

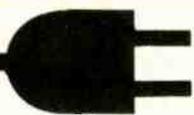10. C. The op-amp connection of Figure 7 is a well-known current-to-voltage circuit.



Plug in!

To the NESDA system.

YOUR BUSINESS is in the world's fastest changing industry. If you're not careful, you could find your business in the dark.

But, you don't have to stay there.

Through a system of local, state, and regional groups, the National Electronics Sales & Service Dealers Assn. (NESDA) keeps members up-to-date with the fast pace of advancing technology while offering:

- ◆ Managerial and technical training.
- ◆ Business contacts.
- ◆ Technical and management certification.
- ◆ Information on new products.
- ◆ Legislative activities that affect the industry.

Don't be left in the dark. Let the NESDA system work FOR YOU!

For more information and an application, write to:
NESDA, 2708 W. Berry St., Ft. Worth, TX 76109; Ph (817) 921-9061

Name _____

Bus. Name _____

Address _____

State _____ Zip _____ Phone _____

Member of State Local Assn. _____

HIGH VOLTAGE TRIPLERS/MULTIPLIERS

REPLACEMENT FOR

ECG®/GE®/SK®

| | | |
|---------------------|-------|------|
| 500A/GE527 & SK3304 | 8.75 | 6.95 |
| 523/GE528 & SK3306 | 8.85 | 7.20 |
| 526A/SK3306 | 8.85 | 7.20 |
| 528/SK3906 | 10.70 | 8.70 |
| 529/GE529 & SK3307 | 9.99 | 7.95 |

3 MIN. 100 MIN.

OUTPUT TRANSISTORS

| | | | |
|-------------------|------|------|------|
| 165/SK3115 & GE38 | 2.25 | 1.95 | 1.75 |
| 238/GE37 & SK3710 | 2.25 | 1.95 | 1.75 |
| 283/SK3467 | 2.75 | 2.35 | 1.80 |
| 2SD1341P | 2.25 | 1.95 | 1.75 |
| 2SC1172B | 2.25 | 1.95 | 1.55 |

5 MIN. 50 MIN. 100 MIN.

AUDIO POWER

| TYPE | 10 min | 50 min | 100 min | TYPE | 10 min | 50 min | 100 min | TYPE | 10 min | 50 min | 100 min |
|------------|--------|--------|---------|------------|--------|--------|---------|------------|--------|--------|---------|
| 152/SK3893 | .30 | .25 | .21 | 196/SK3054 | .49 | .44 | .39 | 291/SK3440 | .49 | .44 | .39 |
| 153/SK3274 | .30 | .25 | .21 | 197/SK3083 | .59 | .54 | .49 | 292/SK3441 | .49 | .45 | .40 |

RECTIFIER DIODES

| | | | | |
|-----|------------------------------|-----|-----|-----|
| 125 | 1000V/2.5A | 7c | 6c | 5c |
| 156 | 1000V/5A | 18c | 16c | 13c |
| 506 | DAMPER/HI-VOLT—FAST RECOVERY | 29c | 24c | 19c |

\$\$\$ ADDITIONAL SAVINGS \$\$\$

| | | | | | | | |
|-------|------|------|------|-----|-----|-----|-----|
| 102A | .35 | .32 | .29 | 171 | .49 | .44 | .38 |
| 123A | .18 | .16 | .14 | 184 | .38 | .35 | .28 |
| 123AP | .13 | .11 | .09 | 185 | .38 | .35 | .28 |
| 128 | .38 | .35 | .29 | 198 | .60 | .54 | .49 |
| 129 | .38 | .35 | .29 | 199 | .18 | .15 | .12 |
| 130 | .59 | .55 | .49 | 234 | .19 | .16 | .13 |
| 159 | .16 | .13 | .11 | 375 | .44 | .42 | .39 |
| 162 | 2.25 | 1.95 | 1.49 | 712 | .75 | .69 | .60 |
| 163A | 2.35 | 1.99 | 1.55 | | | | |

FOR A COMPLETE LIST CALL OR WRITE—C.O.D. Orders Welcome (Min. Order \$25)

DIGITRON ELECTRONICS

110 HILLSIDE AVENUE, SPRINGFIELD, NEW JERSEY 07081
Toll Free 1-800-526-4928 In NJ 201-379-9016 Telex 138441
PRICES SUBJECT TO CHANGE WITHOUT NOTICE. OFFER GOOD WHILE SUPPLY LASTS.
ECG is a Trade Mark of Phillips ECG, Digatron Ele. not associated with Phillips ECG.

Circle (21) on Reply Card

Readers' Exchange

Wanted:

Good, used CRT 510ZEB22 (not 510ZB22), original is from MGA/Mitsubishi model CS1971; Rider's radio manuals No. 2, 4, 5, 7 and 8. *Mike's Repair Service, M. Danish, P.O. Box 217, Aberdeen Proving Ground, MD 21005; 301-272-4984, evenings.*

Sams Scanner service manuals, SD-1, SD-4, SD-5, SD-7, SD-8, SD-9 and SD-10; service information on Luxman stereo R-1120. *Billy Stewart, P.O. Box 2076, Hickory, NC 28603-2076.*

VHF and UHF mobile radio, prefer two channel, needs PL or provision for PL board; base radio; UHF and VHF Handy Talkies; battery packs or whole, broken redecom/Cook's XF617 radio; deviation meter; 1COM O2AT and O4AT; any type of laser items; repair manual and/or not-working Hallicrafter's 2-meter radio model H2M 1000; UHF repeater, with or without duplexer, any condition, need not work. *Gary Bernard, P.O. Box 5523, Merritt Island, FL 32954.*

Telefunken, Becker and Ampex tube audio equipment and reel-to-reel tape machines; schematics for above. Interested in prewar Telefunken pre-amp tuners, the Becker tube radio for autos and the Ampex 351-2 or MR-70 tube tape recorders; help in finding units or schematics will be appreciated. *Mike Milbert, 18 Warrior Brook Court, Germantown, MD 20874.*

Signal-strength meter for CATV levels. *John Russo, 1057 Big Pine Drive, Santa Maria, CA 93454; 805-925-2173, evenings, 805-925-8773, days.*

Knight RF generator and signal tracer (83Y135) with manuals; Sams TR-82 Photofact; Tekfax manuals 100, 102, 117. *Charles T. Huth, 229 Melmore St., Tiffin, OH 44883.*

Schematic for Heathkit regulated power supply model IP-32. Will buy or copy and return. *William A. Thoma, 762 Silverleaf Drive, Dayton, OH 45431.*

Owner/operating manual for Crusader 300 amateur bilinear amplifier, or the name and address of the manufacturer. *John Lykins, 404-H Glascock Drive, Flemingsburg, KY 41041; 606-849-8681.*

Service information and owner's manual for TEAC reel-to-reel tape recorder, model A4010S. Will copy and return, or will buy outright. *Tri-City TV, Route No. 3, Birch Tree, MO 65438.*

Service literature for Sony 4-203W (Sams 774-3 or Sony S.M.). Help appreciated. Will pay. *Larry's Island TV; 813-472-4100.*

Dual-trace, dual-time-base scope, 60MHz to 100MHz; sweep/function generator with lin/log sweep; benchr paddle. All with manuals, and at low price. *John Waskowitz, 580 83rd St., Brooklyn, NY 11209.*

Sams CB Radio manuals - volumes 148-154, 166, 167, 169-177, 179-207, 281, 282, 284-293. *Larry Jackson, Route 2, Box 299J, Hamptonville, NC 27020.*

Sencore VA62 VCR test accessory, and NTSC accessory. *Al's TV, P.O. Box 115, Anita, IA 50020; 712-762-4210.*

Radio Electronics, June 1971, or any parts, information, board or layout for RF pre-amp article. *Merimack, Attn: Hilary, 986 Monroe Ave., Rochester, NY 14620.*

Sencore Powerite No. PR57 in good working condition. Send price. *Ron Grega, 107 Ridgeview Drive, Dunmore, PA 18512; 717-547-6842.*

Any 2-way radios, HTs, CBs, scanners. Need not work. Cheap color computer with one disk drive, can be obsolete model, working or not. Deviation meter and frequency counter. Any lasers and related items. Also, Yeasu FT727RA, ICOMO2AT, ICOM 04At. *P.O. 5523, Merritt Island, FL 32954.*

Tube, type 812A. Manual and schematic for Precision signal generator E-200-C. Will buy or copy and return. *John Zuba, 23 Patton St., High Bridge, NJ 08829; 201-638-8370.*

EICO model 232, working or not. *P.S. Martinez, P.O. Box 20972, Phoenix, AZ 85036.*

Keypad tuner switch No. 56D33-1 for Admiral chassis 28M55. *Dave Morning, 24370 Hedgewood Ave., Westlake, OH 44145.*

Schematic for Panasonic AM-FM phono-stereo combination, model SE 1160. Out-of-print with Panasonic, no Sams folder or book. Copy appreciated, or will copy and return at my expense. *R.H. Muller, 1201 Aloha Lane, Clearwater, FL 33515.*

Pantek No. KR85, 4-digit, 16-pin display, originally used in Litton microwave, model 420. *Robert E. Seibert, R.D. No. 1, Box 248, Lambertville, NJ 08530.*

NRI TV course or similar instruction; Sencore VA48. *Alan Weinber, 1742 Avenida Sirio, Tucson, AZ 85710; 602-747-5299.*

Manual and/or schematic for Fairchild dual-trace oscilloscope, model 776H. Will buy or copy and return. *A. Szalay, 3838 N. Whittier Place, Indianapolis, IN 46226.*

Service manuals for Advent projection televisions, model 1000A and VB761. *Fred Jones Jr., Fred's Electronic Service, 1203 Corlies Ave., Neptune, NJ 07753; 201-988-8841.*

Horizontal flyback transformer for Quasar color TV receiver, model WP3422QW. Transformer part number is 25-9033A 82, TLF-6032F. *E. Patrick Harrigan, 5165 South Magellan Drive, New Berlin, WI 53151; 414-425-6184.*

Voltage regulator STR459 as used in TV receiver auto-voltage sets. Prepared to pay cost. *Ivan Hamilton, P.O. Box 423, St. Kitts, West Indies; 809-465-8500.*

Schematic and information for Precision model E-200 RF signal generator. *Doug Heimstead, 1349 Hillcrest Drive, Fridley, MN 55432.*

Picture tube No. 330WB22, Sony part No. 873970205, working condition. Send purchase requirements. *Snow, R.R. No. 2, Box 596, Yarmouth, ME 04096.*

Setup chart for checking old 4-pin tubes (45, 27, etc.) in EICO model 666 tube tester. Will copy and return or pay for copy. *Don Maurer TV, 29 S. 4th St., Lebanon, PA 17042.*

Schematic for Ross radio, RE8000. Will buy or copy and return. *Rivera TV, 9235 Telegraph Road, P100, Rivera, CA 99660; 213-949-2161.*

Horizontal output transformer No. AC-145629 for Crosley model 9-419M1 television, or substitute part Stancor A-8128/1 or Merit HVO-3. *Myron H. Freedman, Mickey's TV Service, 8915 E. Bellevue St., Tucson, AZ 85715.*

Bearcat 210 scanner custom 8-pin chip; Motorola SC74012P, or cross-reference and copy of the schematic. Will buy or copy and return. *Larry Bivins, 309 Burton Court, Thousand Oaks, CA 91360.*

Transformers rewound (someone in the industry who has the know-how and equipment); power and audio outputs. *Kenneth L. Mixon, 401 E. San Pedro Ave., Perry, FL 32347; 904-584-2116.*

Service manuals and schematics for CPI frequency counter FC-70 and frequency converter FA-70. Will buy or copy and return. *Black Mountain Electronics, 186 E. May St., Heppner, OR 97836; 503-676-5560.*

Power transformer for Heathkit oscilloscope, model IO-18, part No. 54-103-24, transformer no longer available from Heath; B&W picture tube No. 440 ANB4 for Panasonic television No. TR-216. *Joseph S. Grishin, 976 Ray Road, Wantagh, NY 11793; 516-785-8298.*

Magnavox flyback transformer, Fly 360, part No. 361308-1/c Thordarson, for Magnavox B&W portable television. *J. Kapral, 101 Newberry Circle, Oak Ridge, TN 37830; 615-432-1432, call collect.*

Copy of manual or schematic for EICO model 369 solid-state version, TV sweep-marker generator. *Jack Lionel, Jalisa Techs, P.O. Box 604, Bloomfield, NJ 07003.*

Schematic or service manual for Electronics Relays GR Power Chopper (power factor corrector). Company is out of business. *Leo Unger, 4066 Inglewood Blvd., Los Angeles, CA 90066.*

Glass dial scales for Radiola model 76Z-12, and for Telefunken Caprice 5051W. *Paul M. Williams, 2364 Beaver Valley Pike, New Providence, PA 17560.*

HV tripler part no. 561B026-1 for MGA color television, model CS196. Please send price. *Augustine's TV and Radio Service, 530 N. 9th St., Reading, PA 19604; 215-372-5438.*

NTSC generator, state price, model and condition. *J. Konney, 2519 N. Austin, Chicago, IL 60639; 312-237-7845.*

Continued on page 64

Products

SK solid-state replacement guide

A new edition of the RCA "SK Guide to Reliable Replacement Semiconductors" has been introduced by RCA's *Distributor and Special Products Division*.

This edition contains 2,900 SK and KH types that replace more than 214,000 industry types. Included for the first time are QMOS logic devices and an extensive line of RF devices.

Circle (75) on Reply Card

TV-RF signal analyzer

Sencore Electronics has completed development of the FS73 Channelizer Jr. The instrument is accurate within 1dB for each channel. Sencore reports that the FS73 has a fully auto-ranging meter, per-

forms tests not found elsewhere and is fully portable.

The FS73 reportedly provides an exclusive all channel microprocessor-controlled tuner for checking every standard and cable channel RF level with FCC accuracy. Exclusive 1-touch frequency offset allows the customer to select either normal, HRC, or ICC carrier shift. Dial in the channel, then read the level on the fully auto-ranging meter. This same method is used to measure the RF audio and FM sound (broadcast) through the same input.

Circle (76) on Reply Card

Low-cost transmission test set

A full transmission test set has been introduced by *Triplett Corporation* for the communications market.

Compact and lightweight, this basic transmission test set was designed for use both indoors and outdoors by service technicians, telephone installers, repairmen

and anyone else involved in testing communications equipment.

The test set performs the following functions: circuit loss (with an accuracy of $\pm 0.2\text{dB}$); circuit noise (accuracy of $\pm 0.2\text{dB}$ at 1,000 Hz); power influence (accuracy of $\pm 0.4\text{dB}$ at 1,000 Hz); and line current (accuracy of $\pm 2\%$).

A standard volt meter is also included for measuring ac and dc volts, plus there's a special ohmmeter for conducting 8455 tests.

Circle (77) on Reply Card

Clean, control static-generated dust

Chemtronics' Screen Prep provides a convenient method for cleaning smudges and stains that result from equipment handling prior to or during service calls. It also effectively removes CRT screen contaminants that inhibit and distort vision, thereby reducing eye strain and improving operator efficiency.

Circle (78) on Reply Card



You Can Be

One Of The

20,000 Technicians

Certified BY ISCET



The International Society Of Certified Electronics Technicians offers permanent certification by administering the CET exam with the FCC recognized communications option for \$20. A second exam on FCC regulations for a \$10 fee is required for a Radiotelephone License. Upon passing, technicians receive both a permanent Radiotelephone Operator Certificate and a CET Certificate issued by ISCET.

ISCET Offers License Renewal

ISCET has developed a program for registration of those who currently hold a valid Radiotelephone Operator License. By sending a completed application, a photocopy of your FCC License, and \$10 your license will be renewed with the assurance of a recognized national technicians association behind it.

For More Information Contact:
ISCET 2708 W. Berry, Ft. Worth, TX
76109. (817) 921-9101

ATTENTION TECHNICIANS

- ★ JOB OPENINGS
- ★ MONTHLY TECHNICAL TRAINING PROGRAM
- ★ BUSINESS MANAGEMENT TRAINING
- ★ LOW COST INSURANCE
- ★ CERTIFICATION
- ★ TECHNICAL SEMINARS

All of this in a nonprofit international association for technicians


FIND OUT MORE:



604 N. Jackson St.
Greencastle, IN 46135

CIE Cleveland Institute of Electronics

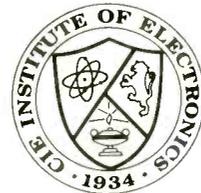Accredited Member National Home Study Council



CIE is the world's largest independent study electronics school. We offer ten courses covering basic electronics to advanced digital and microprocessor technology. An Associate in Applied Science in Electronics Engineering Technology is also offered.

Study at home — no classes. Programs accredited and eligible for VA benefits.

CIE Cleveland Institute of Electronics
1776 East 17th St., Cleveland, Ohio 44114
YES! I want to get started. Send me my CIE school catalog including details about the Associate Degree program.

Print Name _____
Address _____ Apt. _____
City _____ State _____ Zip _____
Age _____ Area Code/Phone No. _____
Check box for G.I. Bulletin on Educational Benefits
 Veteran Active Duty MAIL TODAY!

AES-21

Circle (22) on Reply Card

Continued from page 62

Sencore VA48, still in original carton; Conar 255 solid-state trigger scope, ESR capacitor analyst; EICO 667 dynamic tube tester. Make offer, all most be sold. *R.M. Hoffmeyer, 1170 Pino Solo Drive, Santa Maria, CA 93455; 805-937-4078.*

Tequipment oscilloscope, type 52; F.S. meter for television; Hickok VTVM with large meter face. *Jim Shoemaker, 600 First St., Leechburg, PA 15656; 412-842-8321.*

Old B&K scopes, models 1431, 1460, 1435, any condition. *Mike Shelton, 2708 May Drive, Burlington, NC 27215.*

Used Panasonic telephone answering machine model KX-T1625 or KX-T1730, need not be working, but must be complete and include ac adapter (if required). Please indicate model, condition and asking price. *Dave, P.O. Box 151, Poway, CA 92064.*

Micronta DMM, model 22-200 (by Radio Shack); Robyn CB radio, model T240D; Lectrotech TO-60, TO-55 or TO-50 scope; Hallicrafters short wave radio S-120 or any other models. All, working or not. Also, a copy of tube setup chart for Hickok 53 tube tester. *Stanley Chalker, 1176 Smithsonian Ave., Youngstown, OH 44505.*

Odyssey video game cartridges. *Donald Lewis, Route 1, Box 308, Central City, NE 68826.*

By high school class to repair donated video equipment, schematics for the following—Sony ac power adapter, AC-3400; Sony camera adapter, CMA-1 and CMA-2; Sony monitor, PVM400; Sony camera, AVE-3450; Sony reel-to-reel recorder, AV-3400 and Panasonic monitor, TN63. Will purchase or copy and return. *Jerry St. Jacques, Manchester Technical Center, 4420 Manchester Road, Middletown, OH 45042; 513-422-6446.*

For Sale:

Leader sine/square wave generator, model 120A, make offer; numerous electronics books and parts, s.a.s.e. for list. *Mike Shelton, 2708 May Drive, Burlington, NC 27215.*

TEK 545B scope, \$300 or best offer; Heath condenser checker, Systron-Donner DMM, mini digit DPM, two boxes assorted tubes, gates, limiters. Everything must sell. *Tim's Audio Service, P.O. Box 2461, Augusta, ME 04330.*

Sams Photofact folders: 67 to 625 plus 33 others. \$300 plus shipping. *Lyle D. Kinney, R.D. No. 4, Box 295, Bath, NY 14810; 607-776-9234.*

Sams Photofact folders No. 1500 to No. 1955, a total of 445 issues, new, unopened, \$3 each as a package, no singles. Same for Ar 19 to 79 and TR15 to 64, \$2 per issue. *Stanley Chalker, 1176 Smithsonian Ave., Youngstown, OH 44505.*

Hitachi 20MHz dual-trace oscilloscope, model V-212 with probes. Bought new, never used, \$300 plus shipping. *Victor M. Ortiz, Ortiz TV Service, Avenue Ferrocarril, Isabela, Puerto Rico 09662.*

Sony AVC-1400 B&W video camera and power unit with two lens, telefoto and wide angle, like new, \$125; ALCO mini toggle switches; many SPDT 6A, 125V, new, \$1 each or two for \$1.50. *Rygwalski, 2100 S. Beech Road, West Palm Beach, FL 33409; 305-683-2472, evenings.*

Sencore model CG141 color generator, \$40; Sencore model TF166 transistor and FET tester, \$60, both include manuals and leads; Heathkit model IP-17 power supply, \$100 with manual, no reasonable offers refused. *Dennis Dillon, 1616 S. 94th St., West Allis, WI 53214; 414-774-2255.*

Tubes, new and used, \$1 up. Used tubes, untested and unsorted, \$35 per hundred, special. Send \$1 (deductible from order) with list of your needs and prices. Shipping charges are extra. *Ed Barlow, P.O. Box 29, Tweed, Ontario, Canada K0K 3J0.*

Modules—two MAE001A, three MAE001B, \$5 each; three MAL001B, one MAL001A, \$6 each; three MAG001B, \$7 each; seven PM200, \$3 each; one MAK001, one MLK002, \$10 each; one MAN002A, six MAD001A, \$4 each. All, \$145 plus shipping. *M.E. Andrews Jr., Box 91, Exeter, RI 02822.*

Radar Range scope, early 1940s, by Dumont, weighs approximately 90 lbs, several G's shock resistant; Webcor hi-fi, reel-to-reel, tube-type tape recorder, model TP2718-1, weighs approximately 40 lbs. Make offers on each. *Shannon O. Sellers, 7908 Franklin Drive, Bessemer, AL 35023.*

More than 100 TV tubes, \$20; pilot bulbs and fuses. *Al Crispo, 3225 Chipmunk Drive, New Port Richey, FL 33552.*

Tentelometer and spindle-height gauges, \$495. *J. Gilbert, 4049 N. Newhall St., Milwaukee, WI 53211; 414-962-0974.*

B&K electronics multimeter, model 290; B&K transistor tester with case, model 510; Diehl SuperTech model IV; Viz WP 29 monitor, 150Vac; all, \$600. Will ship UPS or c.o.d. *John Cooper, Route 3, Box 925, Kountze, TX 77625.*

Parts for following color sets—Quasar T915, 919; GGY16227A Ward's E22 chassis; CE8181W Ward's E21-32 chassis; 25EC58 Zenith; M25 Admiral; T-995 Magnavox; RCA CTC48, 58, 86, 88, 91. B&W sets—Sears 528.51330, RCA KCS 183E, 195B. Many other chassis on hand. *D.J. Aijala, 50 Fir Circle, Babbitt, MN 55706.*

Sencore SG165 stereo analyzer, \$250. *Ray LaFrance, P.O. Box 1279, Medford, OR 97501; 503-779-4329 or 503-772-2141.*

B&K model 1570A 80 MHz scope, quad trace with probe case and three probes (10x, 10:1/direct, RF det.), has scope cover, \$1,000; B&K universal counter, model 1822, 175MHz, \$350. Both, mint condition, used only few times. *Ron Grega, 107 Ridgeview Drive, Dunmore, PA 18512; 717-347-6842.*

B&K model 707 tube tester, \$120; Amphenol model 860 color generator, \$100; Telemetric model 730 tuner-subber, \$80; degaussing coil, \$20; many modules and parts. Retiring. Prices include shipping. *Kaz Glista, 274 Newington Road, West Hartford, CT 06110; 203-666-6007.*

Sencore—VA48 video analyzer, SG165 stereo analyzer, CR70 CRT tester and rejuvenator, LC75 Z-meter, TF46 transistor tester, CT25 color-bar generator; B&K 667 tube tester. All new condition, complete with accessories and literature. Sams Photofact folders, complete, between No. 2229 and 2361, plus miscellaneous between No. 897 and 2132. Manufacturers' service manuals. Must sell; no reasonable offers refused. *Michael Schmaeling, Route 2, Box 1002, Irvington, AL 36544; 205-957-2892.*

B&K 1827 6-digit autoranging frequency counter with SA-27 antenna, BC-27 ac adapter-charger and manual, asking \$68; 300 new receiving tubes, mostly for color television, each tube boxed, asking \$325. Send s.a.s.e. for tube list—prefer pickup on tubes. Thordarson flyback No. 308, never used, \$15. Shipping and c.o.d. extra. *Ronald Kolasa, 4942 E. Flower Ave., Mesa, AZ 85206.*

Sams manuals—TSM No. 1 through 11, plus Nos. 13, 27, 30, 35, 42, 48, 49, 50, 52 through 62, 68, 73. AR 4, 8, 9, 10, 12, 19, 21, 23, 25, 28, 35, 45; MHF 177. Any book, \$3.50 postpaid, or make offer on any five or more. Need Sams CB207 manual; will give any three of above, or purchase. *Don Nash, 1444 Pulaski St., Port Charlotte, FL 33952.*

RCA repair parts for XL-100 TV CTC-70 series; 95% of parts in original boxes, net cost approximately \$500, will take \$50 plus postage. Send s.a.s.e. for list. *John Gorman, 210 Sprague Ave., South Plainfield, NJ 07080.*

Sams Photofact folders, 376 total between Nos. 63 through 1460. Make offer on one or all, send s.a.s.e. for list. *Donald Lewis, Route 1, Box 308, Central City, NE 68826.*

Jackson tube tester, model 658-1, \$75; EMC tube tester model 213, \$30, both check new tubes; B&K 283 DMM, like new, in original box, \$75. All prices plus shipping. *Kenneth Miller, 10027 Calvin St., Pittsburgh, PA 15235; 412-242-4701.*

Sencore VA48 with TR219, AT218, excellent condition, factory-refurbished one year ago, \$600. *Fred's TV Service, 3901 Rosewood Drive, Midwest City, OK 73110.*

Sencore VA62 with VC63, NT64, \$2800; Tentel HP6-1 head protrusion and eccentricity gauge, \$400; Tentel TSH-V4 spindle-height and elevator gauge, \$300; JVC VHS torque meter, \$250; JVC torque gauge, \$150. *Jim Bullington, P.O. Box 61, Thomaston, GA 30286; 404-647-2718.*

Tubes, transistors, magazines, diagrams, Sams Photofact folders, test equipment, radio parts, speakers; tube and parts location, send s.a.s.e. *Florian Rogowski, 25108 Cunningham, Warren, MI 48091.*

B&K 467 CRT restorer/analyzer with many adapters, \$225; B&K 520 transistor tester, \$85; B&K 1076 television analyst, \$95; B&K 707 tube tester, \$35; Sencore CA 122B color-circuit analyzer, \$35. All in excellent condition. *Frank Manera, 137 Lynch St., Providence, RI 02908; 401-831-7156.*

Sencore VA48 video analyzer, complete with box, books and cables, \$600, includes shipping, UPS, c.o.d. or cash. B&K 1076, best offer. *Charles TV, Route 210 and Poplar Lane, Indian Head, MD 20640; 301-743-7777.*

Sharp flyback-triplers, Nos. RTRNF0003PE22, RTRNF1133CE22, RTRNF1139CE22, RTRNF0001PE22 and deflection yoke No. RC1LH0007ME22, all for \$200 plus shipping. *Globe TV, 3407 Arlington Ave., Riverside, CA 92506; 714-684-9393.*

Photofact

These Photofact folders for TV receivers and other equipment have been released by Howard W. Sams & Co. since the last report in ES&T.

| | |
|---|--------|
| AOC Chassis M9C2-7K2/8K2 (RUN 10) | 2480-1 |
| GOLD STAR CMR-2030, CMR-9080 | 2478-1 |
| JC PENNEY 685-2218-00 (855-4305) | 2476-2 |
| PANASONIC CTG-1962R | 2479-1 |
| RCA GLR2750N/60T/80N/90B, Chassis CTC133A . . . | 2477-1 |
| SANYO 91C615N, 91C620N | 2475-2 |

| | |
|---|--------|
| SEARS 562.41420450/451/452 | 2474-1 |
| SEARS 564.42740550 | 2475-1 |
| SEARS 564.42001550, 564.42000550 | 2477-2 |
| PRODUCTION CHANGE BULLETIN SEARS 564.42540451 | 2478-3 |
| SONY Chassis SCC648Q-A/T-A/U-A | 2478-2 |
| SYLVANIA Chassis 19C401/402/403 | 2474-2 |
| SYLVANIA Chassis 25C401 thru 25C406 | 2480-2 |
| ZENITH B1310WC/W2/22S/82W/82W5/82WC/82WC5, S1306S, SB1327W, V3322S | 2479-2 |
| MONITOR HITACHI CM1216D | 2476-1 |

Classified

Advertising rates in the Classified Section are 85 cents per word, each insertion, and must be accompanied by payment to insure publications.

Each initial or abbreviation counts a full word.

Minimum classified charge is \$20.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$30.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or distributor.

FOR SALE

AUTOMOBILE RADIO and tape replacement parts. Delco, Chrysler, Philco-Ford, Motorola, Panasonic and many others. Large inventory. Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469. (212) 881-9600. National (800) 223-8314, NY State (800) 446-4430. 1-85-tfn

CABLE TV CONVERTERS & EQUIPMENT. Plans and parts. Build or buy. Send S.A.S.E. C&D Electronics, P.O. Box 1402, Dept. ES&T, Hope, Arkansas 71801. 1-86-tfn

SONY-TRINITRON REBUILTS are now available. Call for price & delivery, 1-716-621-5250. 7-86-tfn

VCR REPAIR SOLUTIONS for VHS models. Over 150 symptoms and cures. The hard ones. Send \$11.95 to Eagle Electronics, 2534 Miracle Lane, Mishawaka, IN 46545. 12-86-tf

SERVICE MANUALS. Large Shop has 18 yr. collection of duplicates. All original manufacturer. All new. Audio \$2.00, video \$5.00. Send SASE for list. Tape Recorder Clinic; 4850 E. Speedway; Tucson, Arizona 85712. 11-86-tfn

ATTENTION: Sylvania remote control motor for hospital televisions no. 23-99-383 for sale. With exchange \$39.00, without exchange \$47.00. Kinnirral Electronics, 68-26 64th Place, Glendale, N.Y. 11385. Tel. (718) 366-3859. 1-86-4t

SENCORE VA-48 VCR-TV ANALYZER. Excellent condition, \$500.00. Larry Colman, 28 Spring St., #20, Norwalk, CT 06854, 203-838-4284. 4-87-1t

PHOTOFACTS: Individual folders #1 to #1400 \$3.00. Above #1400 \$5.00. Sent same day first-class postpaid. Loeb, 414 Chestnut Lane, East Meadow, NY 11554. 4-87-6t

3000 COLOR TV REPAIR TIPS, 31 Brands 116 Page Manual. Send \$21.00 to A. Fernandex, Box 546110, Surfside, Florida 33154. 4-87-3t

PORTABLE TV STATION transmits VCR, camera or test generator signals 150 feet on UHF channel 15. Excellent for shops, schools, businesses and hobbyists. \$120 complete. SOLAS PRODUCTS, Box 665, Springhouse, PA 19477, (215) 723-4597. 4-87-1t

UPGRADE KIT FOR LINE ZAPPERS \$19.95. Stops negative pictures, improves clarity. Complete with add-on board. Complete kits available. C&C Specialties, 1432 Heim, Orange, CA 92665, (714) 998-6866. 4-87-1t

TV TROUBLESHOOTING. Over 120 schematic ILLUSTRATED problems-solutions of difficult repairs. Also, 12 steps to easier TV repair, 25 pages \$12.00. Bonus: Remarkable diagnostic tool. Determine operation of high voltage circuits every time, no mistakes. \$5.00. Jones, Box 702, Niceville, Fla. 32578. 4-87-3t

TV TOUGH DOGS 200 symptoms and cures. Send \$6.95 to DAVIS TV, 11772 Old Fashion Way, Garden Grove, CA 92640. 4-87-3t

HELP WANTED

CAMERA-VIDEO Technicians needed. Top pay and benefits for well trained and experienced technicians who are expert with consumer and/or industrial cameras and VCR's. Training by manufacturers such as Sony, Hitachi, Panasonic, etc., are necessary for job experience. Come to sunny Florida and enjoy your work & leisure time. Write or call ATLANTIC ELECTRONICS INC., 1232 NE 26th St., Ft. Lauderdale, FL 33305. (305) 564-8274 10 AM to 6:30 PM. Ask for Dave or Joe. 8-85-tfn

VIDEO/AUDIO technician needed. Top pay and benefits for well trained and experienced technicians who are expert with consumer TV and audio equipment. Training by manufacturers such as: Sony, Hitachi, RCA, Panasonic, etc. are necessary for job experience. Write or call: ATLANTIC ELECTRONICS, INC., 1881 NE 26th St., Ft. Lauderdale, FL 33305, 305-564-8274 (10 AM 6:30 PM). Ask for Dave or Joe. 06-86-tfn

MANAGER/TECHNICIAN needed to run electronics shop in Southwest Florida. We are looking for the best person possible to operate our electronics repair shop. Salary starts at \$32,000.00 per year or better, depending upon qualifications. Partnership of the company is also available. Please send resume to: M.C.R., INC., c/o Steven W. Vergo, 418 S. Barfield Drive, Marco Island, FL 33937. 4-87-1t

BUSINESS OPPORTUNITIES

T.V. SALES & SERVICE. Well established business located northern Virginia. Owner retiring and will help with financing. Call 703-972-7027 after 7:00 p.m. EST. 6/85-tfn

3 HOURS FROM SAN FRANCISCO, Electronic repair shop in Pine Forested foothills. Vision problem forces sale. 7 rm residence, lg beautiful gdn all shop equip included, \$155k min 50% dwn req (916) 872-1962. 10-86-tfn

TV REPAIR SHOP. Complete stock parts, literature, test and office equipment. Large hotel contacts. Middle of Silicon Valley, San Jose, California. 408-986-8232. Look first-make offer. 4-87-1t

Bus. Opportunity (Cont.)

JACKSONVILLE, FLORIDA: TV sales and service. Two businesses with long histories have owners retiring. Have proven gross sales of \$55,000 and \$171,000. Both offering training and owner financing. Land with one. VR business brokers. (904) 264-2164. 4-87-11

INDUSTRIAL ELECTRONICS SERVICE COMPANY. Come live & work in sunny Florida. Earn \$45.00/hr. Established accounts. Owner moving overseas. Asking \$40,000, (813) 923-8016. 4-87-11

TV/VCR SALES/SERVICE business for sale, well established (15 years) excellent location. Assume low rent lease option. (Family health problems force sale.) Great "MONEY MAKER", \$49,000.00 min. 50% down all (negotiable). T.V. Laboratories, Forest Avenue, Staten Island, New York 718-720-6825. 4-87-11


Educ.-Instruction

CABLE TV TRAINING—Training in Cable Television Technology. Learn construction, installation, and maintenance. Cable Correspondence Courses, Inc., P.O. Box 1319, St. Charles, MO 63302. 2-87-31

PERSONALIZED 24-HOUR SERVICE ON OVER 10,000 ELECTRONIC COMPONENTS & PRODUCTS...

CALL TOLL FREE

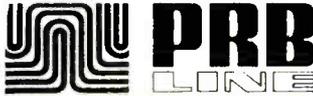IN
1-800-558-9572 WIS 1-800-242-9553
24 HOUR ORDERING: FAX: 414/473-4727



PROJECTOR-RECORDER BELT CORP.
P.O. Box 176 • Whitewater, WI 53190
TLX 4994411 PRBUSA

Circle (23) on Reply Card



"Tech's Guide To Pricing"
updated new 5th edition...a framework for setting rates that apply to Hi-Tech products...a formula that guarantees SUCCESS!
Call Toll Free for details 8/5
1-800-228-4338 CST

Circle (24) on Reply Card

A MUST FOR THE TV TECHNICIAN

UNIVERSAL CRT ADAPTER- Don't buy another socket for your CRT Tester! Join 10,000 satisfied buyers & WIN the Socket War! GUARANTEED to fit your tester. Test/clean/restore ALL Color, BW, Projection. \$59.99ppd w/Setup book, Visa, MC, COB.



1-800-331-9658
DANDY MFG. CO.

2323 Gibson, Muskogee, Oklahoma 74403

Circle (25) on Reply Card

Use ES&T classified ads

ELECTRONIC SERVICING & TECHNOLOGY Volume 7, No. 4 (USPS 462-050) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, P.O. Box 12901, Overland Park, KS 66212. Second Class Postage paid at Shawnee Mission, KS and additional mailing offices. POSTMASTER: Send address changes to ELECTRONIC SERVICING & TECHNOLOGY, P.O. Box 12952, Overland Park, KS 66212-9981.

Advertisers' Index

| | Page Number | Reader Service Number | Advertiser Hotline |
|--------------------------------------|---------------|-----------------------|--------------------|
| Automated Production Equipment Corp. | 29-30 | | 516/654-1197 |
| B&K Precision Dynascan Corp. | 3 | 3 | 312/889-9087 |
| Beckman Industrial Corp. | IFC | 1 | 714/671-4800 |
| C & S Sales | 24 | 13 | 800/292-7711 |
| Chemtronics, Inc. | 38A-38B,59 | 20 | 800/645-5244 |
| Cleveland Institute of Electronics | 30A-30B,63 | 22 | 800/321-2155 |
| Dandy Mfg. Co. | 66 | 25 | 800/331-9658 |
| Digitron Electronic | 61 | 21 | 800/526-4928 |
| Electronic Design Specialists, Inc. | 13,15 | 7 | 800/544-4150 |
| Electronic Specialists, Inc. | 39-40 | | 800/225-4876 |
| ETA | 63 | | |
| Fluke, John Mfg. Co., Inc. | 7 | 6 | 800/227-3800 |
| Fordham Radio Supply Co. | 55 | 18 | 800/645-9518 |
| ISCET | 63 | | 817/921-9101 |
| Jensen Tools Inc. | 30A-30B | | 602/968-6231 |
| Leader Instrument Corp. | 5 | 4,5 | 514/337-9500 |
| MCM Electronics | 21 | 11 | 800/543-4330 |
| Microwave Filter Co. | 38A-38B | | 800/448-1666 |
| NARDA | 57 | 19 | 312/953-8950 |
| National Technical Schools | 29-30 | | 800/BBE-TTER |
| NESDA | 59,61 | | 817/921-9061 |
| NRI Schools-Electronics Division | 27-28 | | 202/244-1600 |
| NTE Electronics, Inc. | 39-40 | | 800/631-1250 |
| OK Industries, Inc. | 19 | 8 | 800/523-0667 |
| OK Industries, Inc. | 29-30,38A-38B | | 800/523-0667 |
| Philips ECG | 23 | 12 | 800/225-8326 |
| Prentice-Hall Inc. | 30A-30B | | |
| Projector Recorder Belt Corp. | 66 | 23 | 800/558-9572 |
| RCA Distributor and Special Products | 27-28 | | 609/853-2441 |
| Sencore, Inc. | 45,47 | 14,15 | 800/843-3338 |
| Sencore, Inc. | 49,51 | 16,17 | 800/843-3338 |
| Simpson Electric Co. | 25 | 10 | 312/687-2265 |
| Sperry Tech, Inc. | 66 | 24 | 800/228-4338 |
| Tektronix, Inc. | IBC | 2 | 800/433-2323 |
| Tentel | 27-28 | | 800/538-6894 |
| Zenith | BC | | |

AD SALES OFFICES

ELECTRONIC
Servicing & Technology

KANSAS CITY, MISSOURI
Greg Garrison, Sales Manager
P.O. Box 12901
Overland Park, KS 66212
Phone: (913) 888-4664

NORWOOD, AUSTRALIA
Hastwell, Williamson, Rouse PTY. LTD.
P.O. Box 419
Norwood, S.A. 5067
Phone: 332-3322
Telex AA 87113

LONDON, ENGLAND
Nicholas McGeachin
Suite 460, Southbank House
Black Prince Rd.,
London SE1 7SJ England
Telex: 295555 LSPG
Telephones: Central Line 01 735-8171
Direct Line 01 587-1578

TOKYO, JAPAN
Haruki Hirayama,
EMS, Inc.
Sagami Bldg., 4-2-21, Shinjuku,
Shinjuku-ku, Tokyo 160, Japan
(03) 350-5666
Telex: 2322520 EMSINCJ
Cable: EMSINCPERIOD

New GPS Series: Tek sets the pace with SmartCursors™ and push-button ease.

Work faster, smarter, with two new general purpose scopes from Tektronix. The four-channel, 100 MHz 2246 and 2245 set the new, fast pace for measurements at the bench or in the field. They're easy to use and afford, by design.

On top: the 2246 with exclusive integrated push-button measurements. Measurements are accessed through easy, pop-up menus and implemented at the touch of a button. Measure peak volts, peak-to-peak, \pm peak, dc volts and gated volts with new hands-off convenience and on-screen readout of values.

SmartCursors™ track voltmeter measurements in the 2246 and visually indicate where ground and trigger levels are located. Or use cursors in the manual mode for immediate, effortless measurement of waveform parameters.

Both scopes build on performance you haven't seen at the bandwidth or prices. Lab grade features include sweep speeds to 2 ns/div. Vertical sensitivity of 2 mV/div at full bandwidth for low-level signal capture. Plus trigger

| Features | 2246 | 2245 |
|-----------------------|---|----------|
| Bandwidth | 100 MHz | 100 MHz |
| No. of Channels | 4 | 4 |
| Scale Factor Readout | Yes | Yes |
| SmartCursors™ | Yes | No |
| Volts Cursors | Yes | No |
| Time Cursors | Yes | No |
| Voltmeter | Yes | No |
| Vertical Sensitivity | 2 mV/div | 2 mV/div |
| Max. Sweep Speed | 2 ns/div | 2 ns/div |
| Vert/Hor Accuracy | 2% | 2% |
| Trigger Modes | Auto Level, Auto, Norm, TV Field, TV Line, Single Sweep | |
| Trigger Level Readout | Yes | No |
| Weight | 6.1 kg | 6.1 kg |
| Warranty | 3-year on parts and labor including CRT | |
| Price | \$2400 | \$1875 |

sensitivity to 0.25 div at 50 MHz, to 0.5 div at 150 MHz.

Accuracy is excellent: 2% at vertical, 2% at horizontal. And four-channel capability includes two channels optimized for logic signals.


Best of all, high performance comes with unmatched convenience. You can see it and feel it — in the

responsive controls and simple front-panel design, in extensive on-screen scale factor readouts, and in simplified trigger operation that includes Tek's Auto Level mode for automatic triggering on any signal. Start to finish, the GPS Series saves steps and simplifies tasks.

Get out in front! Call toll-free today to order, to get more details or a videotape demonstration.

1-800-433-2323

In Oregon, call collect 1-627-9000

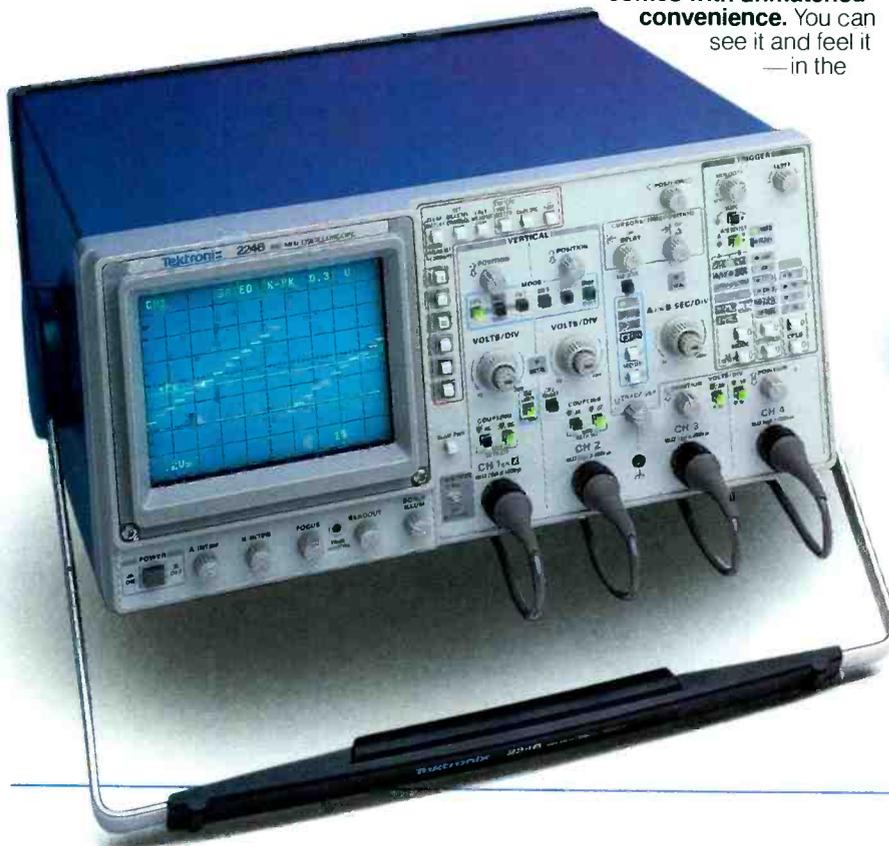


Featuring four channels, flexible triggering, extensive CRT readouts and push-button ease of use, the new Tek 2246 (left) and 2245 (above) bring high-quality, low-cost analysis to diverse applications in digital design, field service and manufacturing.

Tektronix®
COMMITTED TO EXCELLENCE

Circle (2) on Reply Card

ZENITH

VIDEO ACCESSORY HEADQUARTERS

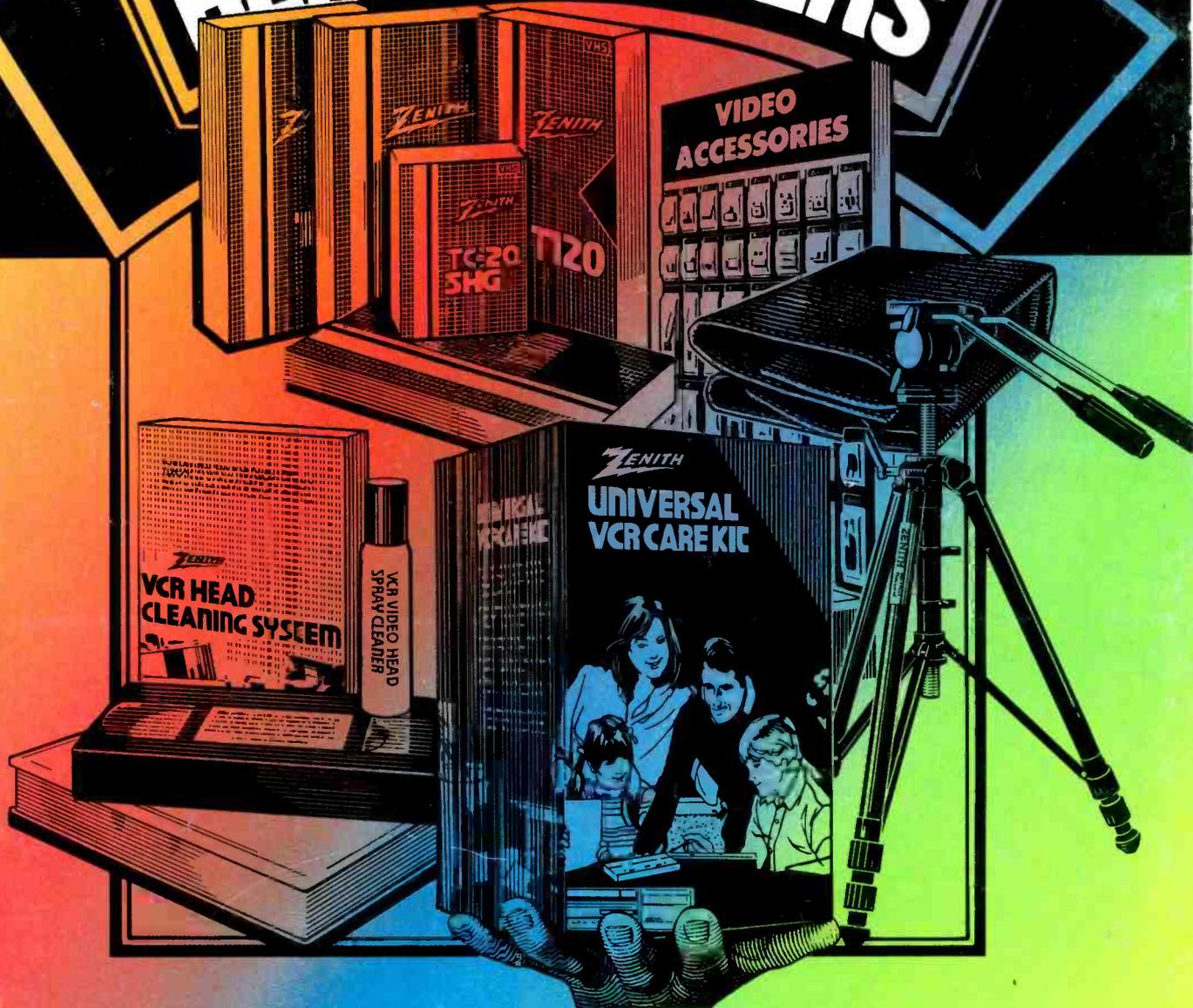

GET IN TOUCH WITH YOUR ZENITH DISTRIBUTOR'S
ACCESSORY SALES MANAGER AND LEARN HOW
YOU CAN MAKE THE MOST OF THE

Springtime '87 Video Accessory Promotion

Zenith Service, Parts & Accessories • 11000 Seymour Avenue • Franklin Park, Illinois • A Division of Zenith Electronics Corporation